

TEAM CLOWNTM PRODUC

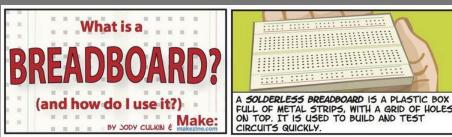

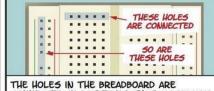




CONNECTED IN PATTERNS THAT ALLOW YOU TO ATTACH COMPONENTS TO EACH OTHER AND TO POWER AND GROUND.








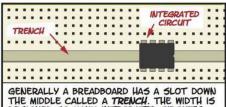BATTERY OR OTHER POWER SOURCE TO POWER AND GROUND TO RUN OUR CIRCUIT



CIRCUITS QUICKLY.



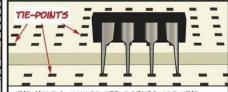

THE HOLES, CALLED TIE-POINTS, ARE THE SAME DISTANCE APART AS THE PINS ON MANY ICS AND OTHER COMPONENTS.




EACH OF THE LONG SIDES OF THE BOARD THAT GET ATTACHED TO POWER AND GROUND. THESE LINES ARE CALLED DISTRIBUTION BUSES.


ROWS OF FIVE CONNECTED TIE-POINTS RUN

PERPENDICULAR TO THE BUSES. TO CONNECT COMPONENTS, PUT THEIR LEADS IN TIE-POINTS IN THE SAME ROW.

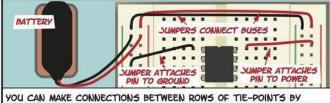HERE A RESISTOR IS CONNECTED TO POWER AND TO THE ANODE OF AN LED. THE OTHER LEAD OF THE LED ATTACHES TO GROUND.



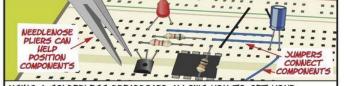INSERTING SHORT PIECES OF WIRE CALLED JUMPERS BETWEEN HOLES IN




USING A SOLDERLESS BREADBOARD ALLOWS YOU TO GET YOUR CIRCUIT UP AND RUNNING QUICKLY SO YOU CAN TEST IT. ONCE YOU HAVE IT JUST RIGHT, YOU CAN BUILD A MORE PERMANENT VERSION ON PERFBOARD OR A PCB!


Source: http://makezine.com/2016/12/22/breadboarding-quick-tips/

DIFFERENT ROWS

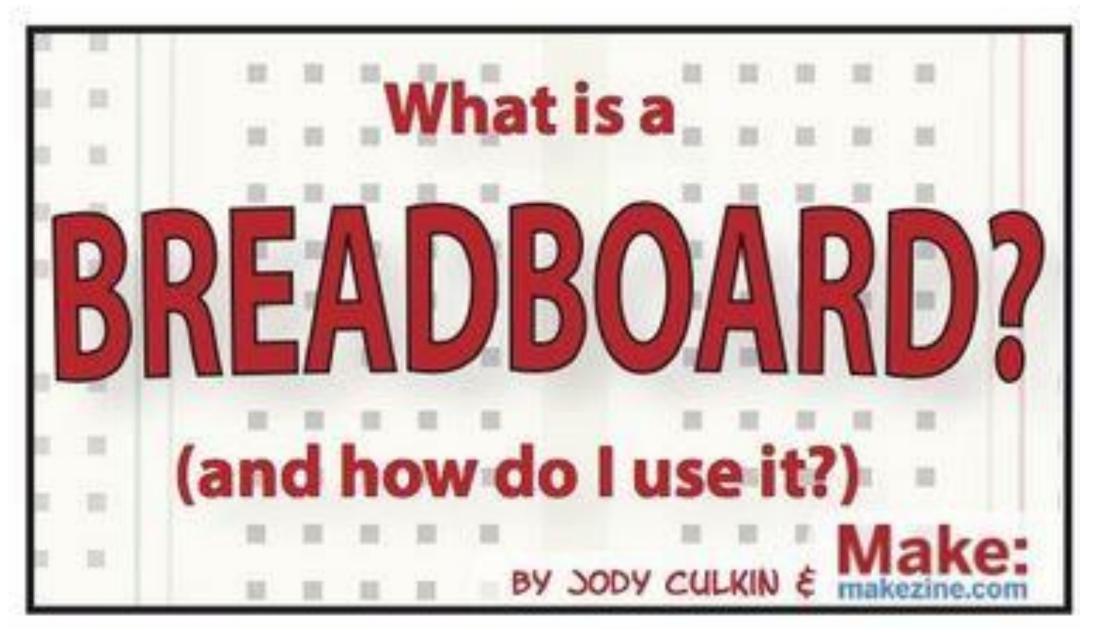
https://i1.wp.com/makezine.com/wp-content/uploads/2016/12/breadboardworkshop.jpg





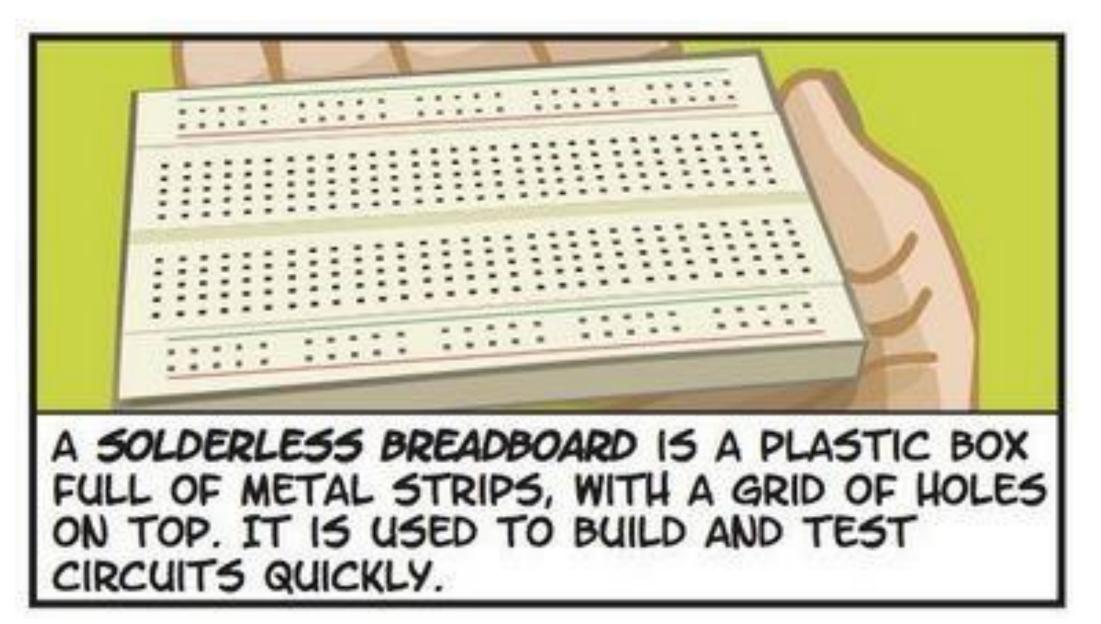




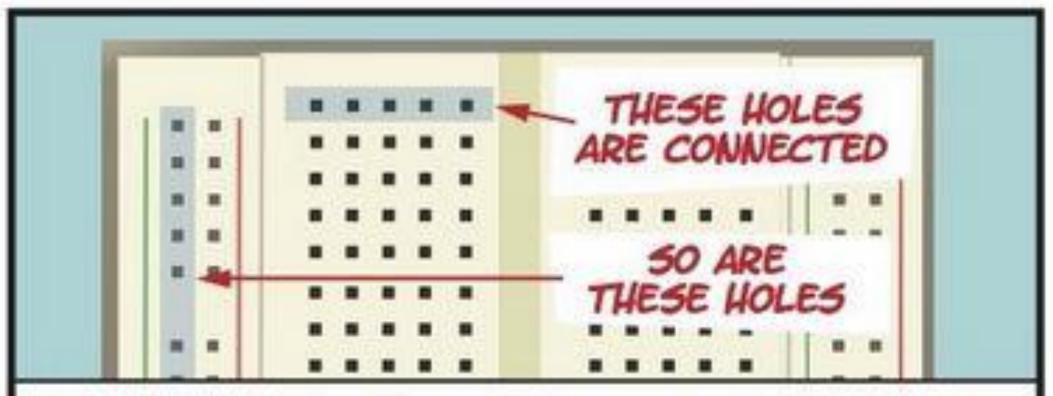


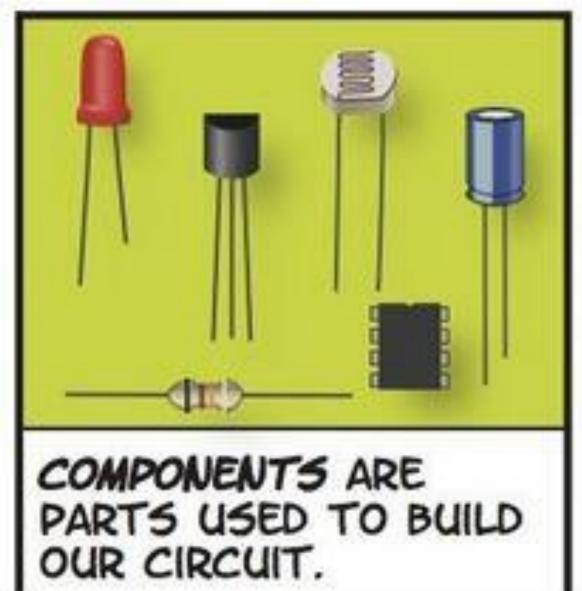
THE HOLES IN THE BREADBOARD ARE CONNECTED IN PATTERNS THAT ALLOW YOU TO ATTACH COMPONENTS TO EACH OTHER AND TO POWER AND GROUND.









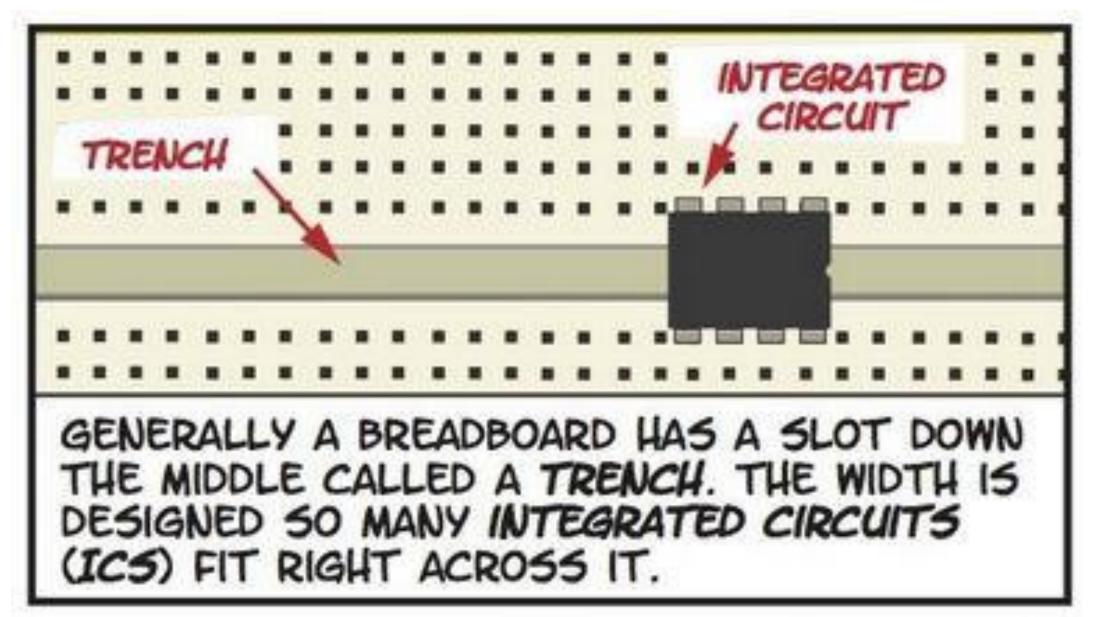

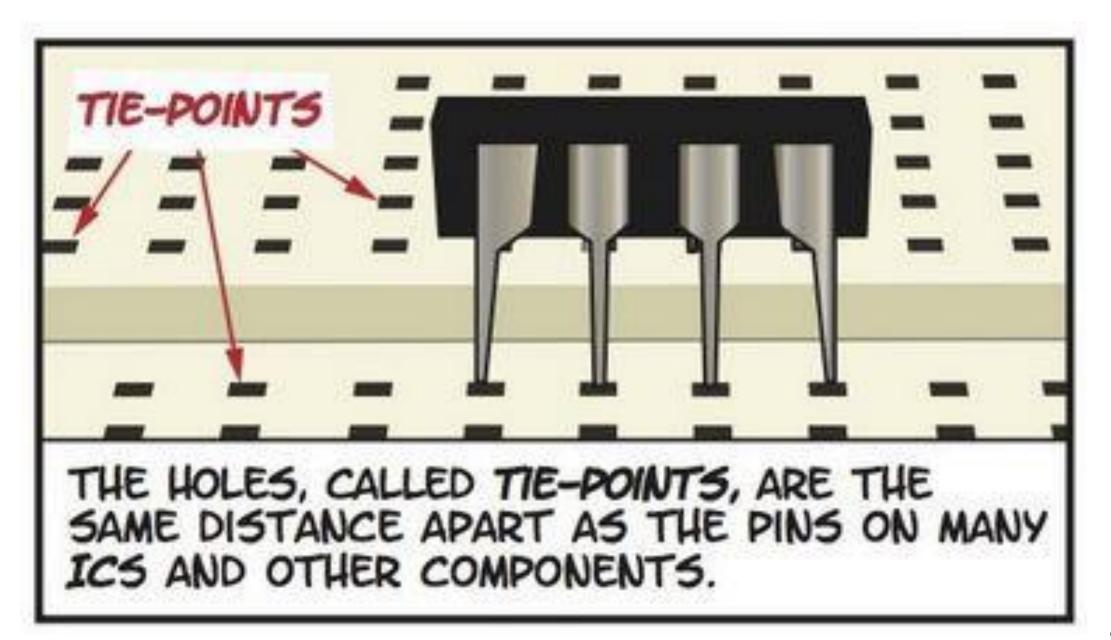

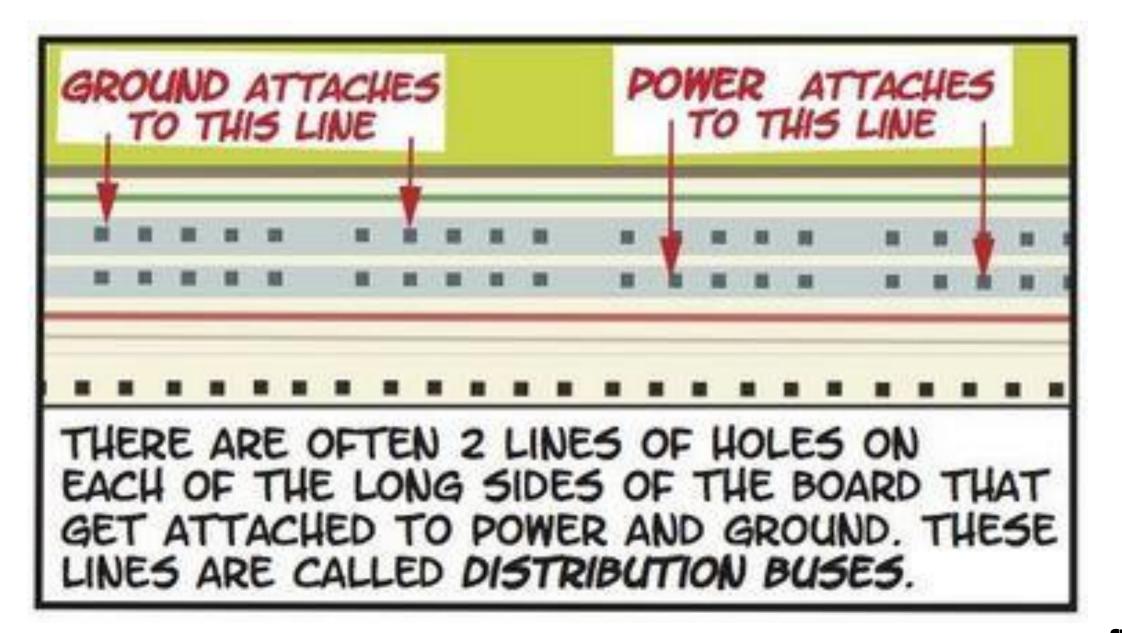

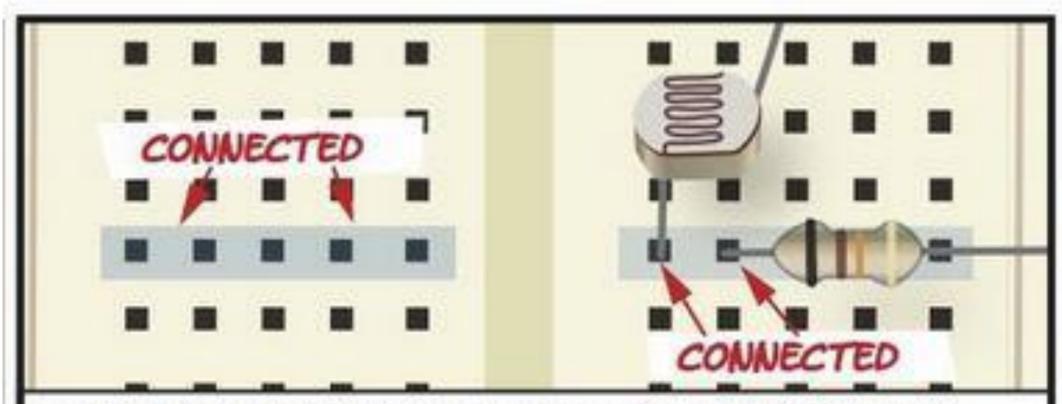

ROWS OF FIVE CONNECTED TIE-POINTS RUN PERPENDICULAR TO THE BUSES. TO CONNECT COMPONENTS, PUT THEIR LEADS IN TIE-POINTS IN THE SAME ROW.



