

OHM'S LAW AND ELECTRONIC CIRCUITS

ELECTRICAL CIRCUITS

All you need to be an inventor is a good imagination and a pile of junk.

-Thomas Edison

OHM'S LAW



Georg Simon **Ohm** (1787-1854)

$$I = V / R$$

I = Current (Amperes) (amps)


V = Voltage (Volts)

R = Resistance (ohms)

OHM'S LAW

- Ohm's Law explains the relationship between voltage (V or E), current (I) and resistance (R)
- The amount of current in a circuit is dependent on its resistance and the applied voltage. Specifically $I = V/R$
- If you know any two of the factors V, I, and R you can calculate the third.
- Current $I = V/R$
- Voltage $V = IR$
- Resistance $R = V/I$

1 ampere = 1 coulomb per second

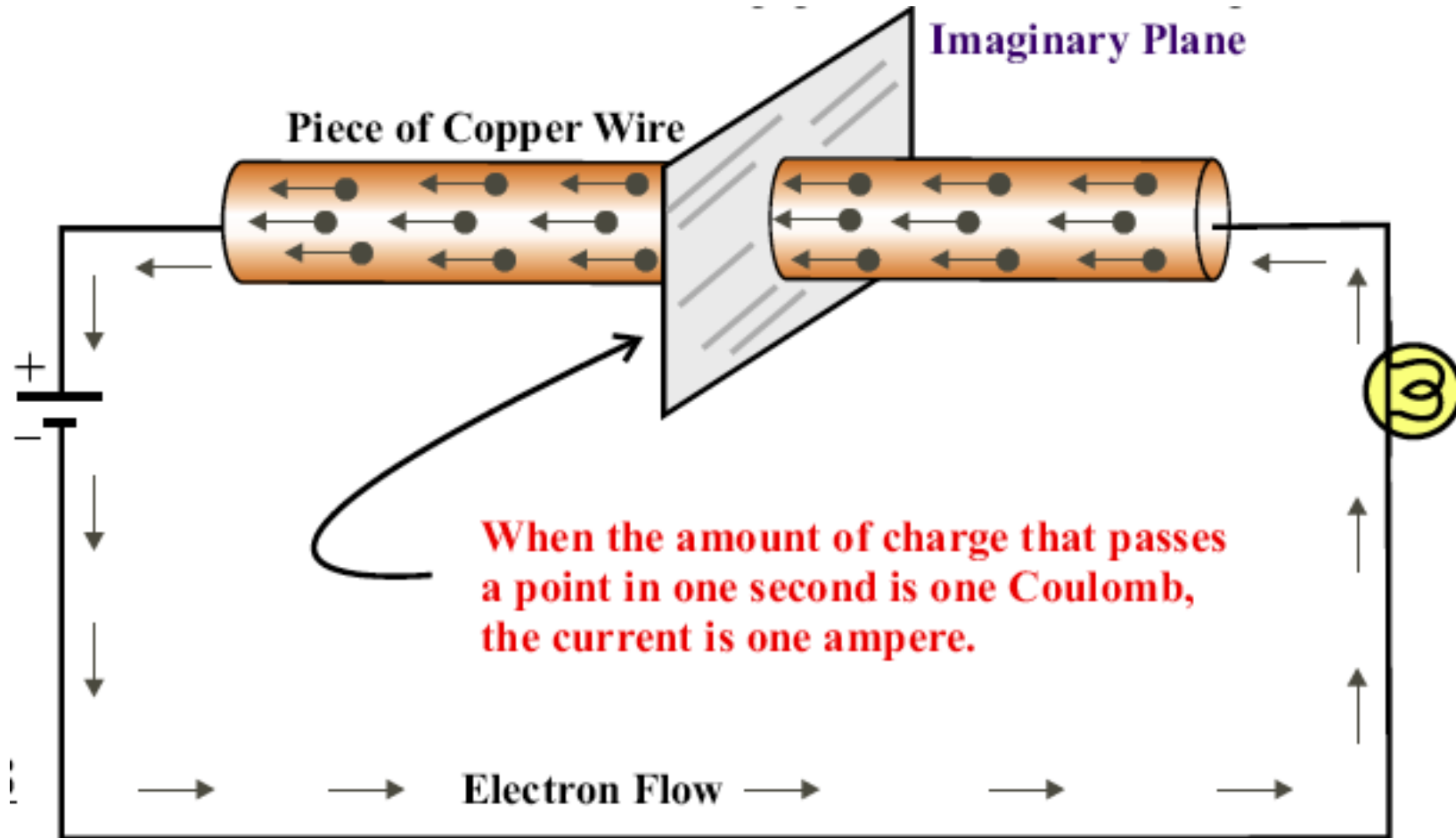

CHART

Quantity	Symbol	Unit of Measurement	Unit Abbreviation
Current	I	Ampere ("Amp")	A
Voltage	E <i>or</i> V	Volt	V
Resistance	R	Ohm	Ω

VOLTAGE (V)

- It is the push or pressure behind current flow through a circuit, and is measured in (V) volts.



CURRENT


- Current refers to the quantity/volume of electrical flow. Measured in Amps (A)
- The symbol for current is I (for intensity) and is measured in **amperes**




RESISTANCE

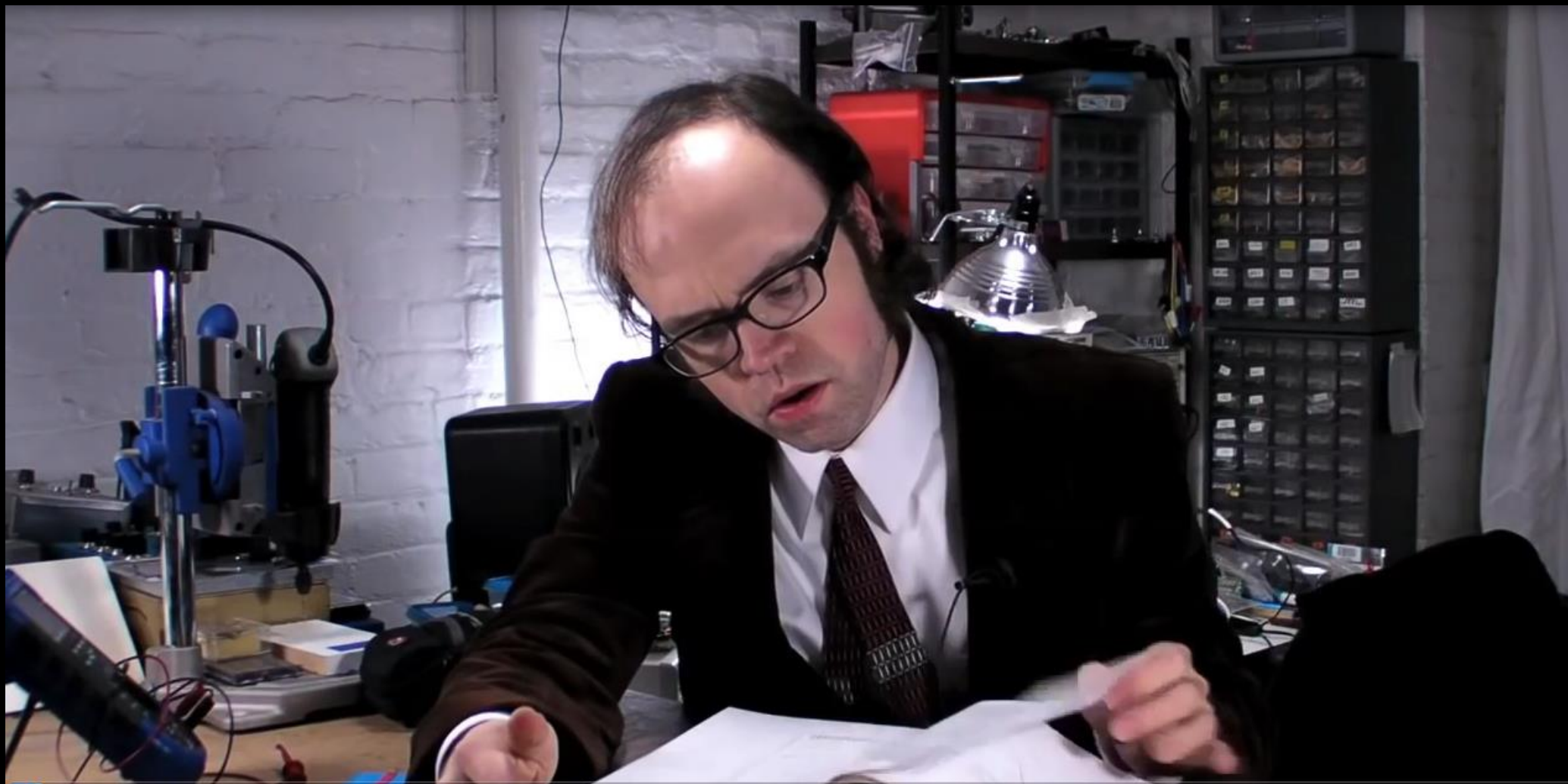- Resistance to the flow of the current. Measured in Ohms Ω
- Opposition to the flow of current is termed resistance.
- The fact that a wire can become hot from the flow of current is evidence of resistance.
- Conductors have very little resistance.
- Insulators have large amounts of resistance.






TRICK TO REMEMBER OHM'S LAW

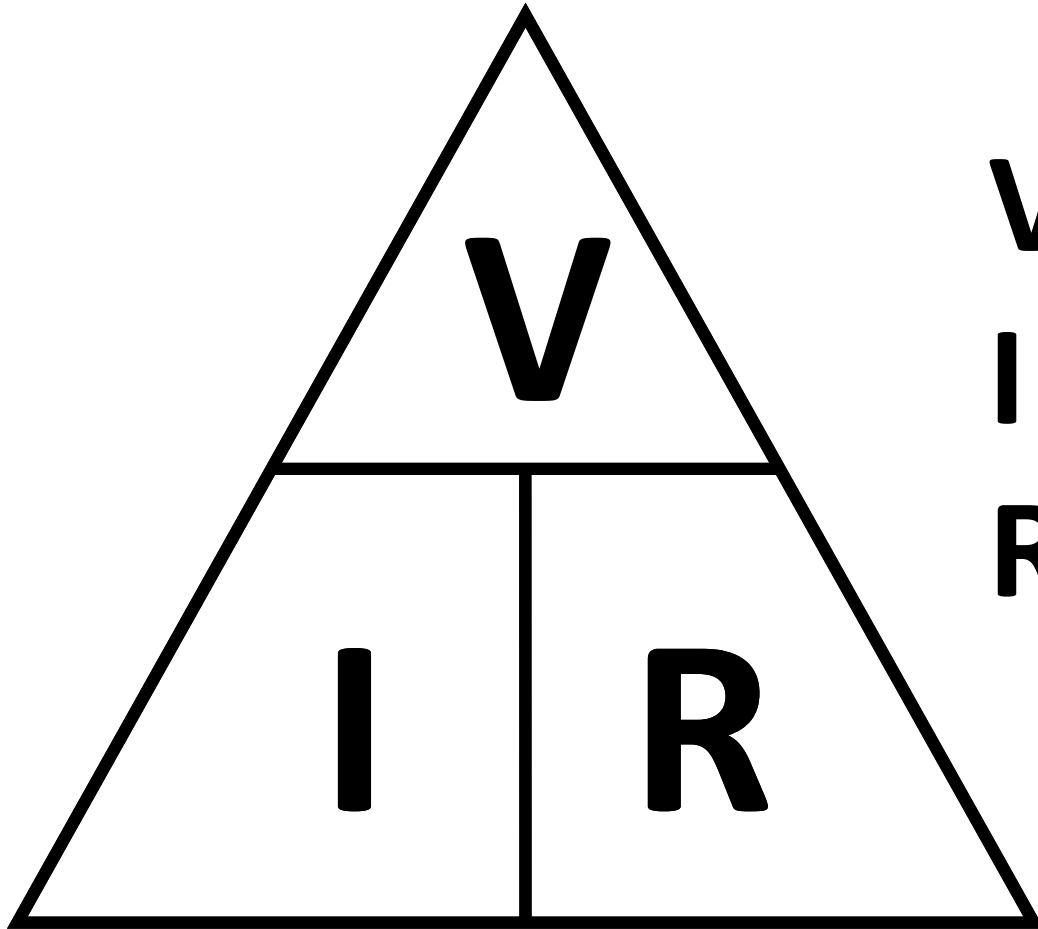


V = Voltage = Volts

I = Amperes = Amps

R = Resistance = Ohms

 **Ω**

TRICK TO REMEMBER OHM'S LAW

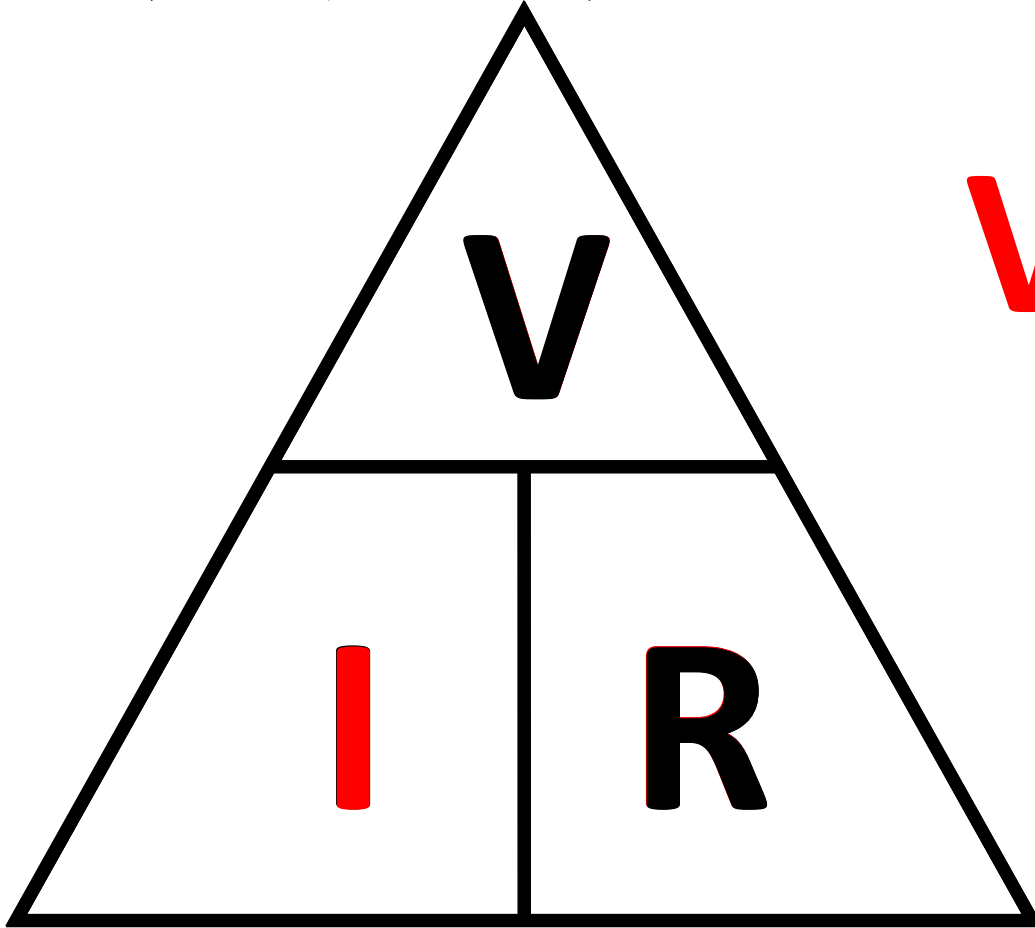


$$V = I * R$$

$$I = \frac{V}{R}$$

$$R = \frac{V}{I}$$

HOW DO CALCULATE CURRENT?

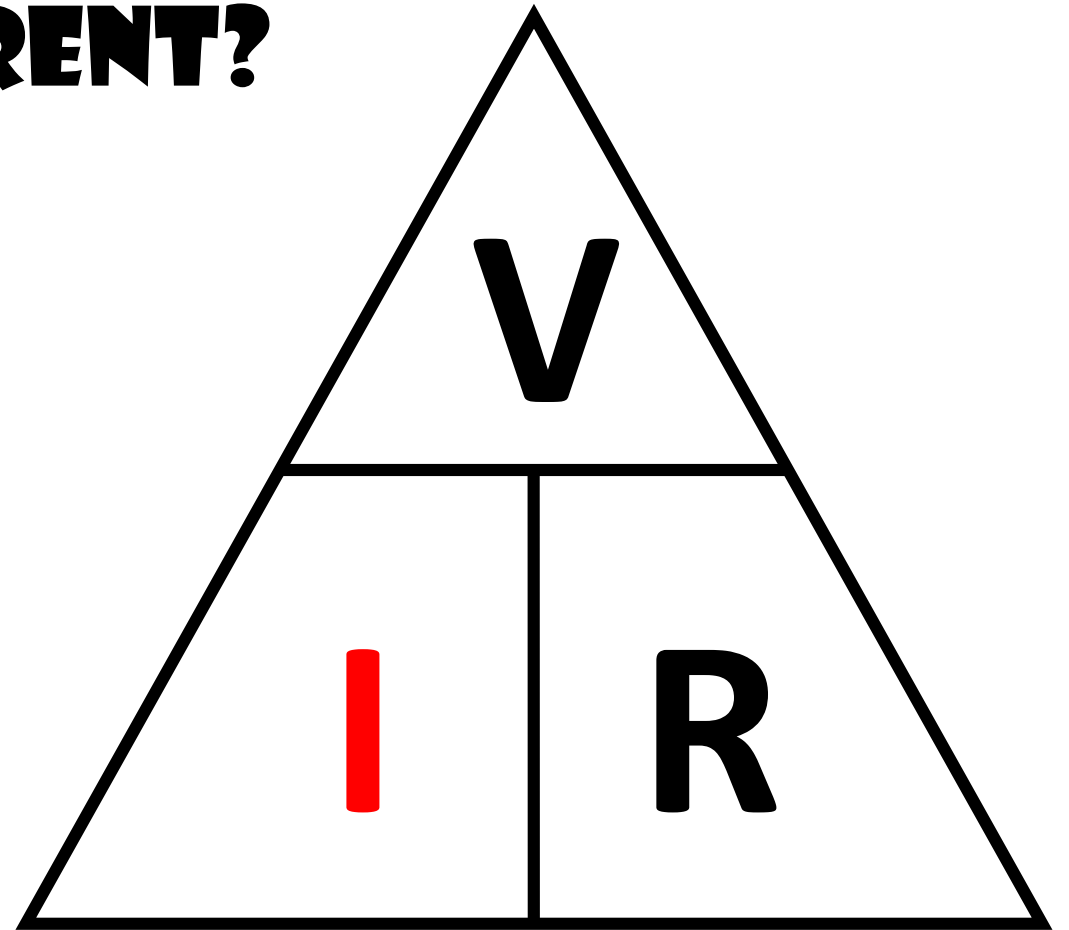- Voltage is 5V
- Resistance is 220 Ω
- Current = Amp ?




$$I = \frac{V}{R} \quad I = \frac{5}{220}$$

$$I = 22.7 \text{ mA}$$

HOW DO CALCULATE RESISTANCE?

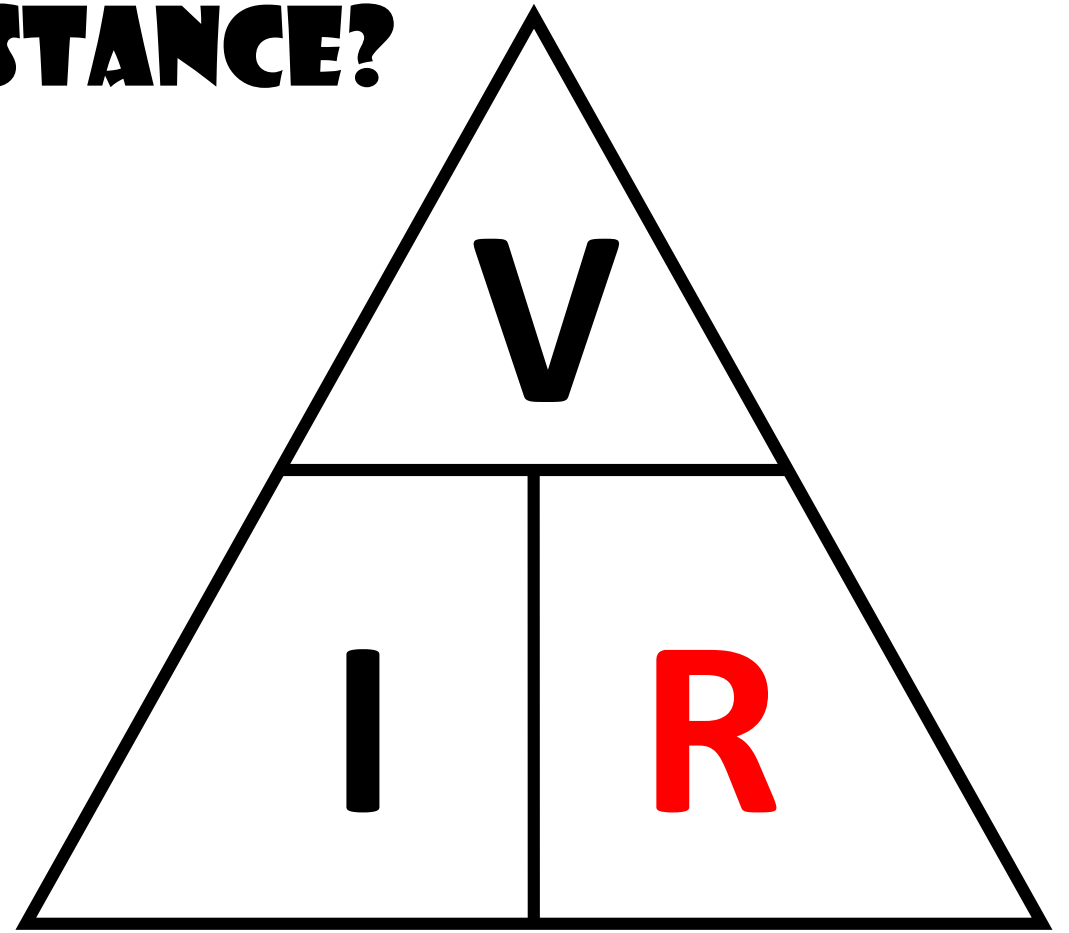- Voltage is 5V
- Current is 10mA
- Resistance = Ohm?




$$R = \frac{V}{I}$$

$$R = \frac{5}{.010 \text{ amp}}$$

$$R = 500 \, \Omega$$

HOW DO CALCULATE VOLTAGE?

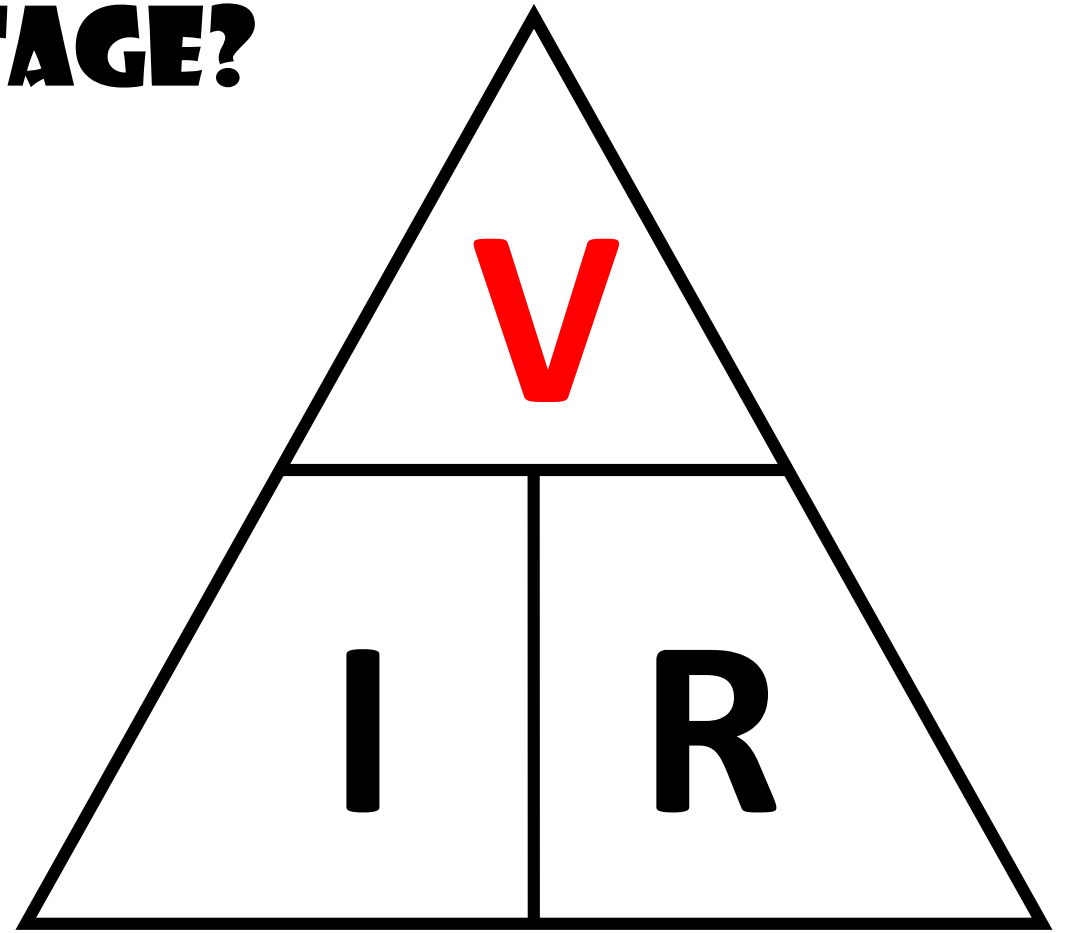- Resistance is $1\text{K}\Omega$
- Current is 200 mA
- Voltage = V ?



$$V = I * R$$

$$V = .2 * 1\text{K}\Omega$$

$$V = 200\text{v}$$

WOULD THIS WORK?



WOULD THIS WORK?



WOULD THIS WORK?





THE CENTRAL CONCEPT: CLOSED CIRCUIT



CIRCUIT DIAGRAM

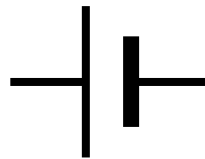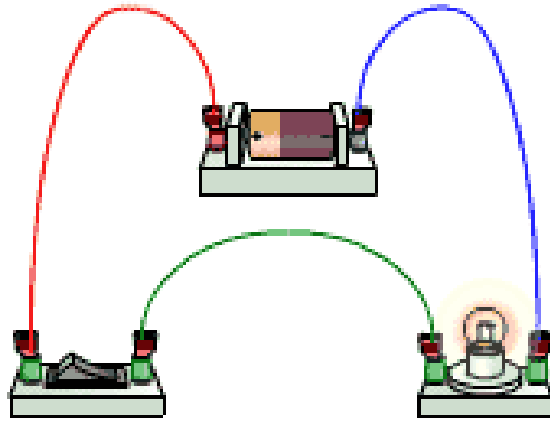
Scientists usually draw electric circuits using symbols;



cell




lamp

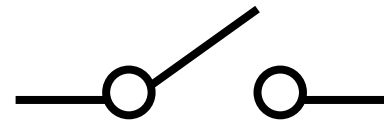

switch



wires

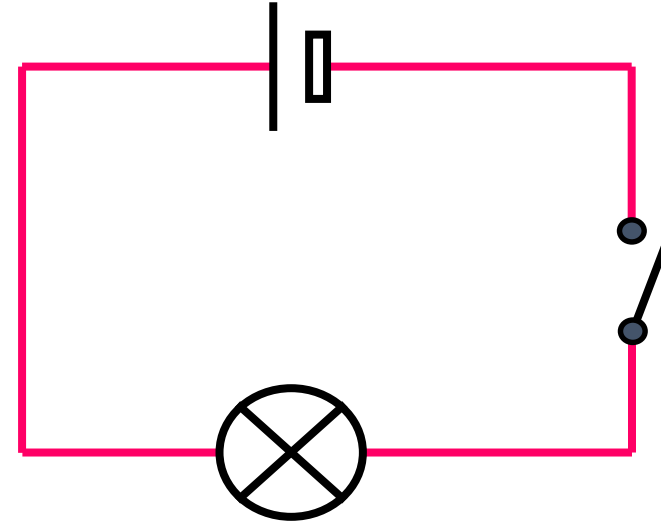


Current is Directly Proportional to Voltage for a Constant Resistance

- For the same resistance, 330Ω , if the voltage is increased, then the current will increase as well

$R = 330\Omega$, Volts = 1V, Current will = 3.0mA
 $R = 330\Omega$, Volts = 2V, Current will = 6.0mA
 $R = 330\Omega$, Volts = 5V, Current will = 15.1mA
 $R = 330\Omega$, Volts = 12V, Current will = 36.3mA
 $R = 330\Omega$, Volts = 15V, Current will = 45.5mA
 $R = 330\Omega$, Volts = 25V, Current will = 75.8mA


OHM' s LAW

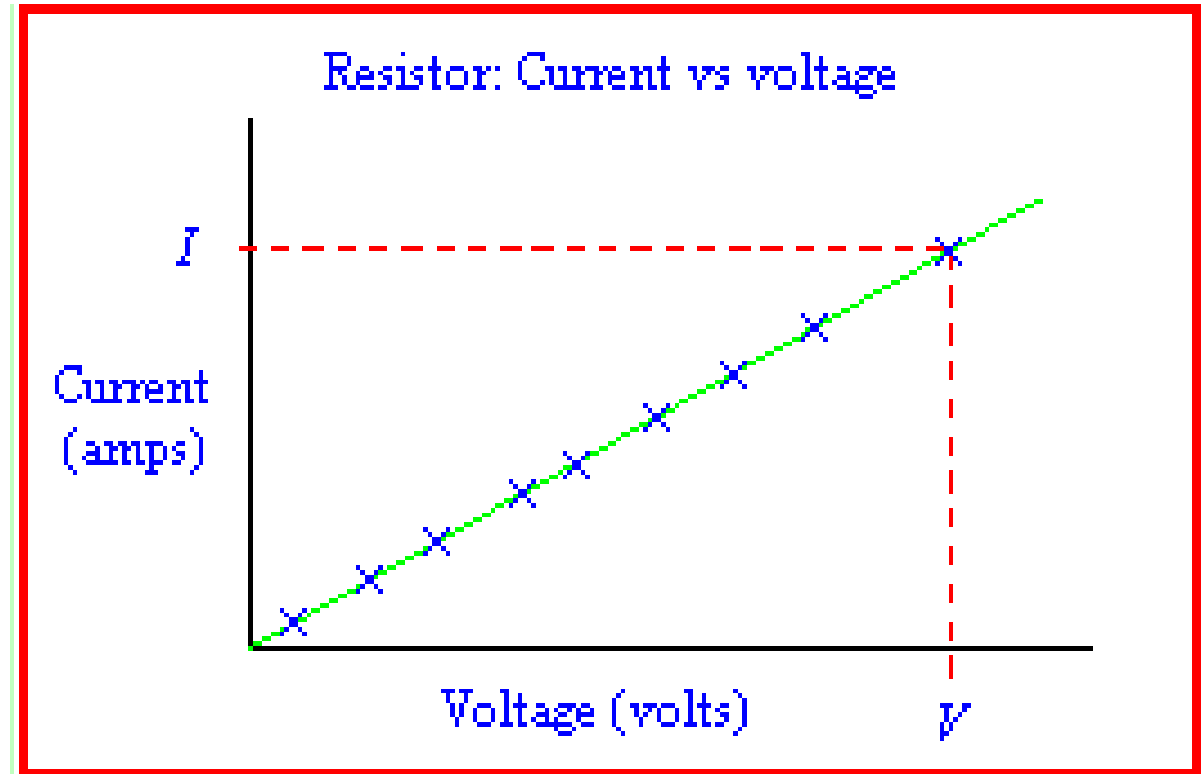

Current is Inversely Proportional to Resistance for a Constant Voltage


Volts = 1V, R = 1Ω, Current will = 1A
Volts = 1V, R = 2Ω, Current will = 500mA
Volts = 1V, R = 4Ω, Current will = 250mA
Volts = 1V, R = 6Ω, Current will = 167mA
Volts = 1V, R = 8Ω, Current will = 125mA
Volts = 1V, R = 10Ω, Current will = 100mA
Volts = 1V, R = 12Ω, Current will = 83.3mA

OHM'S LAW

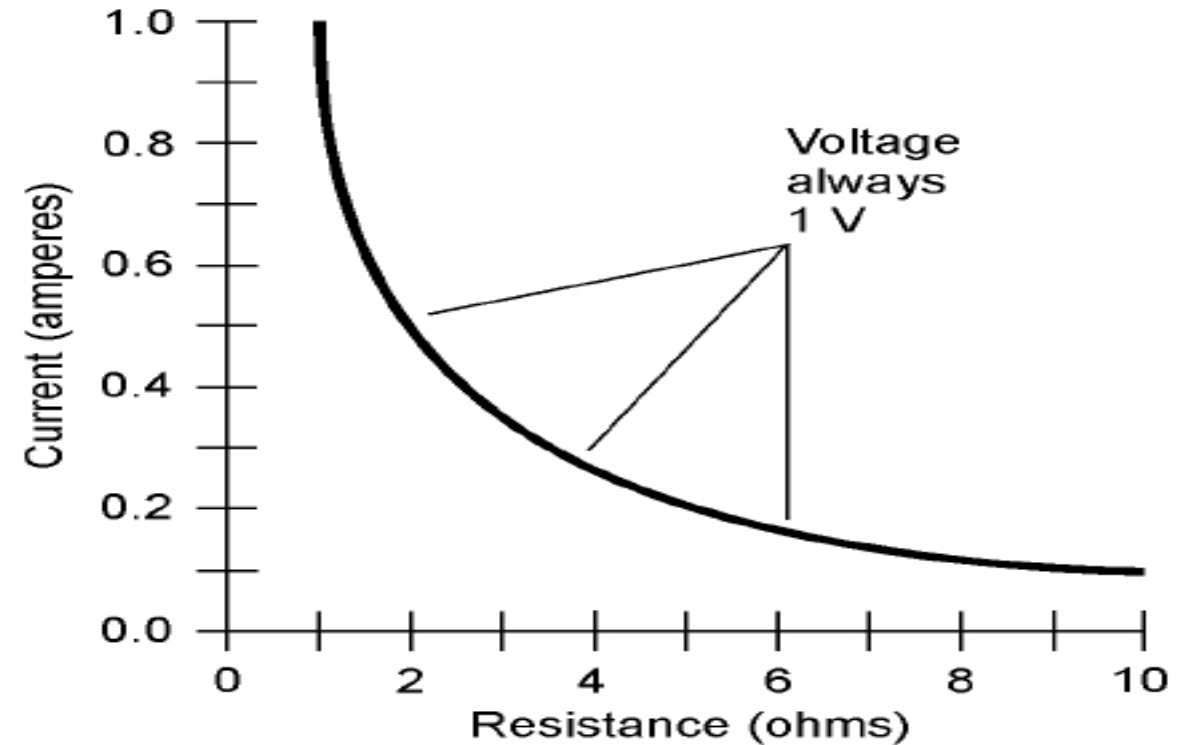

MEASURING VOLTAGE

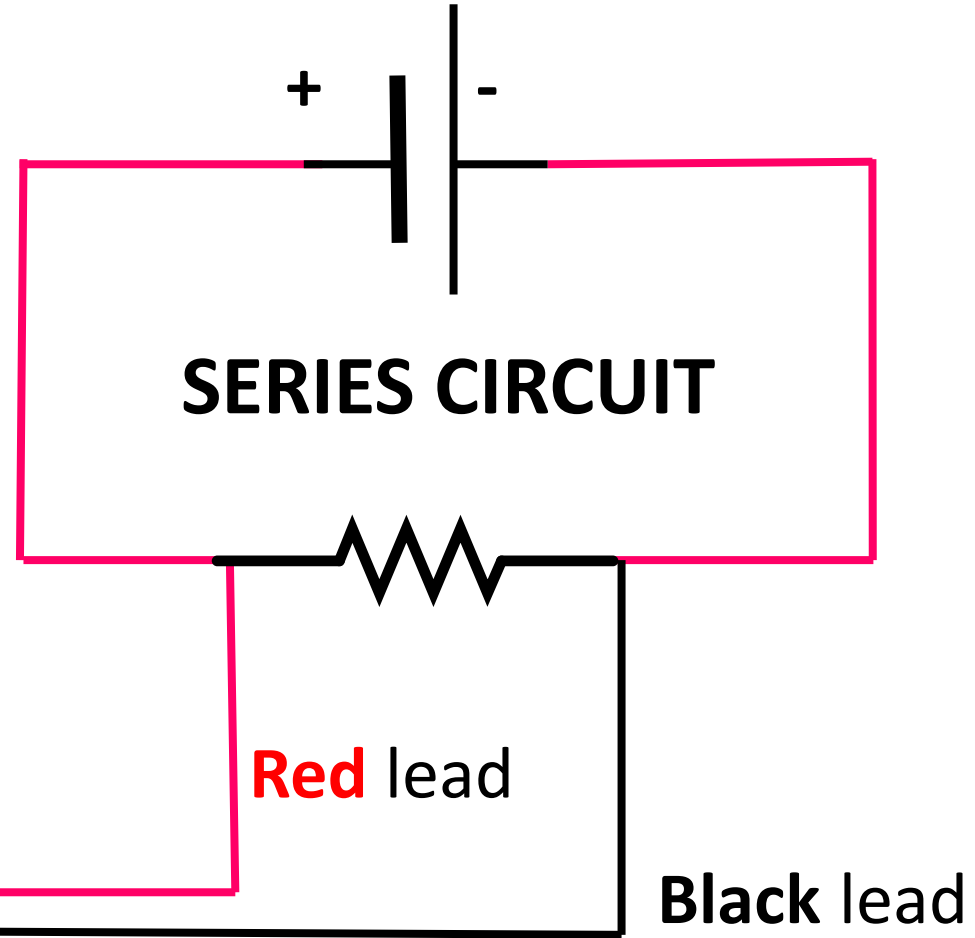
- Set the DMM to Ω (to measure Resistance)
- Set it to the closest value above the target resistor you are measuring



This is how we measure volts in a circuit

MEASURING CURRENT

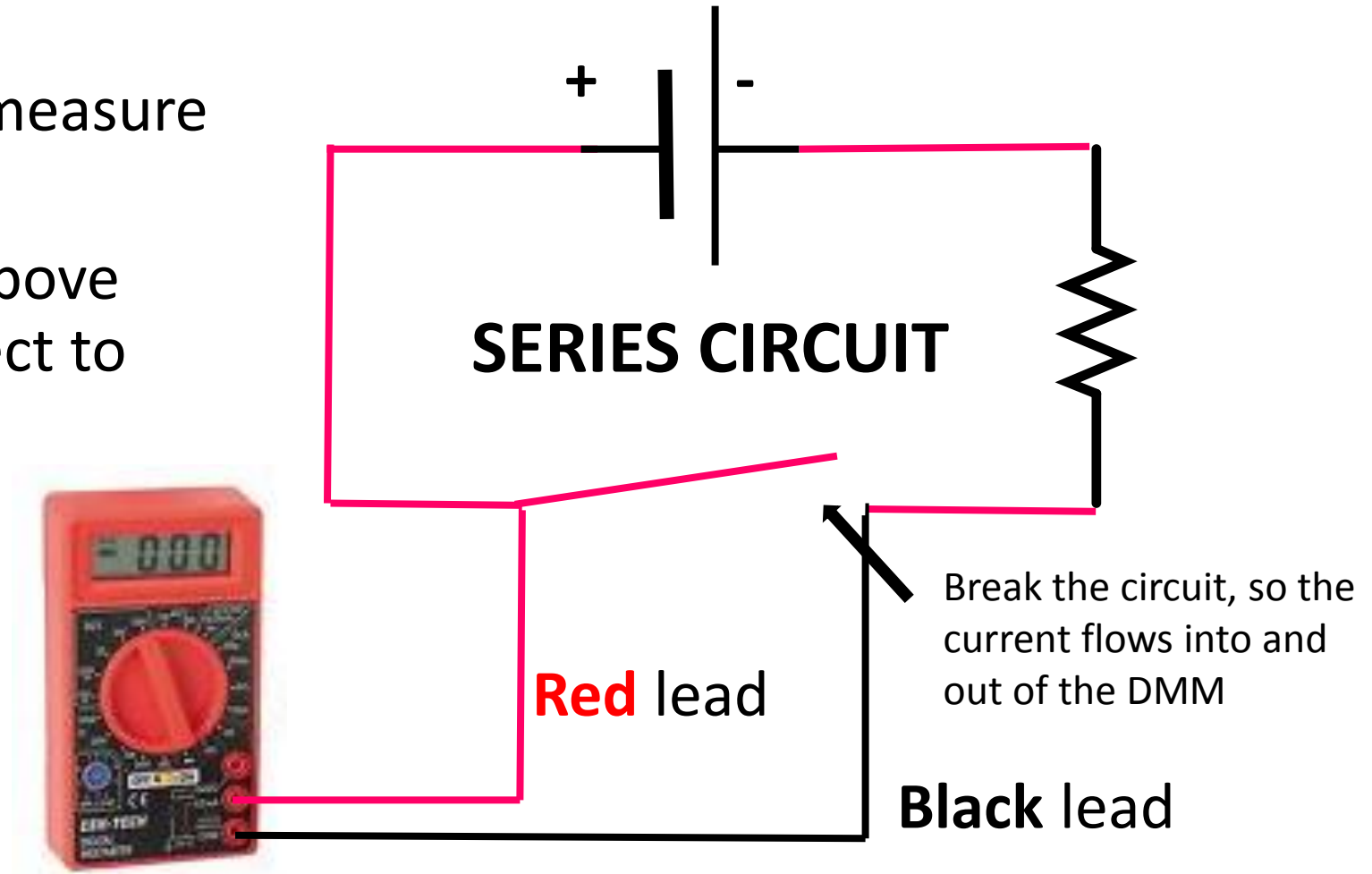- Set the DMM to Amps (to measure Current)
- Set it to the closest value above the target current you expect to measure



This is how we measure Amps in a circuit

GENERAL RULE.


1. Assuming the resistance does not change:
 - As voltage increases, current increases.
 - as voltage decreases, current decreases.

2. Assuming the voltage does not change:
 - As resistance increases, current decreases.
 - As resistance decreases, current increases.


RECAP!!

- What is Voltage?
- What is Current?
- What is Resistance?

SIMPLE CIRCUITS

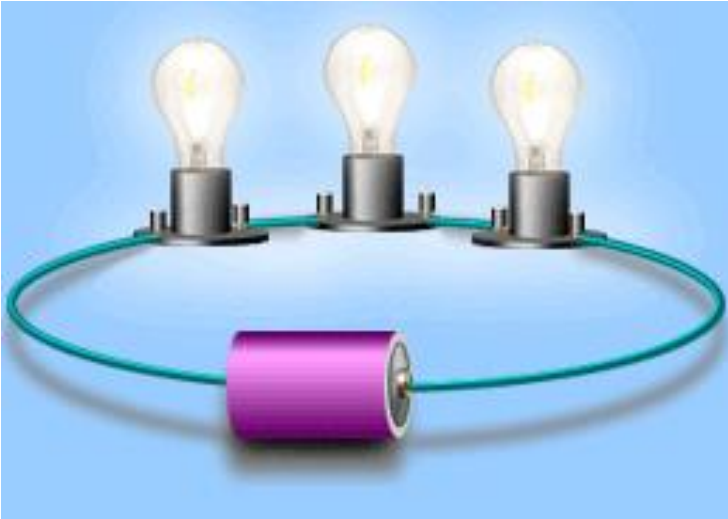


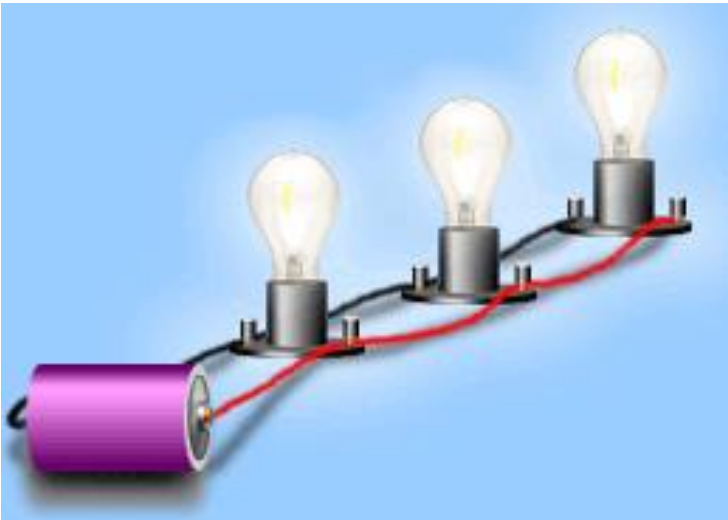- Series circuit
 - All in a row
 - 1 path for electricity
 - 1 light goes out and the circuit is broken



- Parallel circuit
 - Many paths for electricity
 - 1 light goes out and the others stay on



RESISTOR COLOR CHART

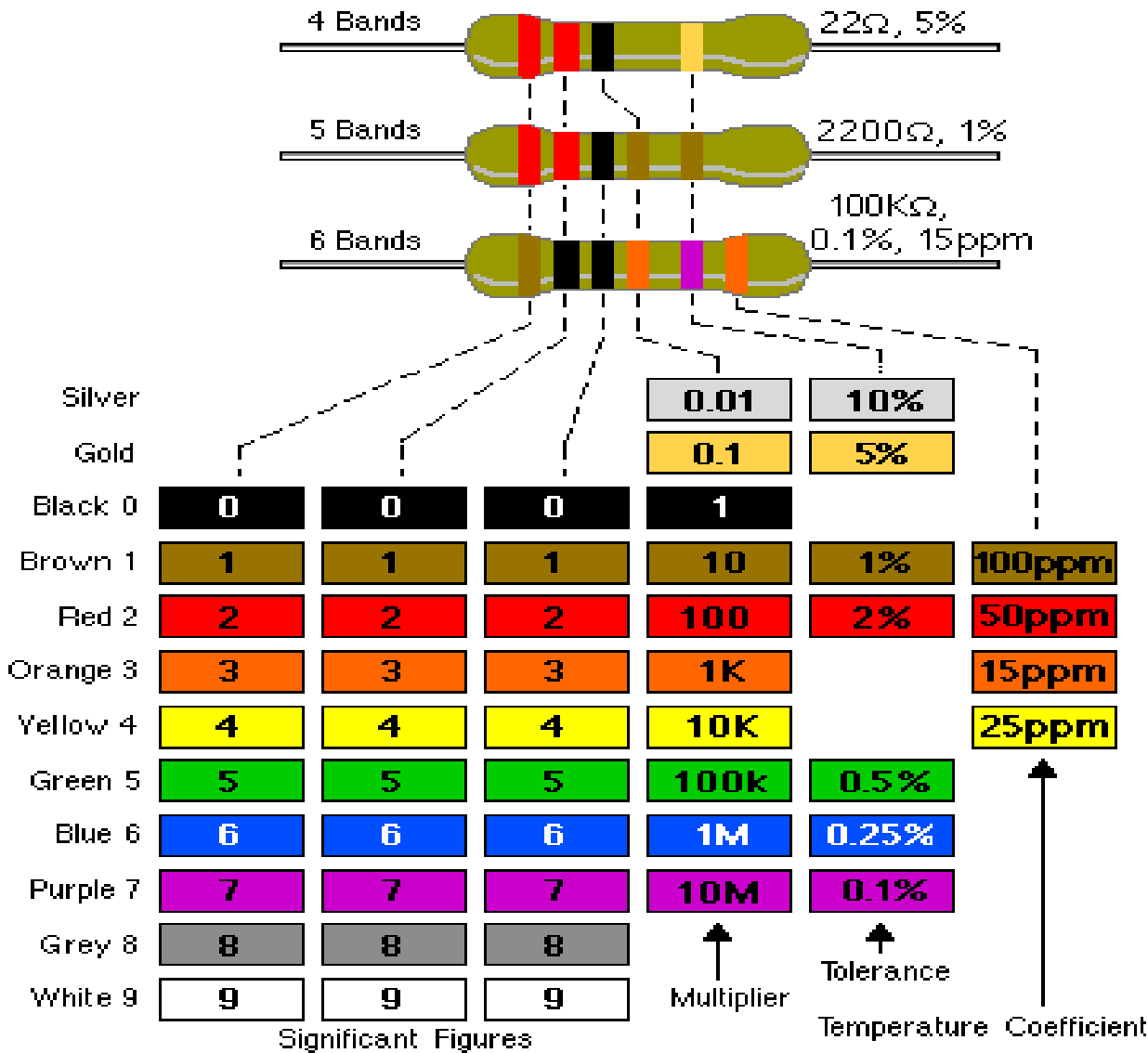

Resistor Color Code System

LAB TIME

TESTING DIFFERENT RESISTOR CIRCUIT

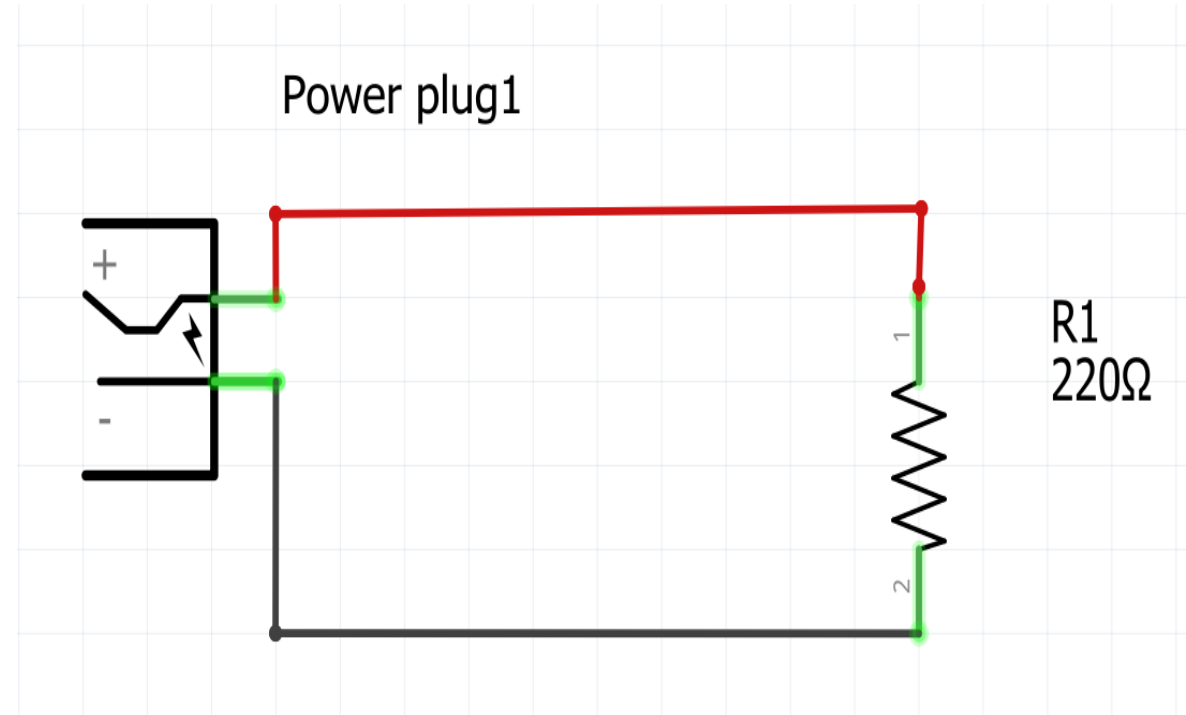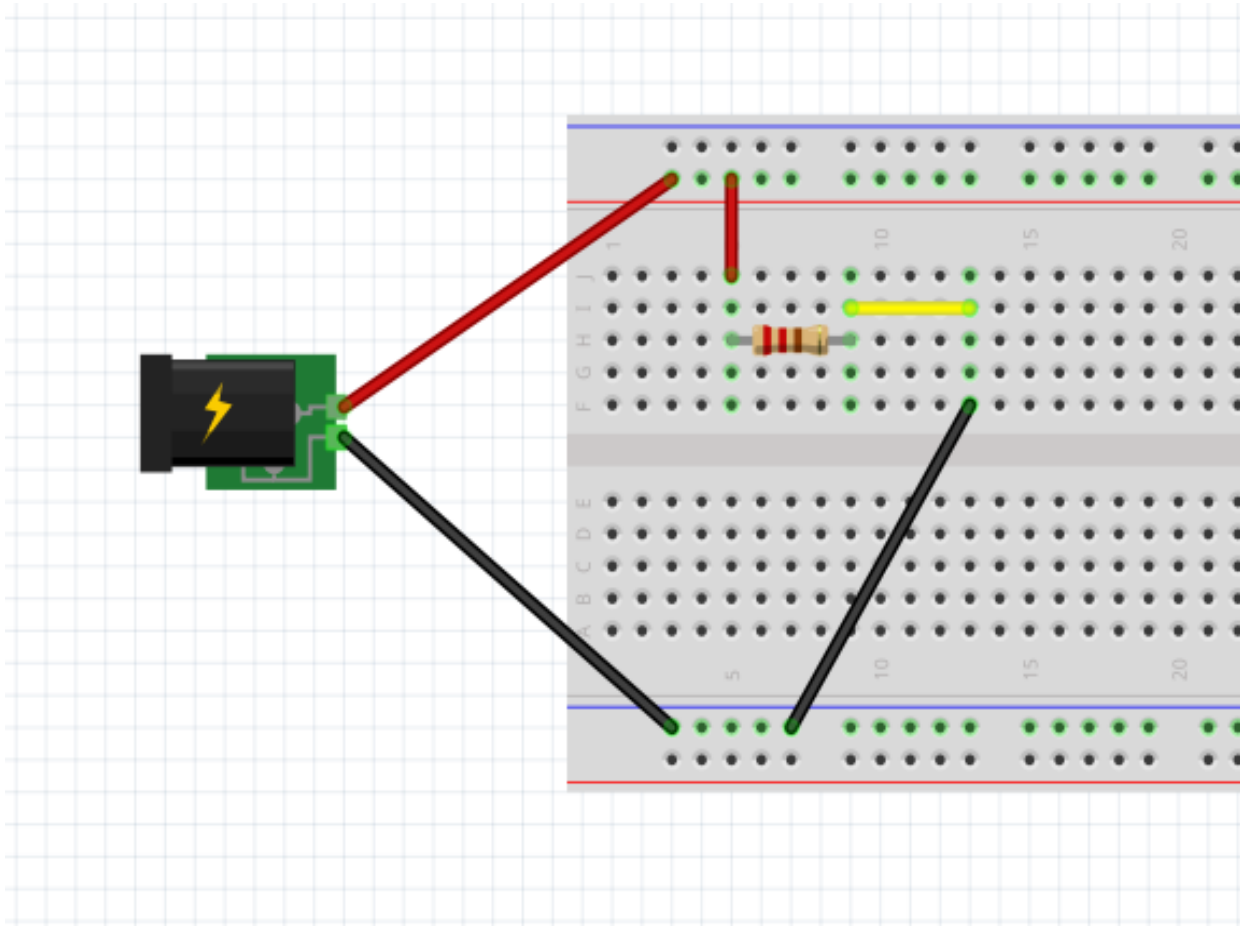

LOG SOME DATA

- Open your log books
- On the next available space
 - Note the Date
 - Draw a table (add table label that says “for a fixed 5 volt power supply”


Resistor Marked Value	Resistor Measured Value	Measured Voltage	Expected Current	Measured Current

MAKE SOME MEASUREMENTS

- On your lab book table, note the marked value of each Resistor
- The measure each Resistor and record the measured value
 - How do we do that?

MAKE SOME MEASUREMENTS

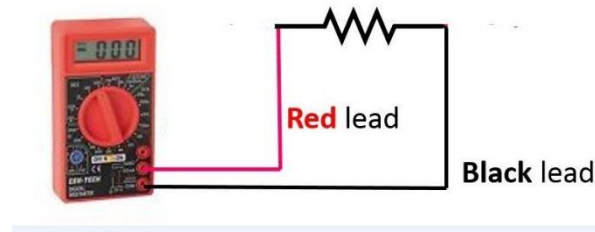
- On your lab book table, note the marked value of each Resistor
- The measure each Resistor and record the measured value
 - How do we do that?



MAKE SOME MEASUREMENTS

- On your lab book table, note the marked value of each Resistor
- The measure each Resistor and record the measured value


- How do we do that?

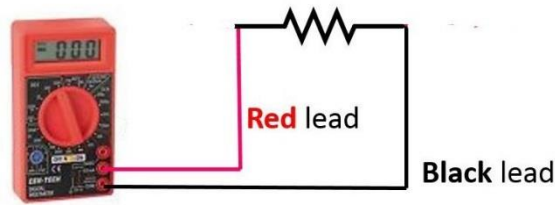


- You have a 5 Volt supply, but it is not exact, so measure it too
 - How do we do that?

MAKE SOME MEASUREMENTS

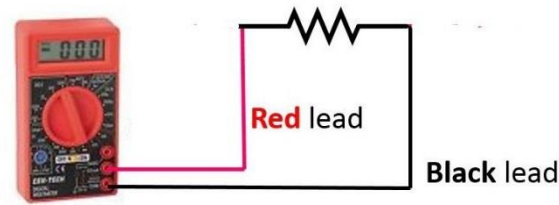- On your lab book table, note the marked value of each Resistor
- The measure each Resistor and record the measured value
 - How do we do that?



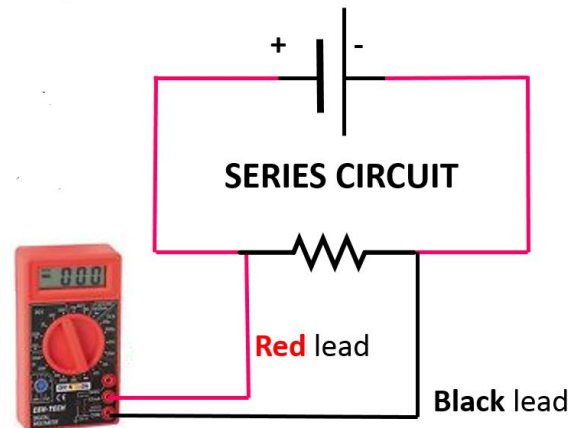
- You have a 5 Volt supply, but it is not exact, so measure it too
 - How do we do that?



MAKE SOME MEASUREMENTS


- The measure each Resistor and record the measured value

- How do we do that?

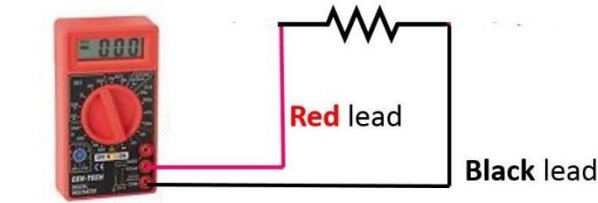

- You have a 5 Volt supply, but it is not exact, so measure it too

- How do we do that?

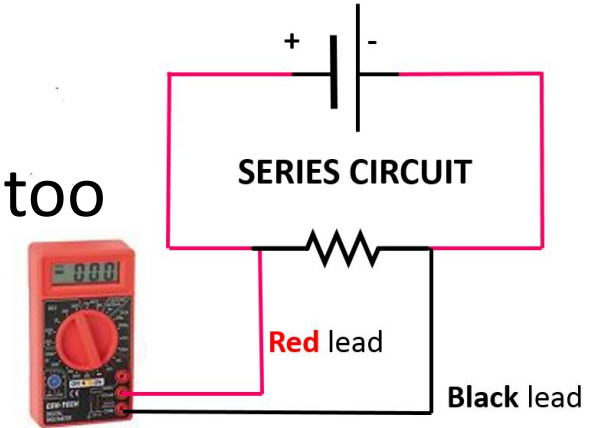


- Now Measure the current for each Resistor

- How do we do that?

MAKE SOME MEASUREMENTS


- The measure each Resistor and record the measured value

- How do we do that?

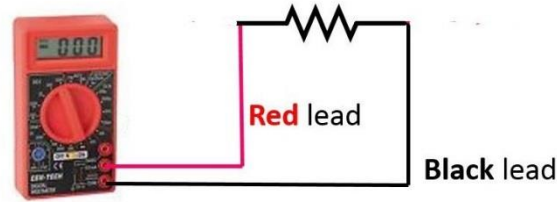


- You have a 5 Volt supply, but it is not exact, so measure it too

- How do we do that?

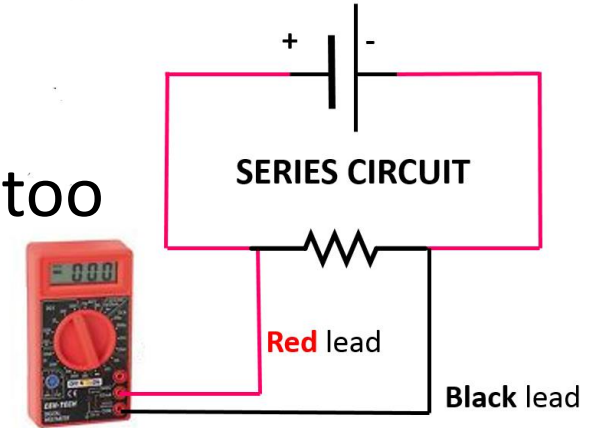


- Now Measure the current for each Resistor

- How do we do that?

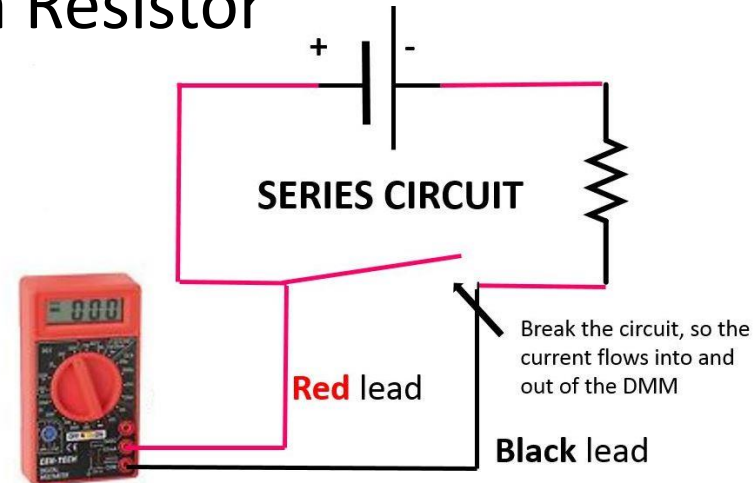


TRICK TO REMEMBER OHM'S LAW

$$V = I * R$$

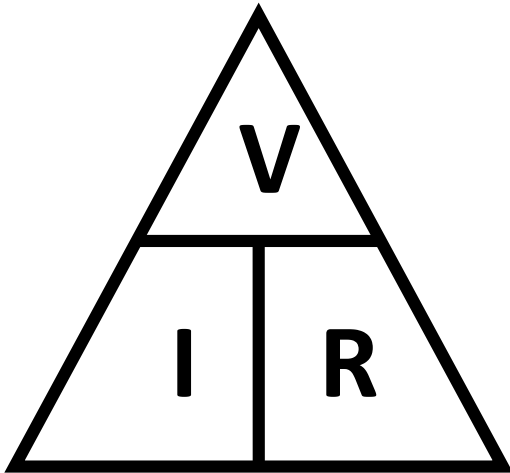


$$I = \frac{V}{R}$$

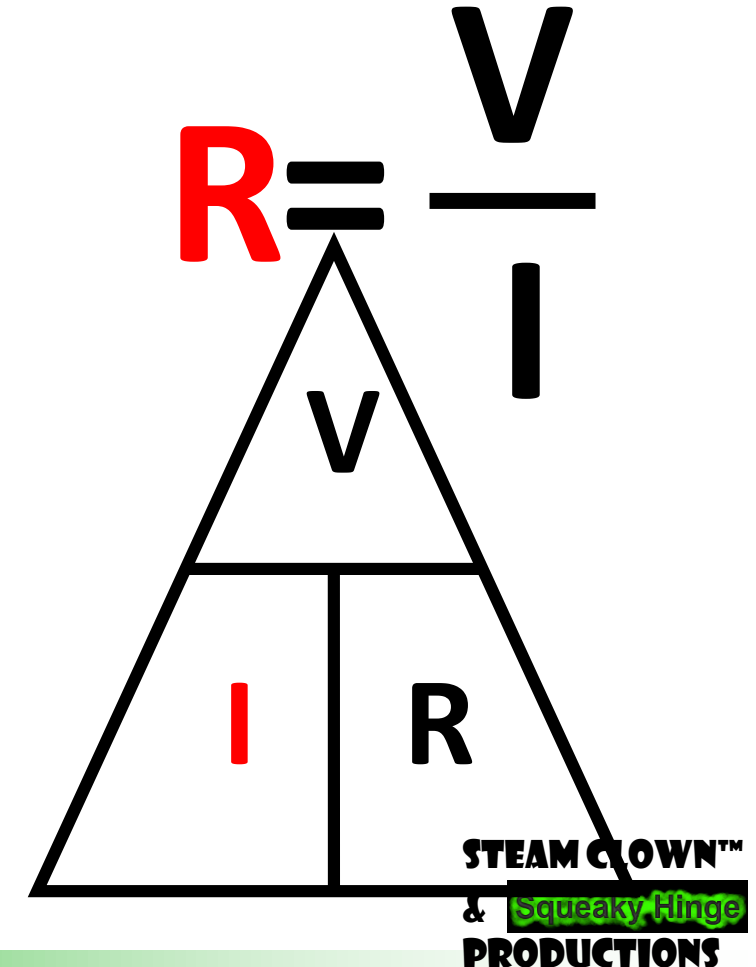

OHM'S LAW PRACTICE SHEET #1

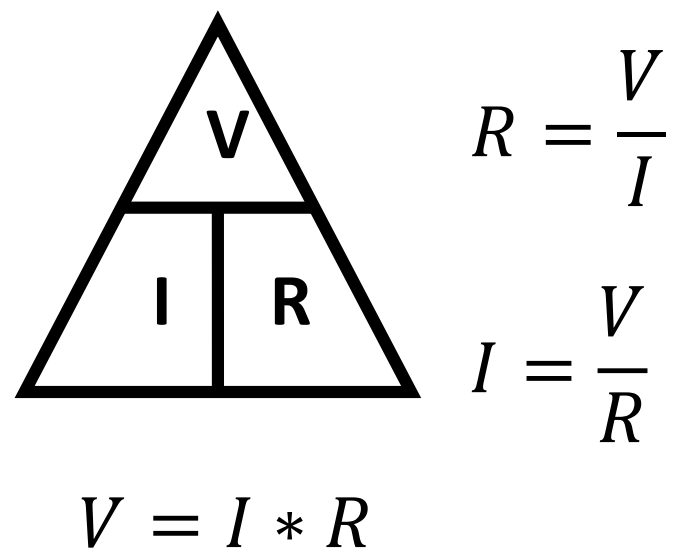- The only way to master Ohm's law is with practice



Volts (V)	Resistance (Ω)	Current (Amps)
5V	20K Ω	_____ A
_____ V	5 Ω	2A
12V	_____ Ω	40mA
_____ V	330 Ω	500mA
5V	220 Ω	_____ A
5V	_____ Ω	35mA
24V	1.2K Ω	_____ A

REFERENCE SLIDES

RESISTANCE

- Opposition to the flow of current is resistance
- The fact that a wire can become hot from the flow of current is evidence of resistance.
- Conductors have very little resistance.
- Insulators have large amounts of resistance.

CONDUCTORS

- Have 1 valence electron
- Materials in which electrons can move freely from atom to atom are called conductors.
- In general all metals are good conductors.
- The purpose of conductors is to allow electrical current to flow with minimum resistance.


INSULATORS

- Have 8 valence electrons
- Materials in which electrons tend to stay put and do not flow easily from atom to atom are termed insulators.
- Insulators are used to prevent the flow of electricity.
- Insulating materials such as glass, rubber, or plastic are also called dielectrics, meaning they can store charges.
- Dielectric materials are used in components like capacitors which must store electric charges.

SEMI-CONDUCTORS

- Have 4 valence electrons
- Materials which are neither conductors nor insulators
- Common semi conductor materials are carbon, germanium and silicone.
- Used in components like transistors


MEASURING VOLTAGE

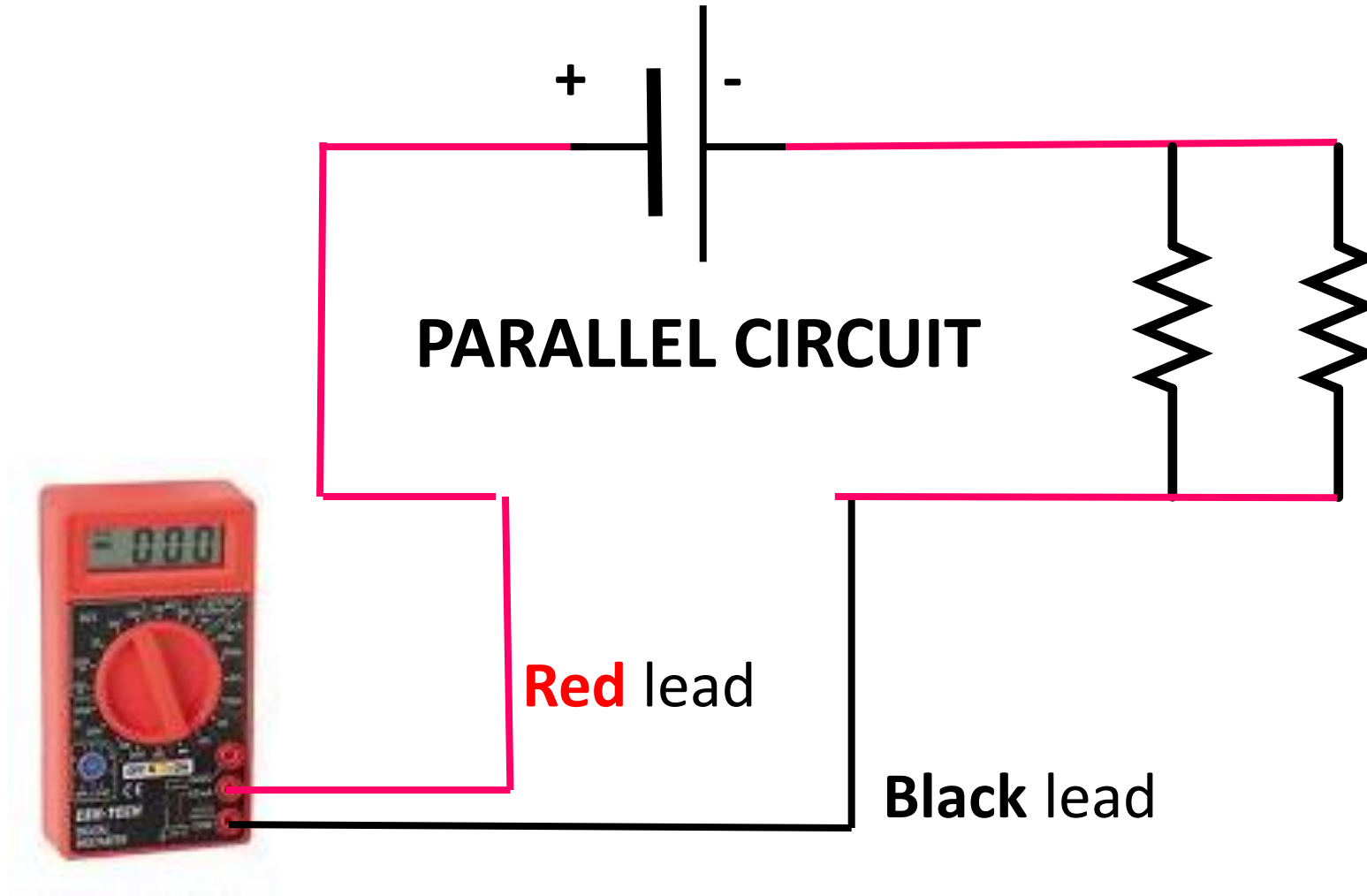

This is how we measure volts in a circuit

MEASURING CURRENT

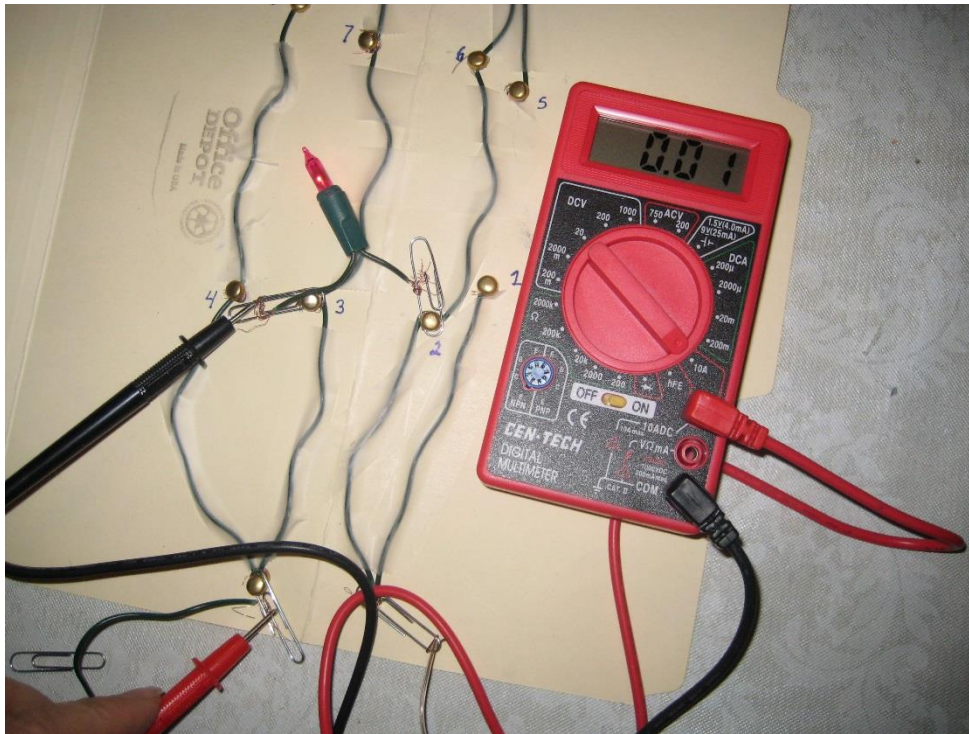
Electric current is measured in **amps** (A) using an ammeter connected in series in the circuit.




SERIES CIRCUITS




Connect one bulb to the battery.

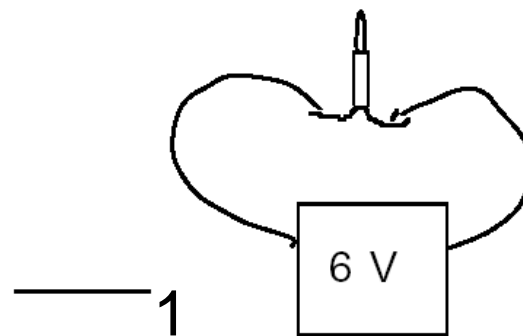

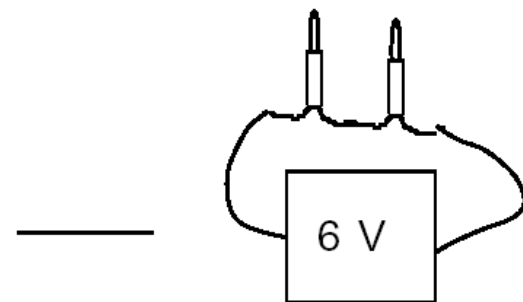Connect 2 bulbs and the battery to form a series circuit.



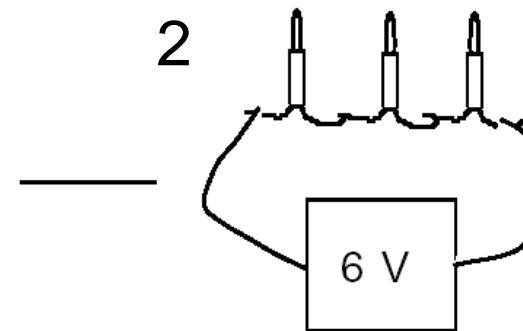Connect 3 bulbs and the battery to form a series circuit.




Mark from 1 to 3 each diagram according to brightness. (3 - brightest)


Since the brightness of the bulbs indicates how much current

measuring voltage

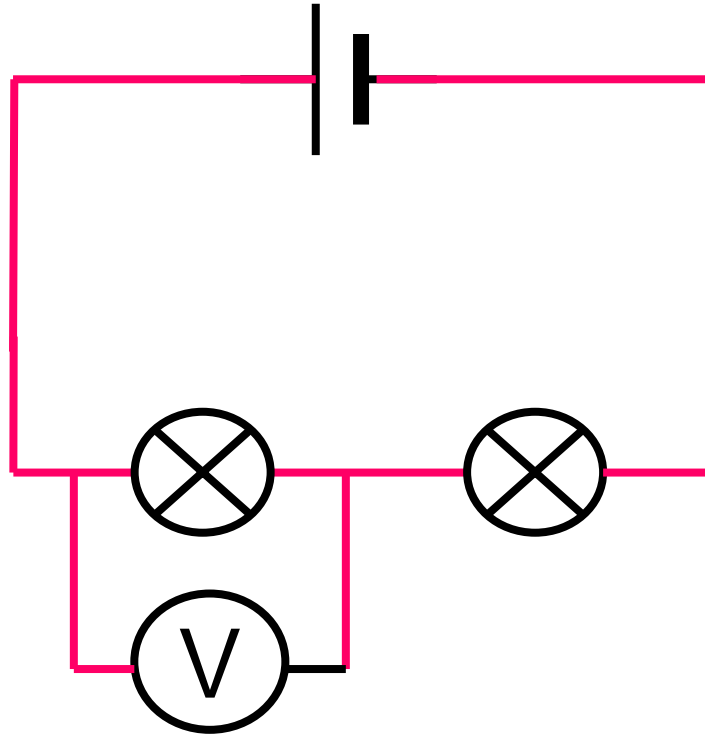This is how we draw a voltmeter in a circuit.




SERIES CIRCUIT

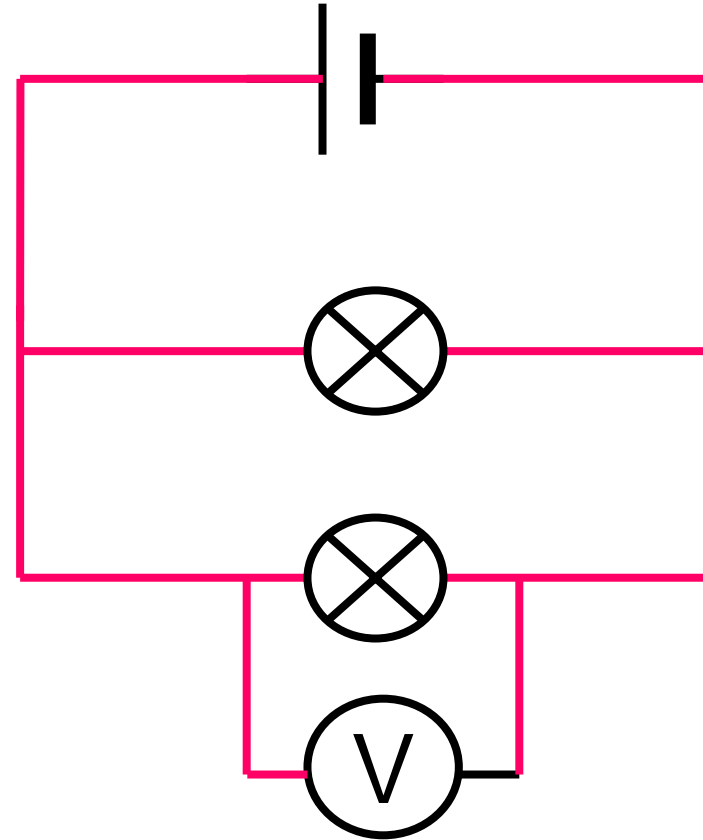

PARALLEL CIRCUIT


MEASURING VOLTAGE

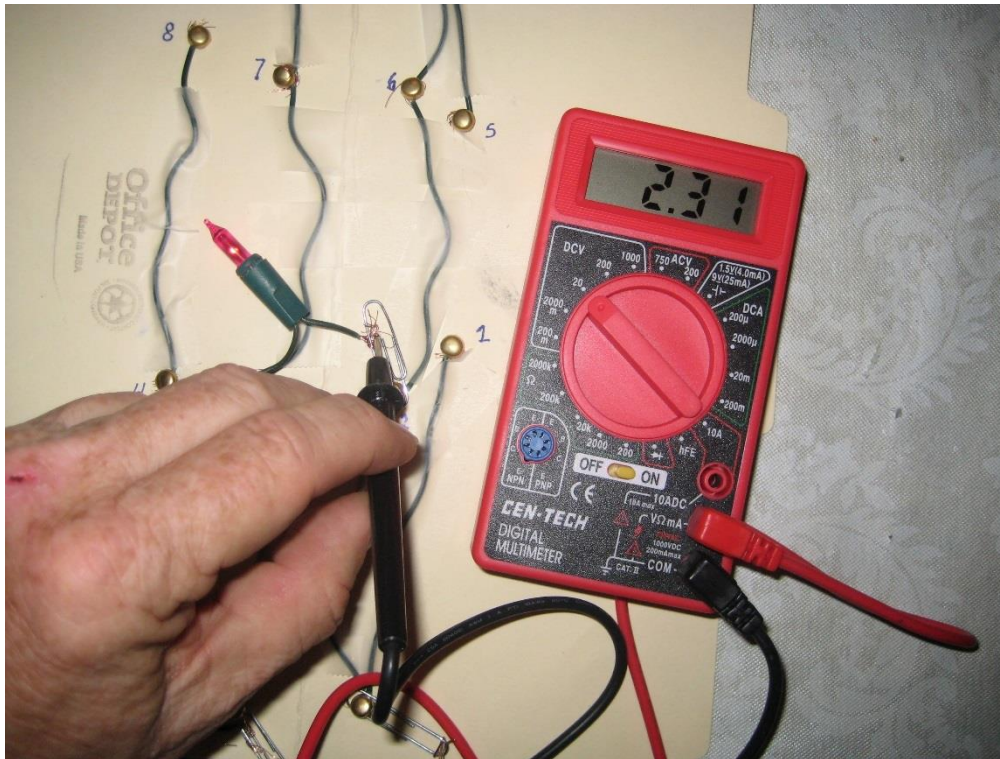The 'electrical push' which the cell gives to the current is called the **voltage**. It is measured in **volts** (V) on a **voltmeter**




MEASURING CURRENT

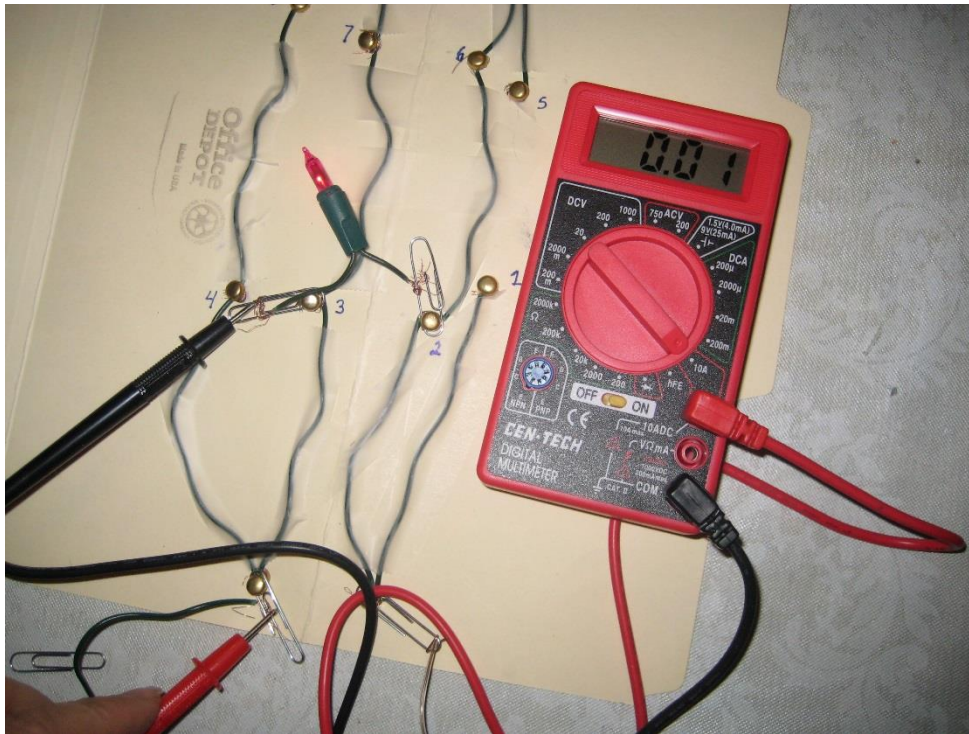Electric current is measured in **amps** (A) using an ammeter connected in series in the circuit.




measuring current

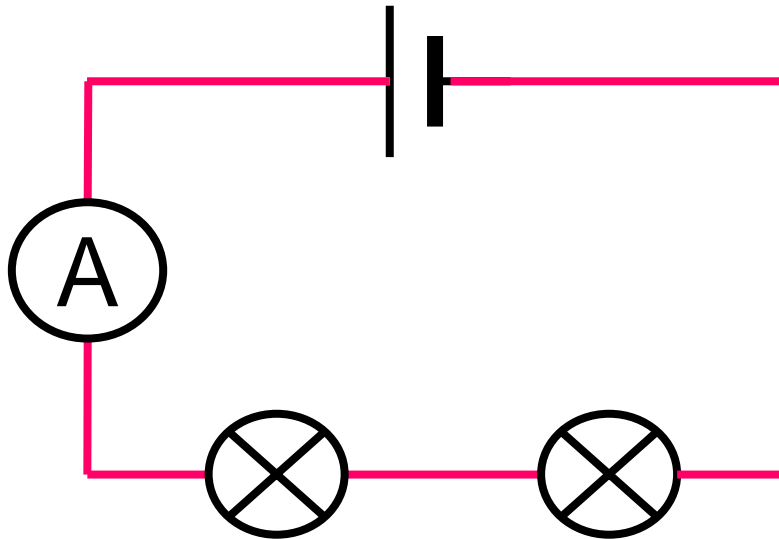This is how we draw an ammeter in a circuit.



SERIES CIRCUIT

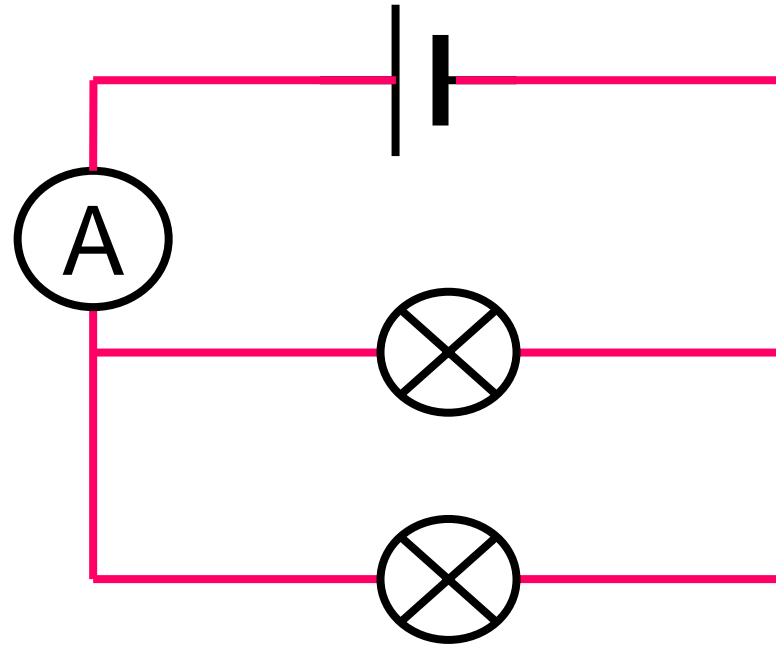

PARALLEL CIRCUIT