



STEAM CLOWN™ PRODUCTIONS

CAPACITORS



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™



STEAM CLOWN™ PRODUCTIONS

Attribution-NonCommercial-ShareAlike
3.0 Unported (CC BY-NC-SA 3.0)

SEE APPENDIX A, FOR LICENSING & ATTRIBUTION INFORMATION

by-nc-sa-3.0

<https://creativecommons.org/licenses/by-nc-sa/3.0/>

<https://creativecommons.org/faq/#what-does-some-rights-reserved-mean>



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™


WHAT YOU WILL KNOW...

- Prior Knowledge
 - How a Bread Board Works
 - How to Use a DMM to measure voltage
- What You Will Be Able To Do Or Know
 - Calculate for Time in and Resistor/Capacitor network
 - Build a R/C circuit and measure the time to charge/discharge
 - Be able to describe how an R/C circuit works



CAPACITORS - INTRODUCTION

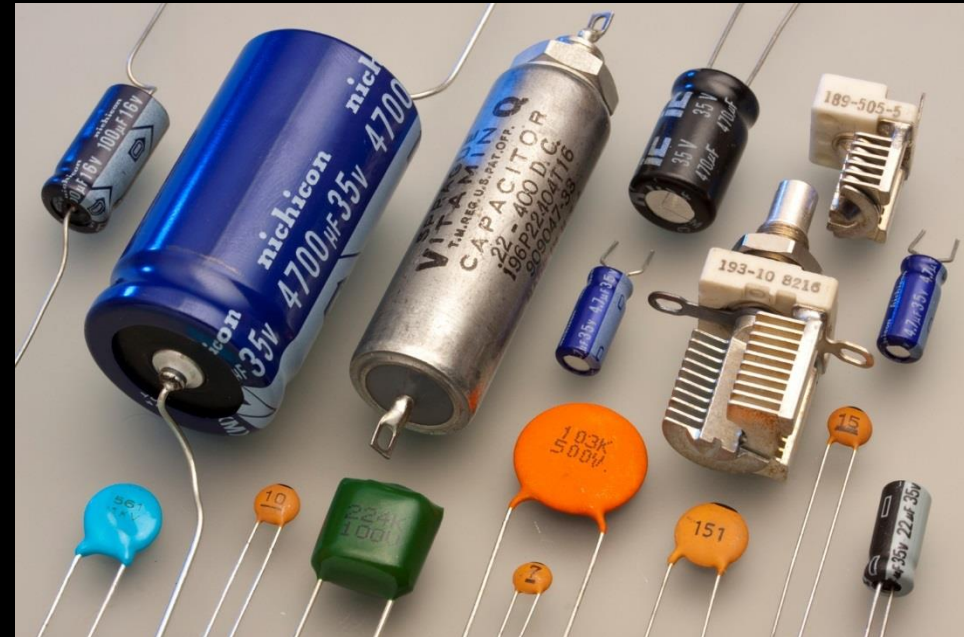- A capacitor is a two-terminal, electrical component that can store and hold energy
- It is a passive components
 - Fundamental, like Resistors & Inductors
 - Almost all circuits have a capacitor in it.





STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

LIKE A LITTLE BATTERY...

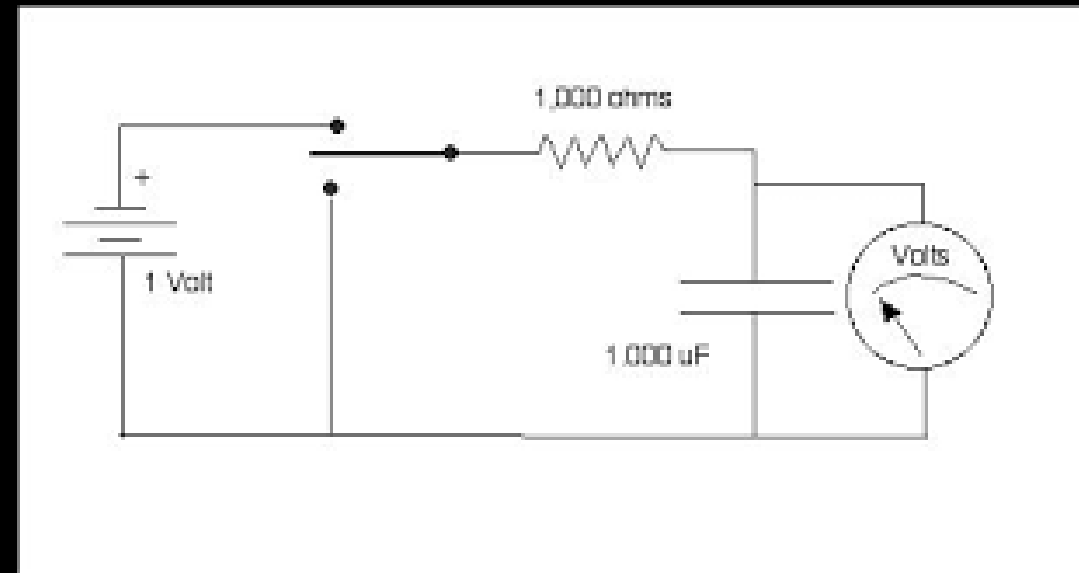- Capacitors have the ability to **store energy**
 - Like a fully charged electric battery
- Common applications include:
 - Local energy storage
 - Voltage spike suppression
 - Complex signal filtering.



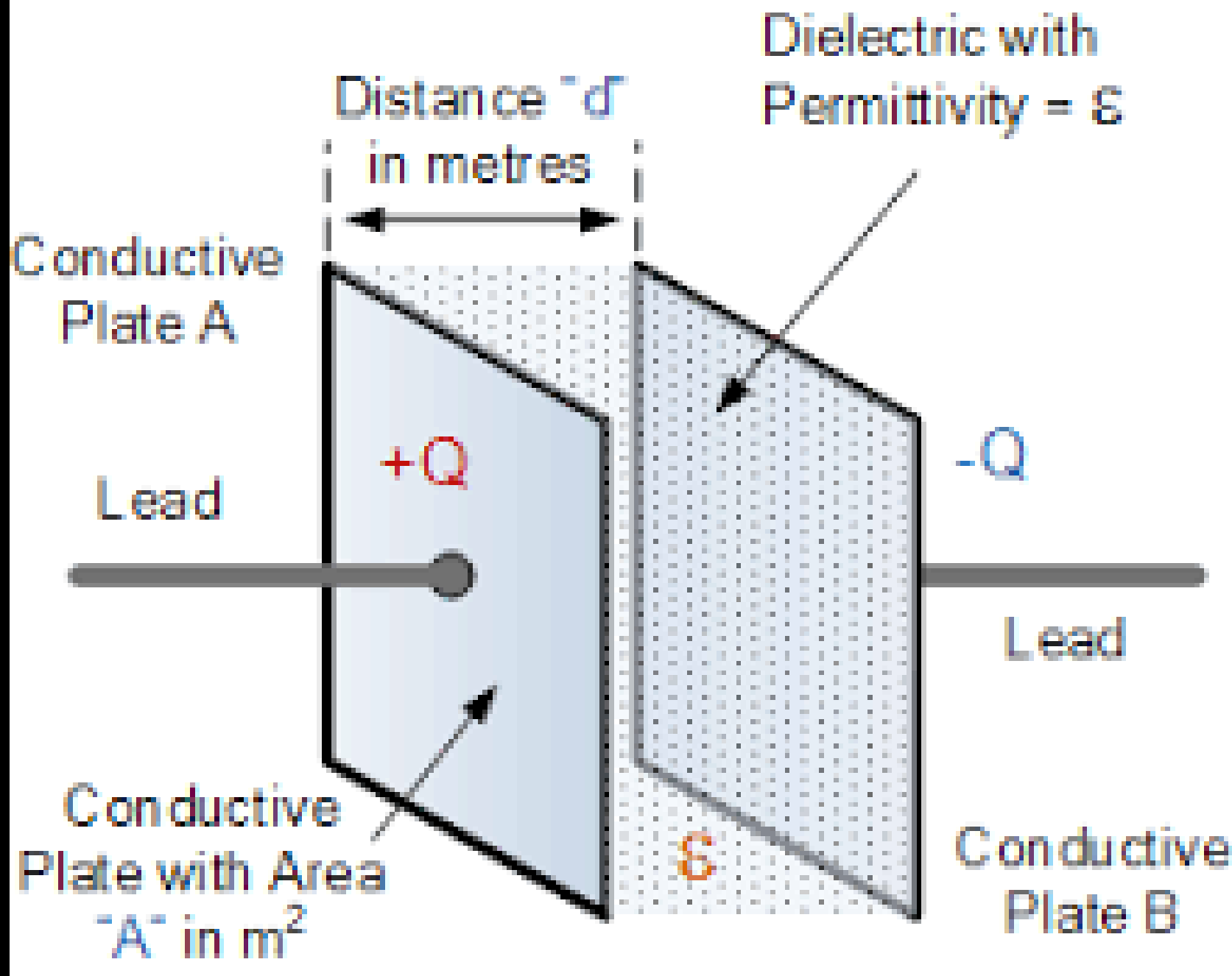

- <https://electronics.stackexchange.com/questions/18301/how-does-a-capacitor-block-dc>

- <https://learn.sparkfun.com/tutorials/capacitors>

CAPACITANCE - FARADS

- The unit of capacitance is F (Farads)
- A capacitor has a capacitance of 1 farad if a charge of 1 coulomb increases the potential difference between its plates by 1 volt
- The farad is coulomb/volt
- The farad is much too big for most practical purposes; microfarads, nanofarads, and picofarads are usually used.



READING CAPACITORS

- $1\mu\text{F} = 1^{-6}$ Farads
- $1\mu\text{F} = .000001$ Farads
- $1000000\mu\text{F} = 1$ Farads

Microfarad [μF]	Farad [F]
0.01 μF	1.0E-8 F
0.1 μF	1.0E-7 F
1 μF	1.0E-6 F
2 μF	2.0E-6 F
3 μF	3.0E-6 F
5 μF	5.0E-6 F
10 μF	1.0E-5 F
20 μF	2.0E-5 F
50 μF	5.0E-5 F
100 μF	0.0001 F
1000 μF	0.001 F

TEAM CLOWN™



& Squeaky Hinge
PRODUCTIONS

© Copyright 2017 STEAM Clown™

TIME CONSTANT $T=RC$

- $t = RC$
- Where R is Ohms and C is FARADS

μF	Farads
100 μF	.0001F
10 μF	.00001F
1 μF	.000001F
.1 μF	.0000001F
.01 μF	.00000001F
.001 μF	.000000001F

- You need to convert any μF to F... so just move the decimal point to the left 6 places



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

TIME CONSTANT $T=RC$

- $t = RC$
- Where R is Ohms and C is FARADS

$$t=RC$$

$$t = 100\mu\text{F} \times 100\text{K}\Omega$$

$$t = .0001\text{F} \times 100\text{K}\Omega$$

$$t = 10 \text{ seconds}$$

μF	Farads
100 μF	.0001F
10 μF	.00001F
1 μF	.000001F
.1 μF	.0000001F
.01 μF	.00000001F
.001 μF	.000000001F




STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

THE TIME CONSTANT...

- is the time taken (in seconds) by the capacitor C that is fed from a resistor R to charge to a certain level.
- The capacitor will charge to 63% of the final voltage in one time constant
- 85% in two time constants
- 100% in five time constants.

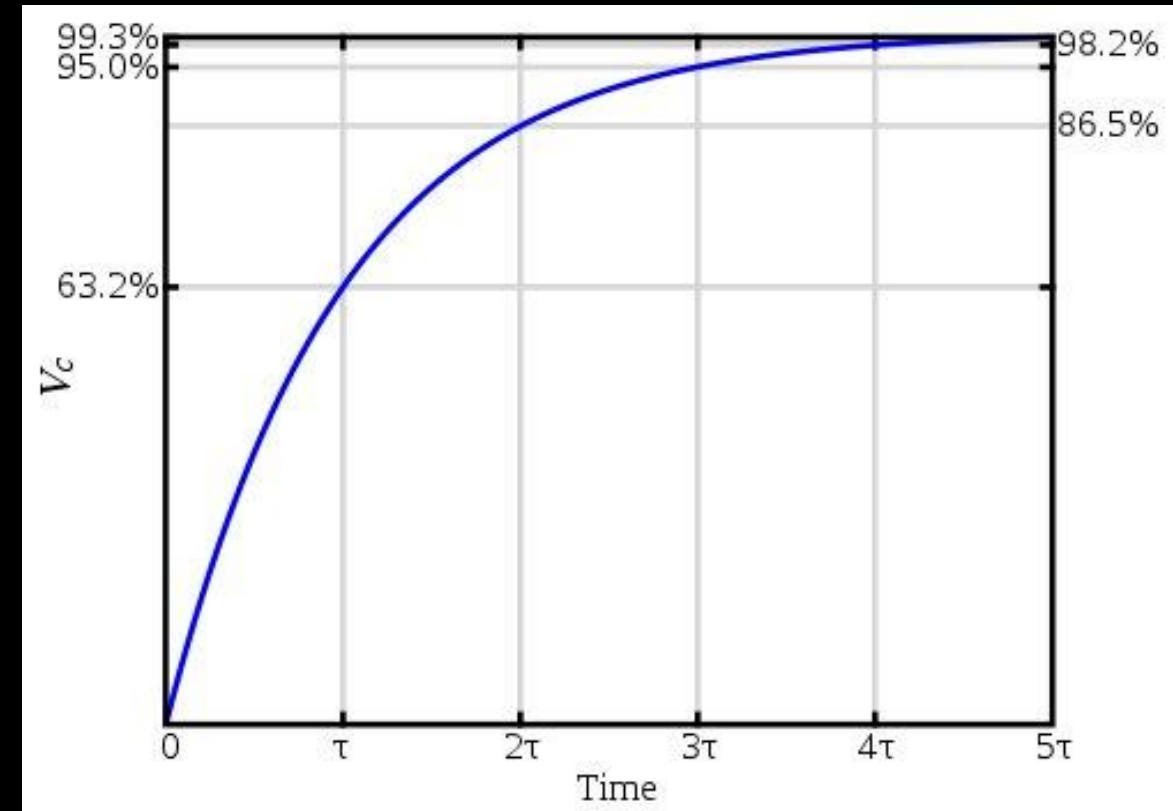If you graphed the % charge against time constant, the result is exponential. That is:



ALGEBRA... SOLVE FOR C AND R

$$t = RC$$

$$t = RC$$

$$\frac{t}{R} = \frac{RC}{R}$$

$$\frac{t}{C} = \frac{RC}{C}$$

$$\frac{t}{R} = C$$

$$\frac{t}{C} = R$$


$$C = \frac{t}{R}$$

$$R = \frac{t}{C}$$




CHECK YOUR MATH TO THE REAL WORLD...

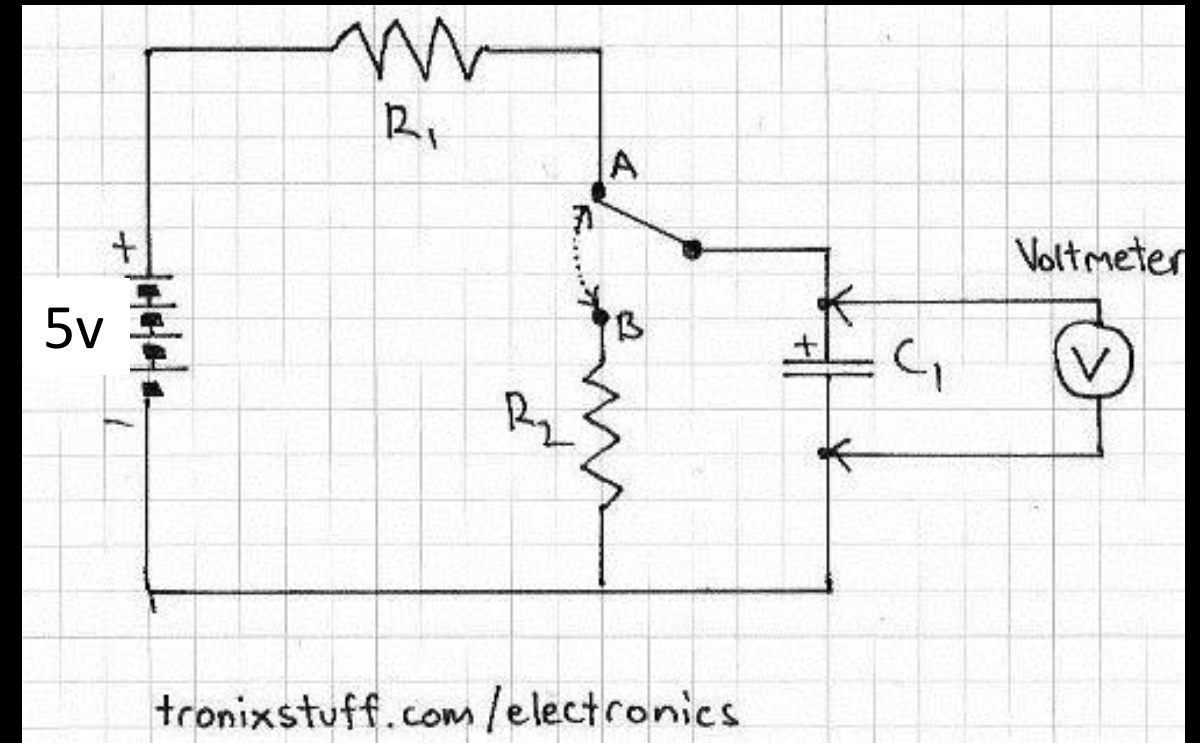- Pick a C_1 and a Time Constant for R_1 and another Time Constant for R_2
- Calculate R_1 and R_2
- Build it, and measure your Time Constants




CHECK YOUR MATH TO THE REAL WORLD...

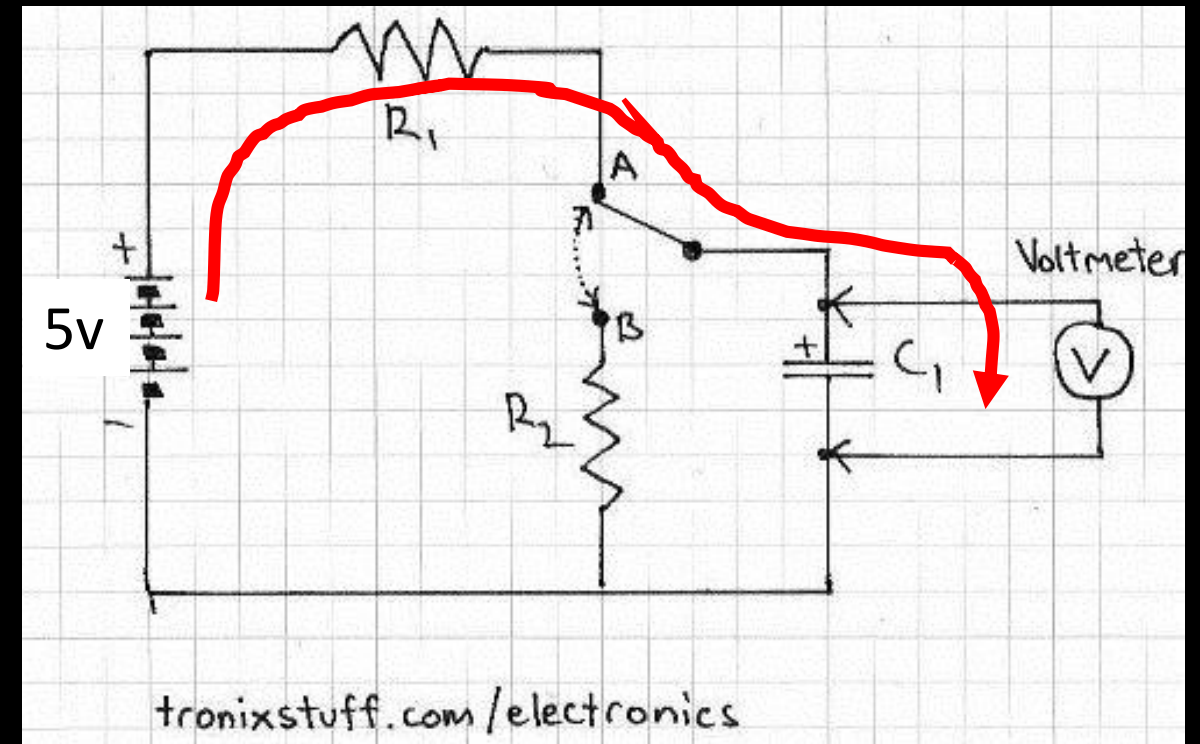- Pick a C_1 - could be the same $100\mu\text{F}$ cap
- Pick a Time Constant for R_1
- Calculate $R_1 = t/C$
- Build it, and measure your Time Constants



CHECK YOUR MATH TO THE REAL WORLD...

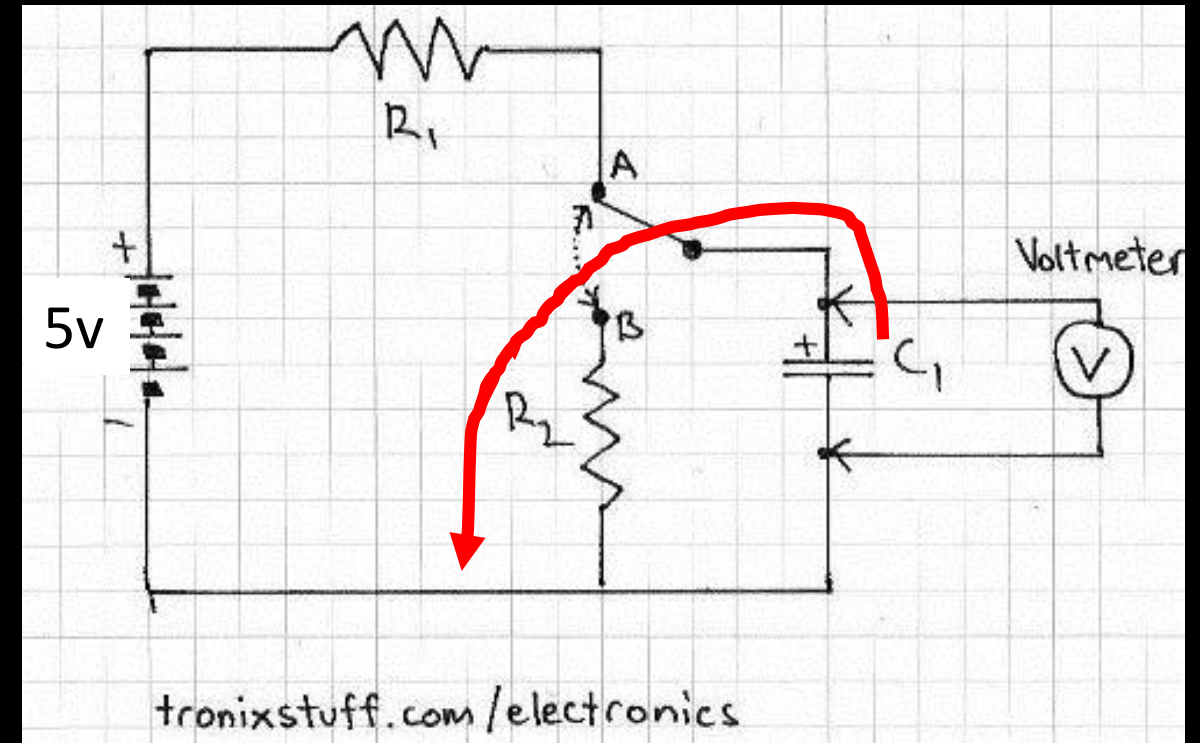- Pick a C_1 - could be the same $100\mu\text{F}$ cap
- Pick a Time Constant for R_2
- Calculate $R_2 = t/C$
- Build it, and measure your Time Constants





STEAM CLOWN™ PRODUCTIONS

APPENDIX



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

APPENDIX A: LICENSE & ATTRIBUTION

- This interpretation is primarily the Intellectual Property of Jim Burnham, Top STEAM Clown, at STEAMClown.org
- This presentation and content is distributed under the Creative Commons License CC-by-nc-sa-3.0
- My best attempt to properly attribute, or reference any other sources or work I have used are listed in Appendix B



Under the following terms:



Attribution — You must give [appropriate credit](#), provide a link to the license, and [indicate if changes were made](#). You may do so in any reasonable manner, but not in any way that suggests the licensor endorses you or your use.



NonCommercial — You may not use the material for [commercial purposes](#).



ShareAlike — If you remix, transform, or build upon the material, you must distribute your contributions under the [same license](#) as the original.

No additional restrictions — You may not apply legal terms or [technological measures](#) that legally restrict others from doing anything the license permits.



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

APPENDIX B: ATTRIBUTION FOR SOURCES USED

- SparkFun – Capacitors

- <https://learn.sparkfun.com/tutorials/capacitors>

- Tronixstuff

- <https://tronixstuff.com/2010/06/11/education-the-rc-circuit-2/>



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™



STEAM CLOWN™ PRODUCTIONS


REFERENCE SLIDES



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

• SS

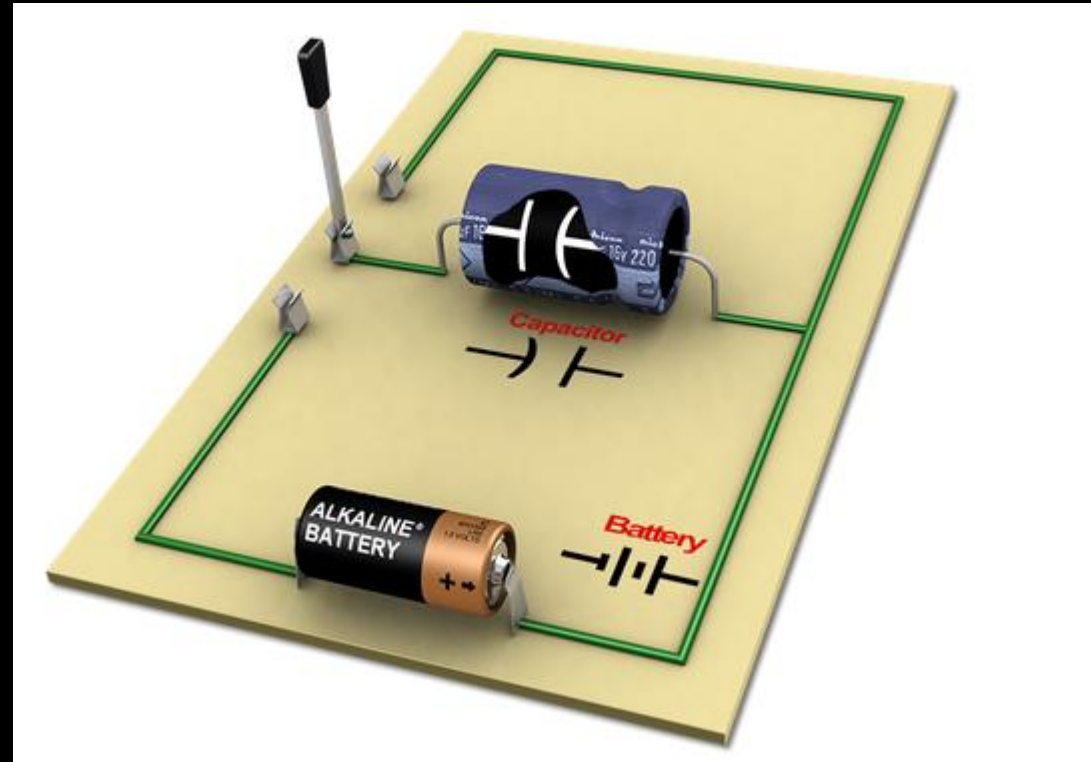


<http://micro.magnet.fsu.edu/electromag/java/capacitor/index.html>



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

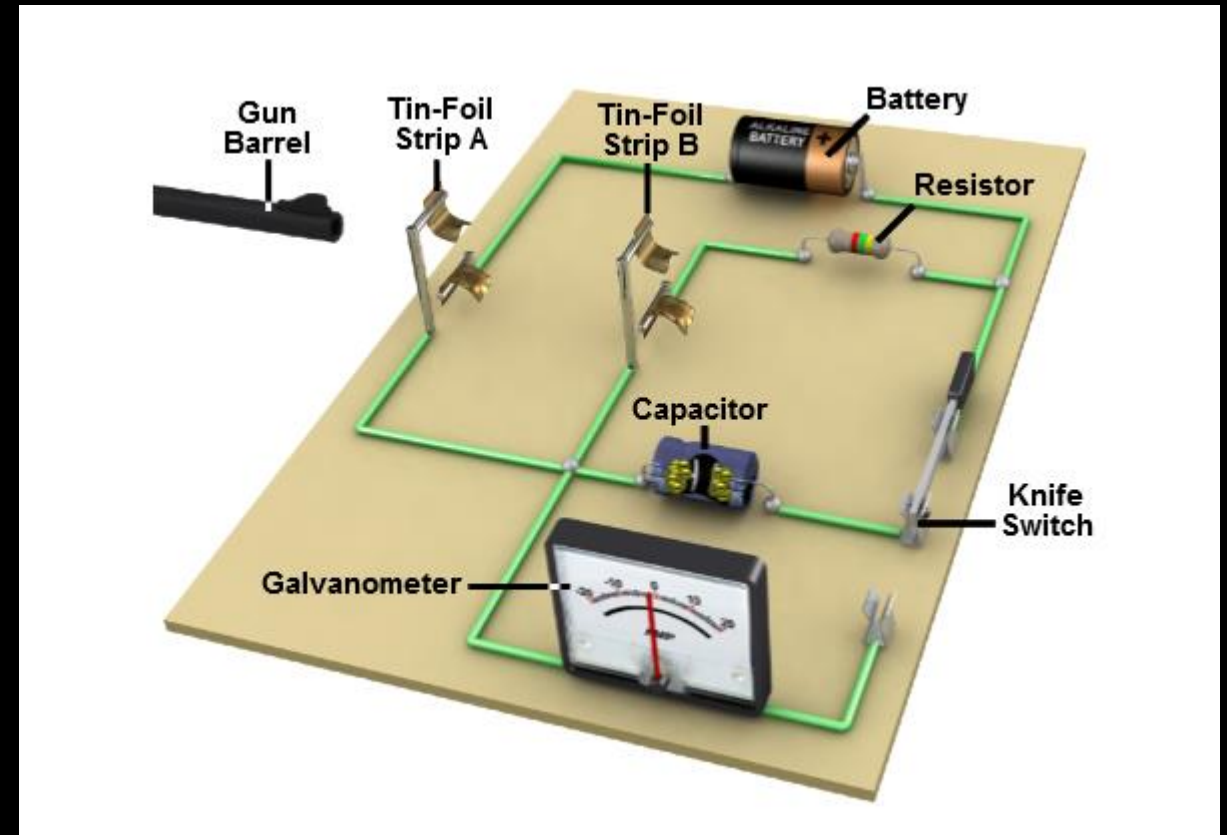

<https://nationalmaglab.org/education/magnet-academy/watch-play/interactive/bullet-speed>



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™