



**STEAM CLOWN™ PRODUCTIONS**

# LOGIC GATES - INTRODUCTION

# OVERVIEW & INTRODUCTION

- Digital Design underpins the creation of the myriad of imaginative digital devices that surround us...
  - Computers
  - Calculators
  - Phones
  - Digital watches
  - Microwave ovens
  - Robots...

Really...  
Everything



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# DIGITAL DESIGN

- Organizing an arrays of simple switches into a discrete system that performs transformations on two-level (Binary) information in a meaningful and predictable way



# STEAM CLOWN™ PRODUCTIONS

Attribution-NonCommercial-ShareAlike  
3.0 Unported (CC BY-NC-SA 3.0)

## SEE APPENDIX A, FOR LICENSING & ATTRIBUTION INFORMATION

by-nc-sa-3.0

<https://creativecommons.org/licenses/by-nc-sa/3.0/>

<https://creativecommons.org/faq/#what-does-some-rights-reserved-mean>



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# WHAT YOU WILL KNOW...

- Prior Knowledge
  - Binary Numbers
    - How to count in binary
    - How to Add in Binary
    - How to Multiply in Binary
- What You Will Know & Be Able To Do
  - Explain the difference between AND, OR, NOT logic gates
  - Read and fill out a Truth Table
  - Convert a Logical Expression in to Gate Diagram
  - Convert a Logical Expression in to a Truth Table

# NEW WORDS...

- Binary
- Logical Expression
- Truth Table

# REVIEW BINARY NUMBERS

- Take 10 minutes and review binary numbers
  - Binary Number Systems
  - Binary Digits



# HOW TO CONVERT FROM BINARY OR DECIMAL

Computer Humor

- Binary is as easy as 01, 10, 11


Convert the Following Binary Numbers:

$$0011 = ? \quad 1 \times 2 + 1 \times 1 = 3$$

$$1011 = ? \quad 1 \times 8 + 0 \times 4 + 1 \times 2 + 1 \times 1 = 11$$

$$10101 = ? \quad 1 \times 16 + 0 \times 8 + 1 \times 4 + 0 \times 2 + 1 \times 1 = 21$$
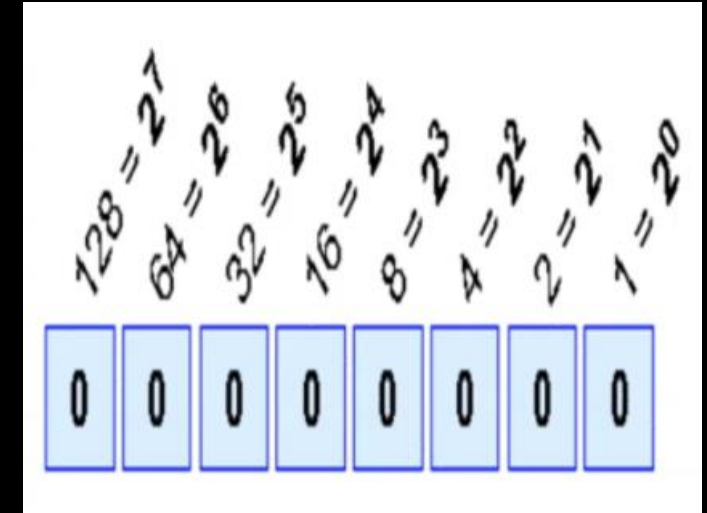
$$110011 = ? \quad 1 \times 32 + 1 \times 16 + 0 \times 8 + 0 \times 4 + 1 \times 2 + 1 \times 1 = 51$$



Place Values



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™



# BINARY QUIZ

- [https://docs.google.com/forms/d/e/1FAIpQLSc82cMmtQFs0CJ7IW1a\\_sVz7N6eGZl64MbAlJmrdc6ZndfYPw/viewform?usp=sf link](https://docs.google.com/forms/d/e/1FAIpQLSc82cMmtQFs0CJ7IW1a_sVz7N6eGZl64MbAlJmrdc6ZndfYPw/viewform?usp=sf_link)



**STEAM CLOWN™ PRODUCTIONS**

# **ADDING AND MULTIPLYING BINARY NUMBERS**



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# ADDING BINARY NUMBERS

$$\begin{array}{r} 110 \\ + 101 \\ \hline 1011 \end{array}$$

Since  $1 + 1 = 10$

Since  $1 + 0 = 1$

Since  $0 + 1 = 1$

Rule 1  $\rightarrow 0 + 0 = 0$

Rule 2  $\rightarrow 0 + 1 = 1$

Rule 3  $\rightarrow 1 + 0 = 1$

Rule 4  $\rightarrow 1 + 1 = 10 \leftarrow$  Surprise!

} Just like  
decimal  
addition



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# MULTIPLYING BINARY NUMBERS

$$\begin{array}{r} 110 \\ * 101 \\ \hline 110 \\ 0000 \\ 11000 \\ \hline 11110 \end{array}$$

Rule 1  $\rightarrow 0 * 0 = 0$

Rule 2  $\rightarrow 0 * 1 = 0$

Rule 3  $\rightarrow 1 * 0 = 0$

Rule 4  $\rightarrow 1 * 1 = 1$



Just like  
decimal  
multiplication



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# ADDING AND MULTIPLYING IN BINARY

- Adding Binary Numbers
  - [Adding in binary | Applying mathematical reasoning](#)
- Multiplying Binary Numbers
  - [Multiplying in binary | Applying mathematical reasoning](#)



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™




**STEAM CLOWN™ PRODUCTIONS**

# INTRO TO LOGIC GATES

# BINARY LOGIC

- Deals with binary variables that take 2 discrete values (0 and 1), and with logic operations
- Three basic logic operations:
  - AND, OR, NOT
- Binary/logic variables are typically represented as letters: A, B, C, ..., X, Y, Z

# BASIC LOGIC OPERATORS

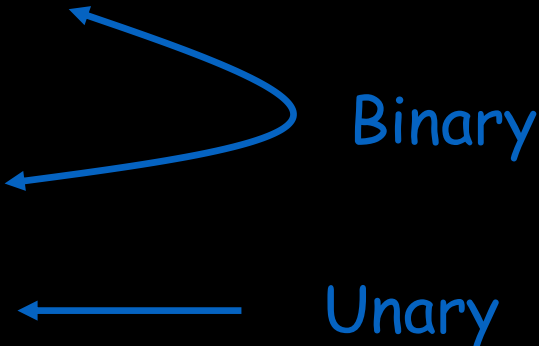- AND
  - OR
  - NOT
- Binary
- Unary
- 

•  $F(a,b) = a \cdot b$ ,  $F$  is 1 if and only if  $a=b=1$

•  $G(a,b) = a + b$ ,  $G$  is 1 if either  $a=1$  or  $b=1$

•  $H(a) = a'$ ,  $H$  is 1 if  $a=0$



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™



# BINARY LOGIC FUNCTION

$F(\text{var}) = \text{expression}$



This is a set of Binary variables  
Defines the set of "Inputs"

Ex:  $F(a,b) = (a' \cdot b) + b'$



$F(a,b,c) = a \cdot ((b+c') + (b'+c))$

Operators ( +, •, ' )

Variables

Constants ( 0, 1 )

Groupings (parenthesis)

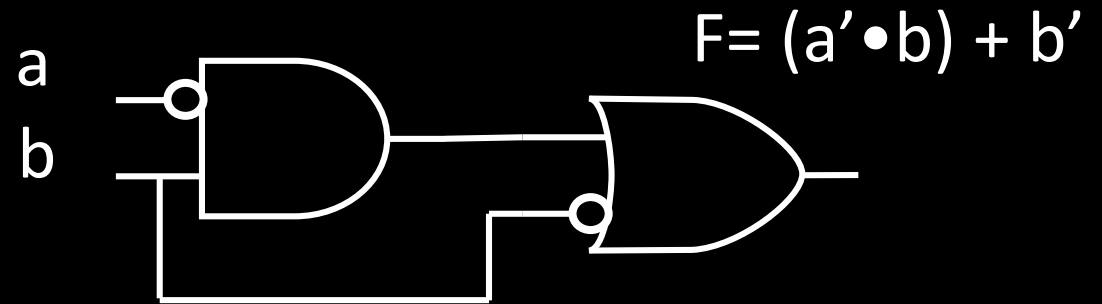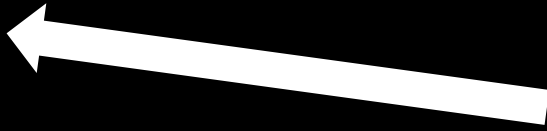

**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# BASIC AND & OR LOGIC OPERATORS


1-bit logic AND resembles binary multiplication:

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

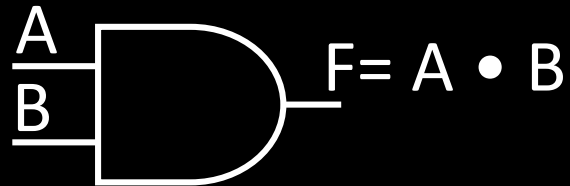


1-bit logic OR resembles binary addition, except for one operation:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1 (\neq 10_2)$$

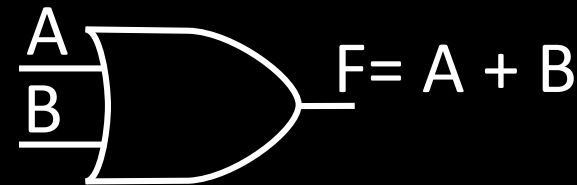

**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™




# COMBINATIONAL LOGIC GATES

- Outputs depend directly on their inputs
- Outputs are generated asynchronously and instantaneous\*
- Do not require a clock or other synchronous signals
- Let's call them "Logic Gates"


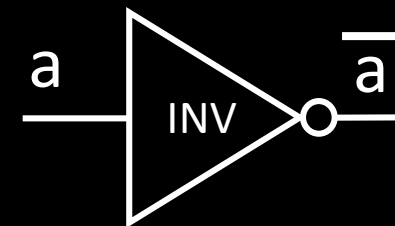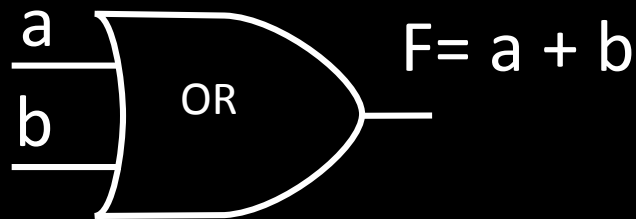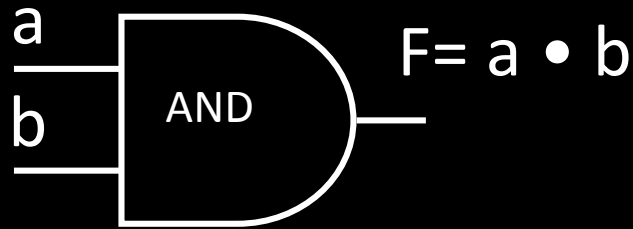
# LOGIC GATES

- Logic gates are abstractions of electronic circuit components that operate on one or more input signals to produce an output signal




# AND GATE

- This AND gate has two inputs and an output
- Output is zero unless both Inputs are 1's

The AND operation is mathematically defined as the product of two Boolean values

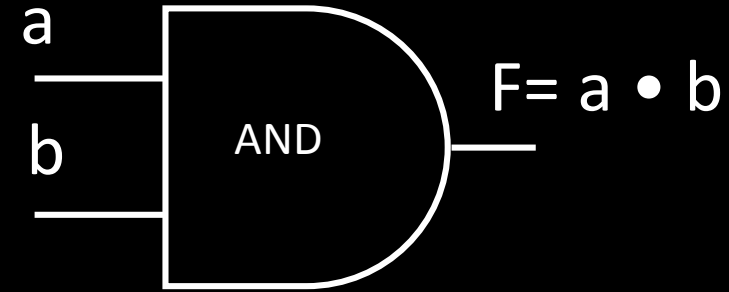**Truth table:** tabular form that uniquely represents the relationship between the input variables of a function and its output



2-Input AND

A	B	F=A•B
0	0	0
0	1	0
1	0	0
1	1	1




**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™
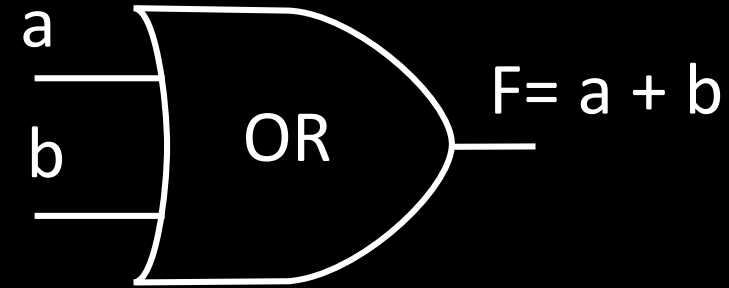
# OR GATE

- This OR gate has two inputs and an output
- Output is 1 if any of the Inputs are 1's



The OR operation is mathematically defined as the summation of two Boolean values

**Truth table:** tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input OR

A	B	F=A+B
0	0	0
0	1	1
1	0	1
1	1	1




**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™
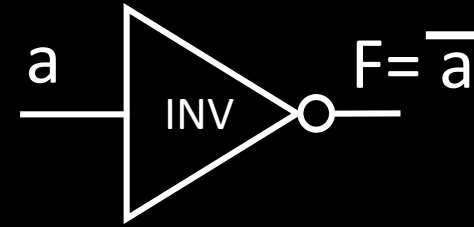
# NOT (INVERTER) GATE

- This NOT gate has one input and one output
- This is an “inverter” function
- Output is 1 if the Input is 0, and 0 if the Input is 1



(Inverter)  
NOT

a	F = $\bar{a}$
0	1
1	0

**Truth table:** tabular form that uniquely represents the relationship between the input variables of a function and its output

# TRUTH TABLES FOR LOGIC OPERATORS

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input AND

A	B	$F=A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

2-Input OR

A	B	$F=A+B$
0	0	0
0	1	1
1	0	1
1	1	1

NOT

A	$F=A'$
0	1
1	0





# TRUTH TABLES - CHECK FOR UNDERSTANDING

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input AND

A	B	$F=A \cdot B$
0	0	
0	1	
1	0	
1	1	

2-Input OR

A	B	$F=A+B$
0	0	
0	1	
1	0	
1	1	

NOT

A	$F=A'$
0	
1	



# TRUTH TABLES - CHECK FOR UNDERSTANDING

Q: Let a function  $F()$  depend on  $n$  variables.

How many rows are there in the truth table of  $F(a,b) = (a+b)$ ?

What about  $F(a,b,c) = (a+b+c)$ ?

What about  $F(a,b,c,d) = (a+b+c+d)$ ?

A	B	F=A+B
0	0	0
0	1	1
1	0	1
1	1	1

A:  $2^n$  rows, since there are  $2^n$  possible binary patterns / combinations for the  $n$  variables



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™



# STEAM CLOWN™ PRODUCTIONS

**LAB TIME -**

**[HTTPS://LOGIC.LY/DEMO/](https://logic.ly/demo/)**






**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**  
© Copyright 2017 STEAM Clown™

# CHECK OUT THIS LOGIC LINK

- Learning about Logic Gates and Circuits
  - <https://logic.ly/lessons/>

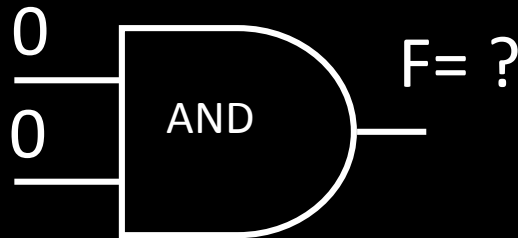
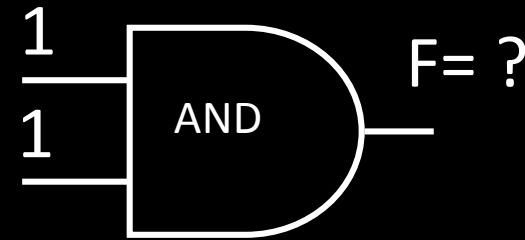
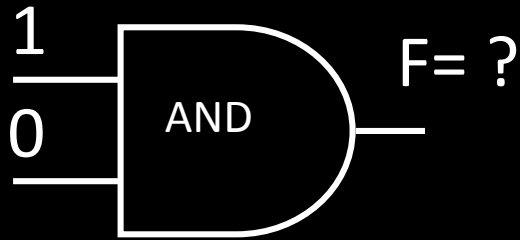
# LOGIC GATES - CHECK FOR UNDERSTANDING

- What are the outputs for each of these gates with the specified inputs values?


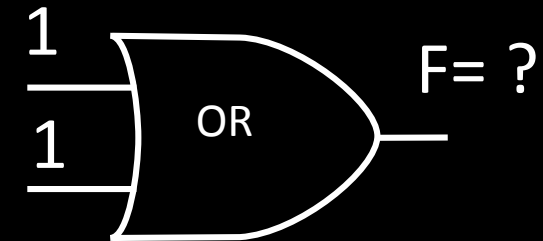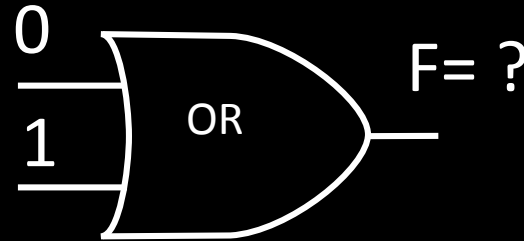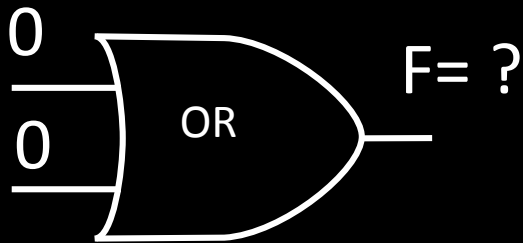
# LOGIC GATES - CHECK FOR UNDERSTANDING

- What are the outputs for each of these gates with the specified inputs values?





**STEAM CLOWN™ PRODUCTIONS**



# XOR, NAND, NOR GATES

# AND GATE + INVERTER

- This NAND gate has two inputs and an output
- Output is 1 unless both Inputs are 1's, then it's 0

2-Input NAND

A	B	F=A•B
0	0	1
0	1	1
1	0	1
1	1	0

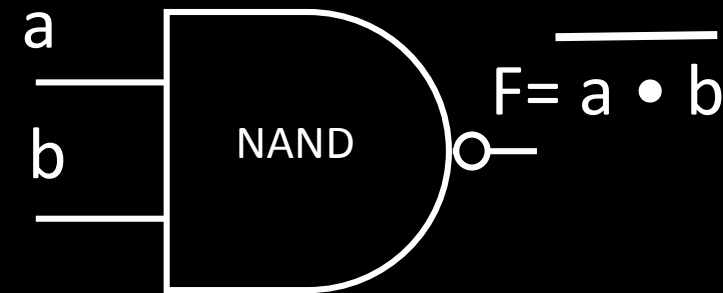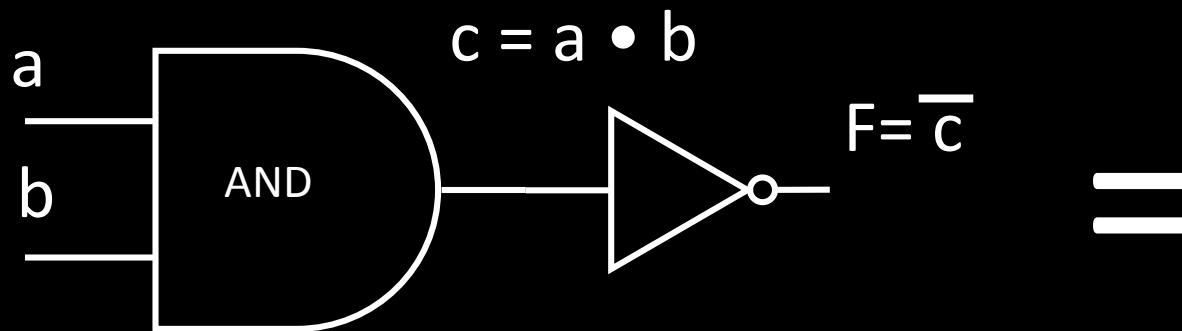




# NAND GATE

- This NAND gate has two inputs and an output
- Output is 1 unless both Inputs are 1's, then it's 0

The NAND operation is mathematically defined as the product of two Boolean values

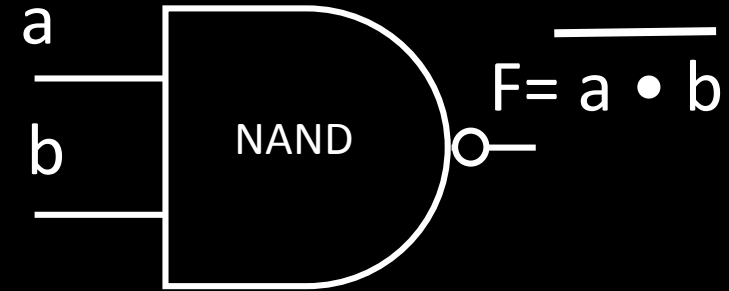**Truth table:** tabular form that uniquely represents the relationship between the input variables of a function and its output



2-Input NAND



A	B	$F = \overline{A \cdot B}$
0	0	1
0	1	1
1	0	1
1	1	0



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# NOR GATE

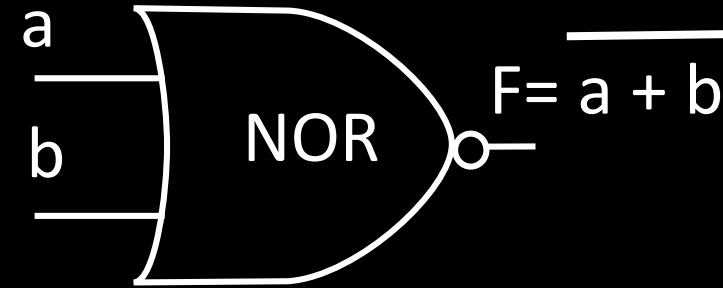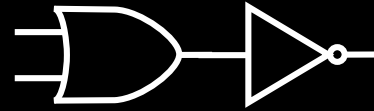

- This NOR gate has two inputs and an output
- Output is 0 if any of the Inputs are 1's

The NOR operation is mathematically defined as the summation of two Boolean values

**Truth table:** tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input NOR

A	B	$F = \overline{A+B}$
0	0	1
0	1	0
1	0	0
1	1	0




**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™
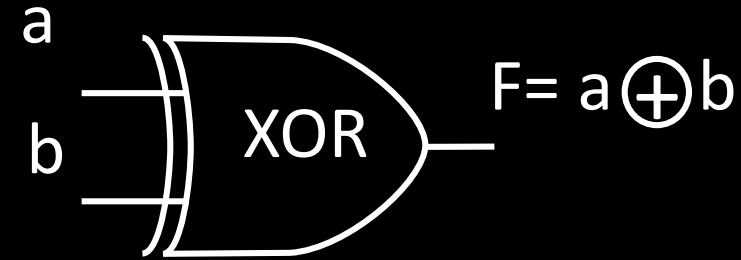
# XOR GATE

- This XOR gate has two inputs and an output
- Output is 1 if the Inputs are different



The XOR operation is mathematically defined as the summation of two Boolean values if they are different

2-Input XOR

A	B	F=A ⊕ B
0	0	0
0	1	1
1	0	1
1	1	0

**Truth table:** tabular form that uniquely represents the relationship between the input variables of a function and its output



# STEAM CLOWN™ PRODUCTIONS

# REFERENCE SLIDES



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™



# STEAM CLOWN™ PRODUCTIONS

# APPENDIX



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# APPENDIX A: LICENSE & ATTRIBUTION

- This interpretation is primarily the Intellectual Property of Jim Burnham, Top STEAM Clown, at STEAMClown.org
- This presentation and content is distributed under the Creative Commons License CC-by-nc-sa-3.0
- My best attempt to properly attribute, or reference any other sources or work I have used are listed in Appendix B



## Under the following terms:



**Attribution** — You must give [appropriate credit](#), provide a link to the license, and [indicate if changes were made](#). You may do so in any reasonable manner, but not in any way that suggests the licensor endorses you or your use.



**NonCommercial** — You may not use the material for [commercial purposes](#).



**ShareAlike** — If you remix, transform, or build upon the material, you must distribute your contributions under the [same license](#) as the original.

**No additional restrictions** — You may not apply legal terms or [technological measures](#) that legally restrict others from doing anything the license permits.



**STEAM CLOWN™**  
& **Squeaky Hinge**  
**PRODUCTIONS**

© Copyright 2017 STEAM Clown™

# APPENDIX B: ATTRIBUTION FOR SOURCES USED

- Power Point [Logic Gates Symbols](#) – Oliver Mannay
- Slide Share [Logic Gates](#)
- PPT from Michigan Tech [EE 4271](#)