

STEAM ClownTM Productions

Bread Boards & LEDs



Overview & Introduction

- This Lecture and Lab is an introduction to Breadboards, Electrical Circuit basics and LEDs
 - You will learn how a breadboard works
 - You will build an LED circuit and get it to light up
- You will use a Breadboard, Resistor, Switch and LED
- You will show me a working LED circuit and be able to explain how and why it is working





STEAM ClownTM Productions







Attribution-NonCommercial-ShareAlike 4.0 International (CC BY-NC-SA 4.0)

See Appendix A,B,C, for Licensing & Attribution Information CC BY-NC-SA 4.0

https://creativecommons.org/licenses/by-nc-sa/4.0/

https://creativecommons.org/licenses/by-nc-sa/4.0/legalcode

GNU Public License


Any included Programming Code Is licensed under GNU General Public License v3.0


EUPL (European Union Public Licence) Code and Content is also licensed under EUPL 1.2 or later



Resources & Materials Needed

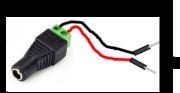- (1) Breadboard
- (1) 5 volt Wall Power Supply
- (1) Power Adaptor
- (3-5) Jumper Wire (Male-Male)
- (1) LED
- (1) 330Ω Resistor
- (1) Push Button Switch



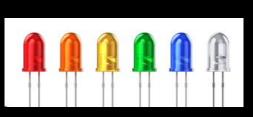







What You WIII Know...

Prior Knowledge

I'm not expecting anyone to have any Electronics experience...
Some of you may, but it's not expected

What You Will Know & Be Able To Do

- Understand the theory of how a breadboard works
- Build an LED, resistor, and switch circuit on a breadboard
- Be able to describe a open and closed series circuit works



New Words...

- Breadboard
- LED
- Resistor
- Circuit
- Series Circuit






STEAM ClownTM Productions


How A Breadboard Works





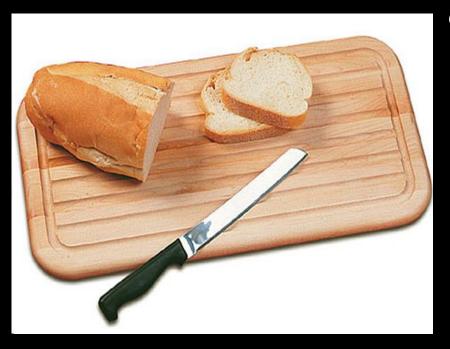


• It is not This...

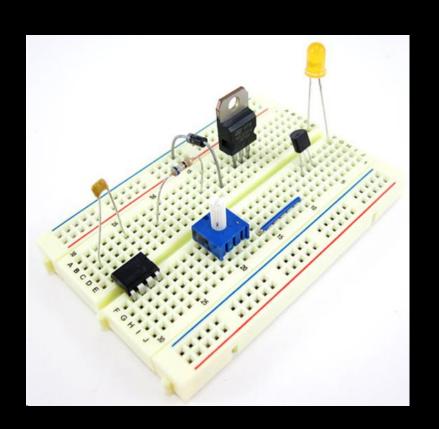

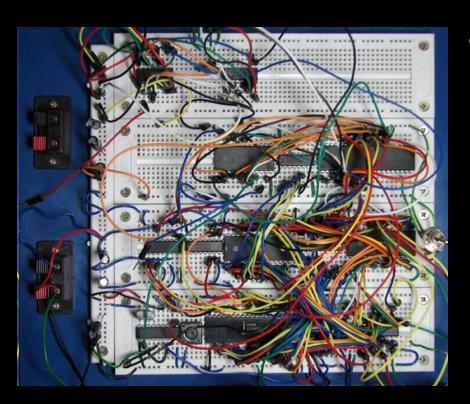- The breadboard derives its name from an early form of point-topoint construction
- In the early days of radio, amateurs would nail copper wire or terminal strips to a wooden board (often literally a board for cutting bread), and solder electronic components to them.






- The breadboard derives its name from an early form of point-topoint construction
- In the early days of radio, amateurs would nail copper wire or terminal strips to a wooden board (often literally a board for cutting bread), and solder electronic components to them.



How Does The Breadboard Work?

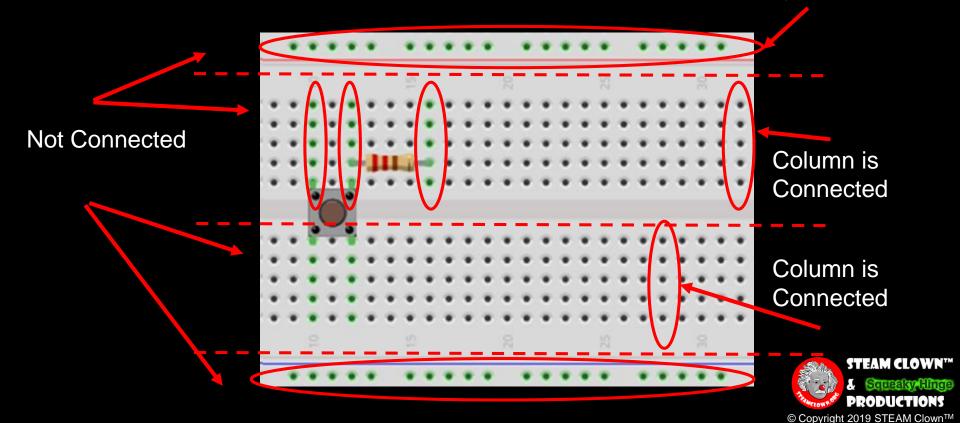All Holes In The Row Are Electrically Connected



Resources & Materials Needed

- (1) Breadboard
- (1) 5 volt Wall Power Supply
- (1) Power Adaptor
- (3-5) Jumper Wire (Male-Male)
- (1) LED
- (1) 330 Ω Resistor
- (1) Push Button Switch













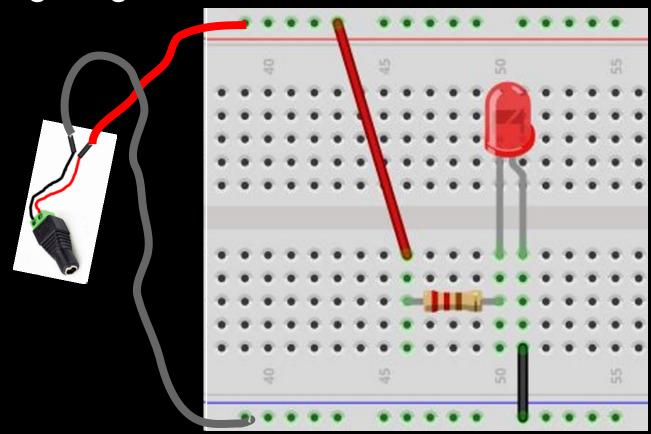




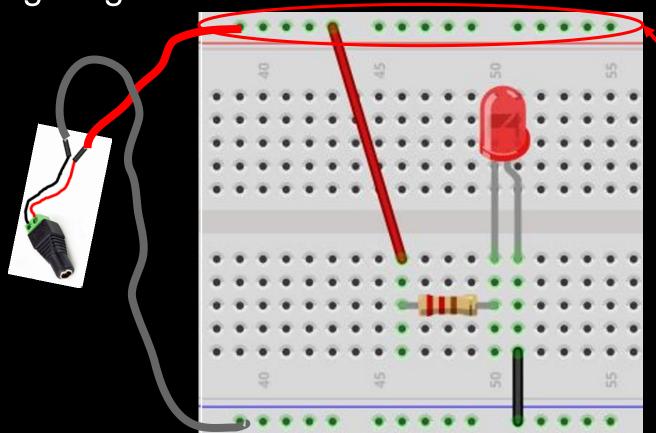


All Holes Are Connected



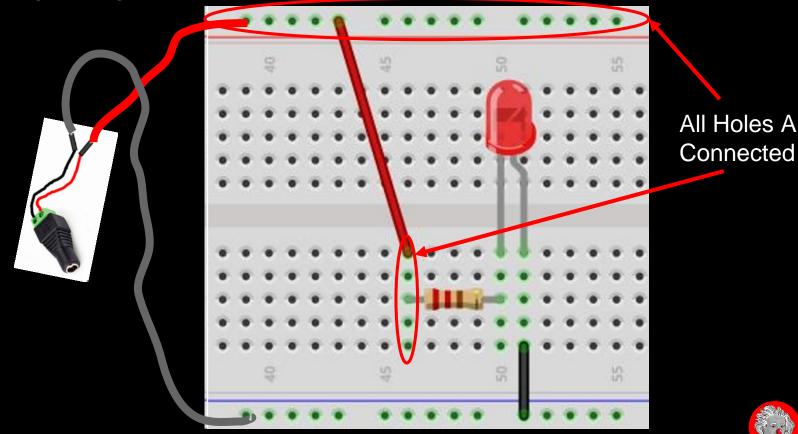


All Holes Are



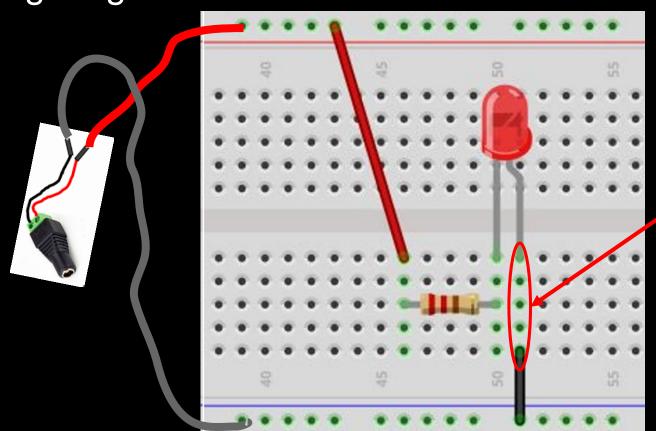


All Holes Are Connected




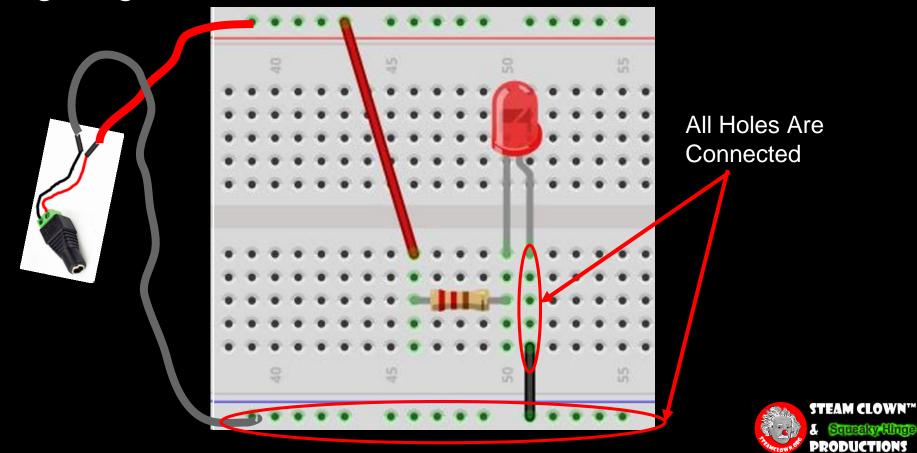

© Copyright 2019 STEAM Clown™

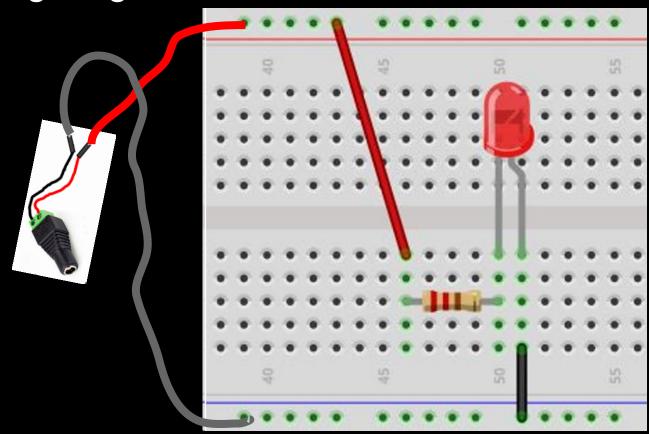




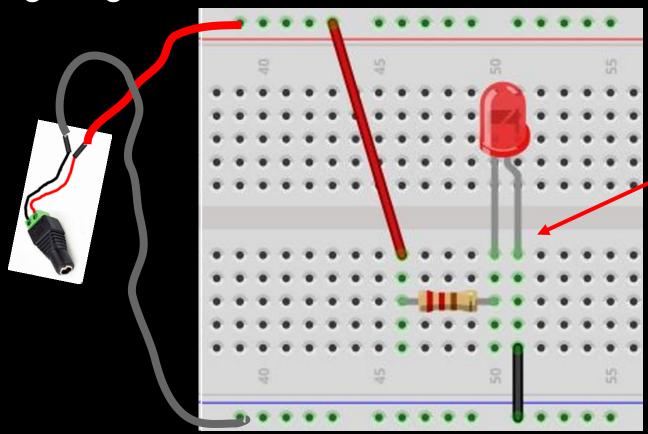


If the LED does not Light, Pull it out and turn it around to "Flip" the Pins




Lighting An LED With A Switch

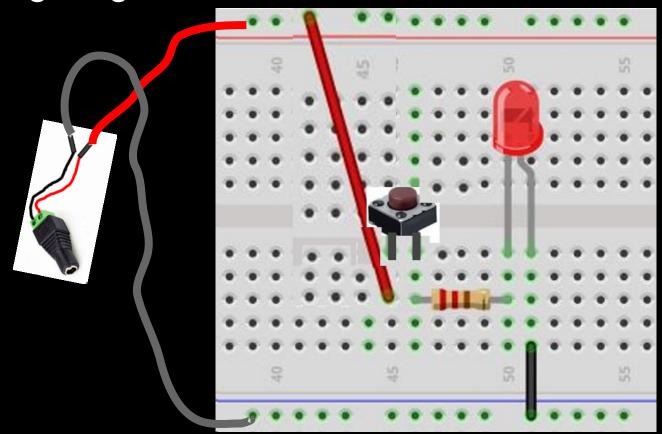





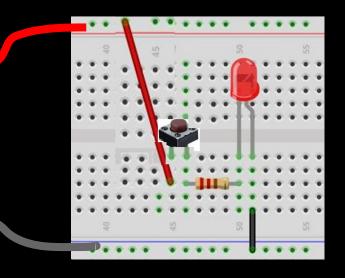


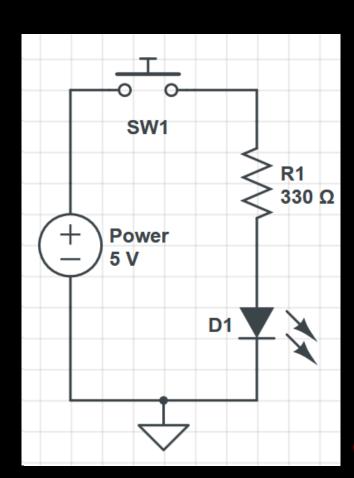





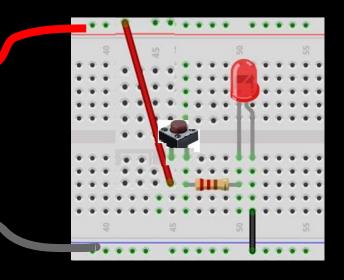


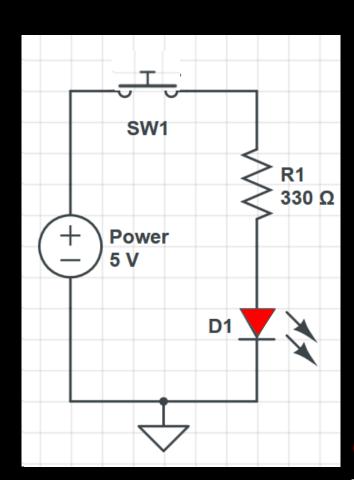

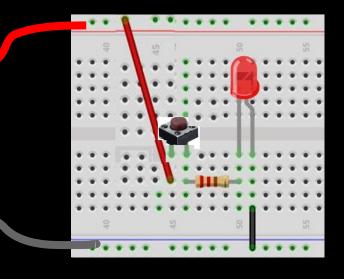

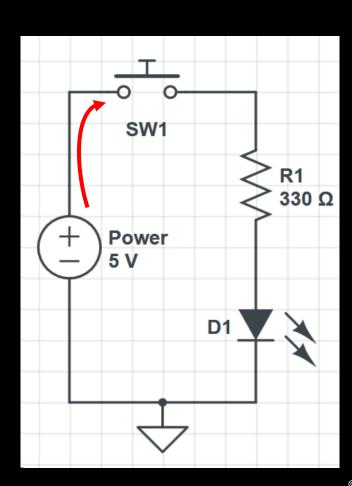

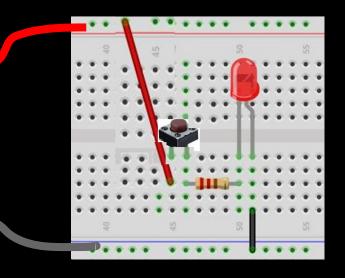

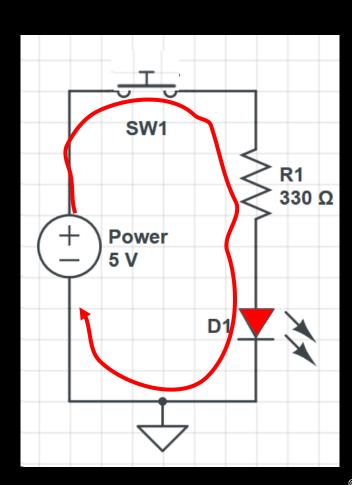







STEAM ClownTM Productions

Reference



Reference Slides

- 5 Breadboarding Quick Tips https://makezine.com/2016/12/22/breadboarding-quick-tips/
- What is a bread board https://i1.wp.com/makezine.com/wp-content/uploads/2016/12/breadboardworkshop.jpg





STEAM ClownTM Productions

Appendix





STEAM ClownTM Productions

Can I Get A Copy Of These Slides? Yes, Probably...

Most presentation lecture slides can be found indexed on www.steamclown.org and maybe blogged about here on Jim The STEAM Clown's Blog, and on STEAM Clown's Mechatronics Engineering Google site, where you can search for the presentation title. While you are there, sign up for email updates



Appendix A: License & Attribution

- This interpretation is primarily the Intellectual Property of Jim Burnham, Top STEAM Clown, at <u>STEAMClown.org</u>
- This presentation and content is distributed under the <u>Creative Commons</u> <u>License CC-BY-NC-SA 4.0</u>
- My best attempt to properly attribute, or reference any other sources or work I have used are listed in Appendix C

Under the following terms:



Attribution — You must give appropriate credit, provide a link to the license, and indicate if changes were made. You may do so in any reasonable manner, but not in any way that suggests the licensor endorses you or your use.



NonCommercial — You may not use the material for commercial purposes.



ShareAlike — If you remix, transform, or build upon the material, you must distribute your contributions under the same license as the original.

No additional restrictions — You may not apply legal terms or technological measures that legally restrict others from doing anything the license permits.



Appendix B: License & Attribution

- This interpretation is primarily the Intellectual Property of Jim Burnham, Top STEAM Clown, at STEAMClown.org
- The programming code found in this presentation or linked to on my Github site is distributed under the:
 - o GNU General Public License v3.0
 - o European Union Public Licence EUPL 1.2 or later
- My best attempt to properly attribute, or reference any other sources or work I have used are listed in Appendix C











Appendix C: Primary Sources & Attribution for Material Used

- 5 Breadboarding Quick Tips https://makezine.com/2016/12/22/breadboarding-quick-tips/
- What is a bread board https://i1.wp.com/makezine.com/wp-content/uploads/2016/12/breadboardworkshop.jpg

