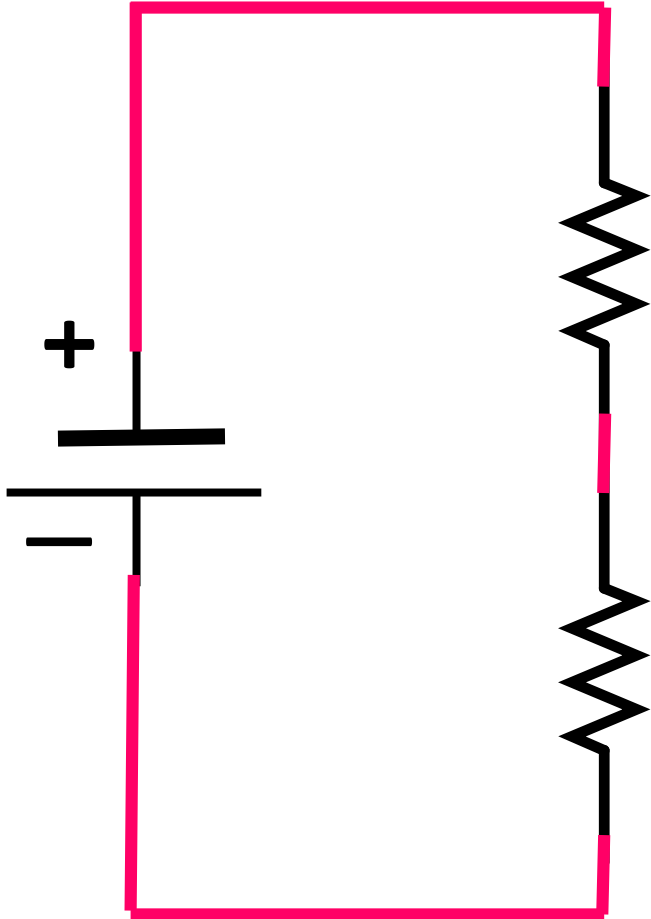


WHAT TO ADD NEXT TIME YOU UPDATE?


- Work sheet with 3 and 4 resistors
- Create worksheet of tables
- Add Hypothesis and Questions
- Add Lab and Lecture Objectives
- Add equipment needed
- Add science standards
- Review links for additional content

PARALLEL CIRCUITS

SERIES & PARALLEL CIRCUITS




SERIES CIRCUIT

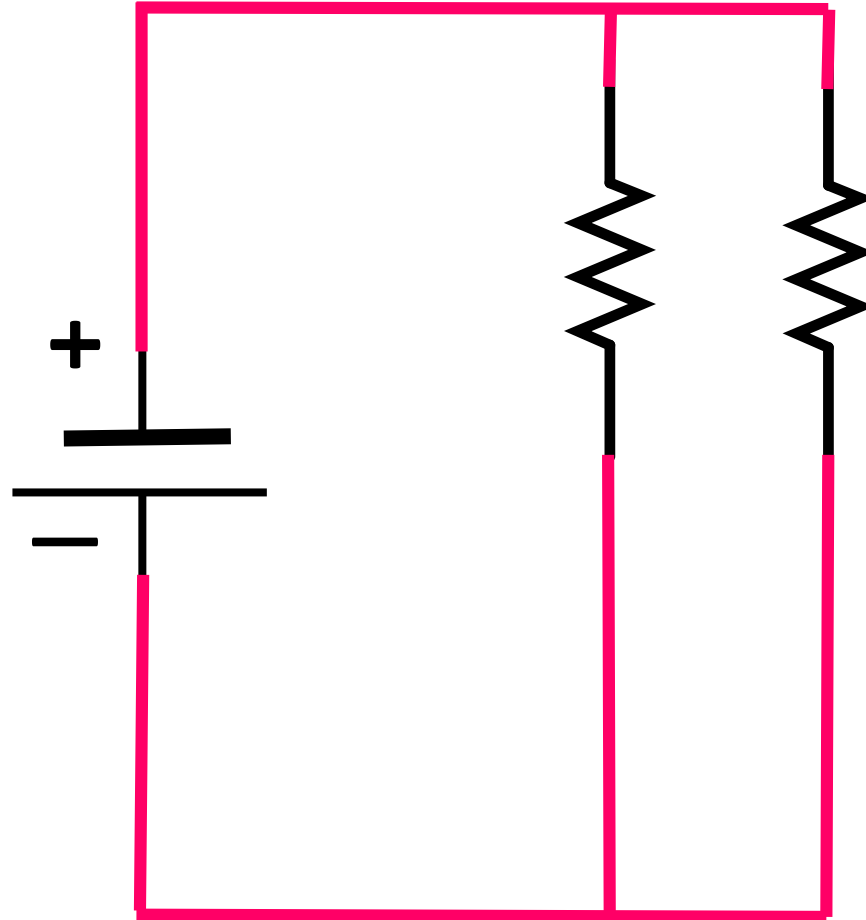

PARALLEL CIRCUIT

TRICK TO REMEMBER OHM'S LAW

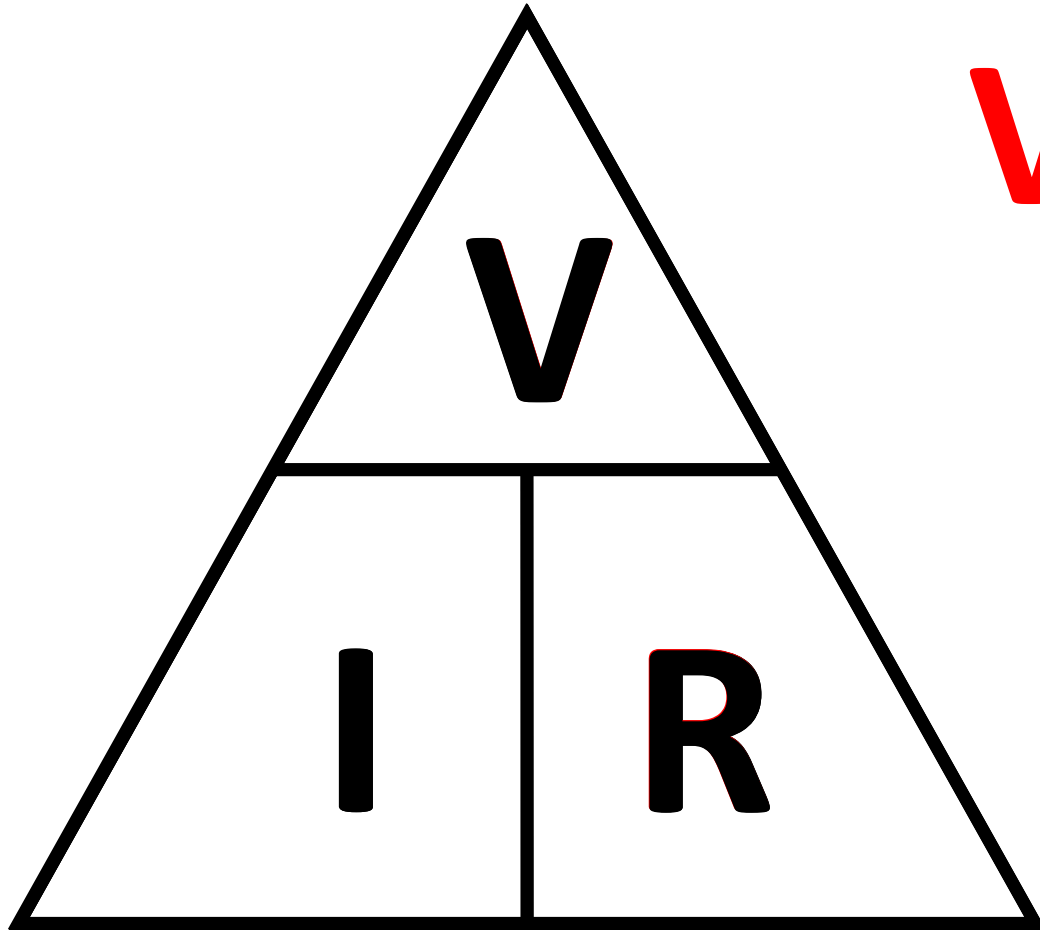

$$V = I * R$$


$$R = \frac{V}{I}$$

$$I = \frac{V}{R}$$

REMEMBER, A SERIES CIRCUIT

- Complete, Closed Circuit
- Single Path from +V to GND
- The same current is flowing in both resistors

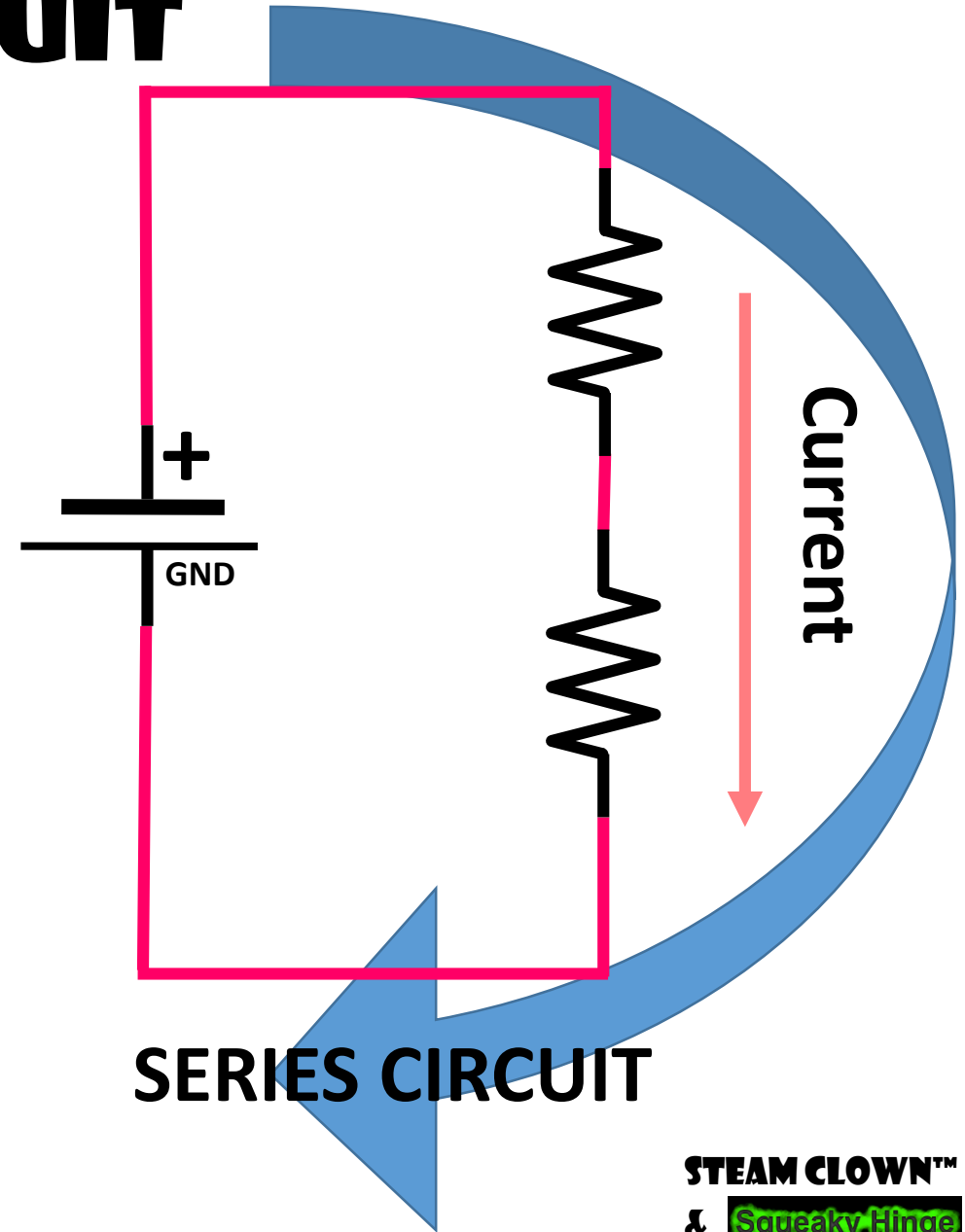
Yes, there is only one path for the current and it is the same at all points in the circuit



PARALLEL CIRCUITS

- Complete, Closed Circuit
- Multiple Paths from +V to GND
- Is the same current flowing in all paths?

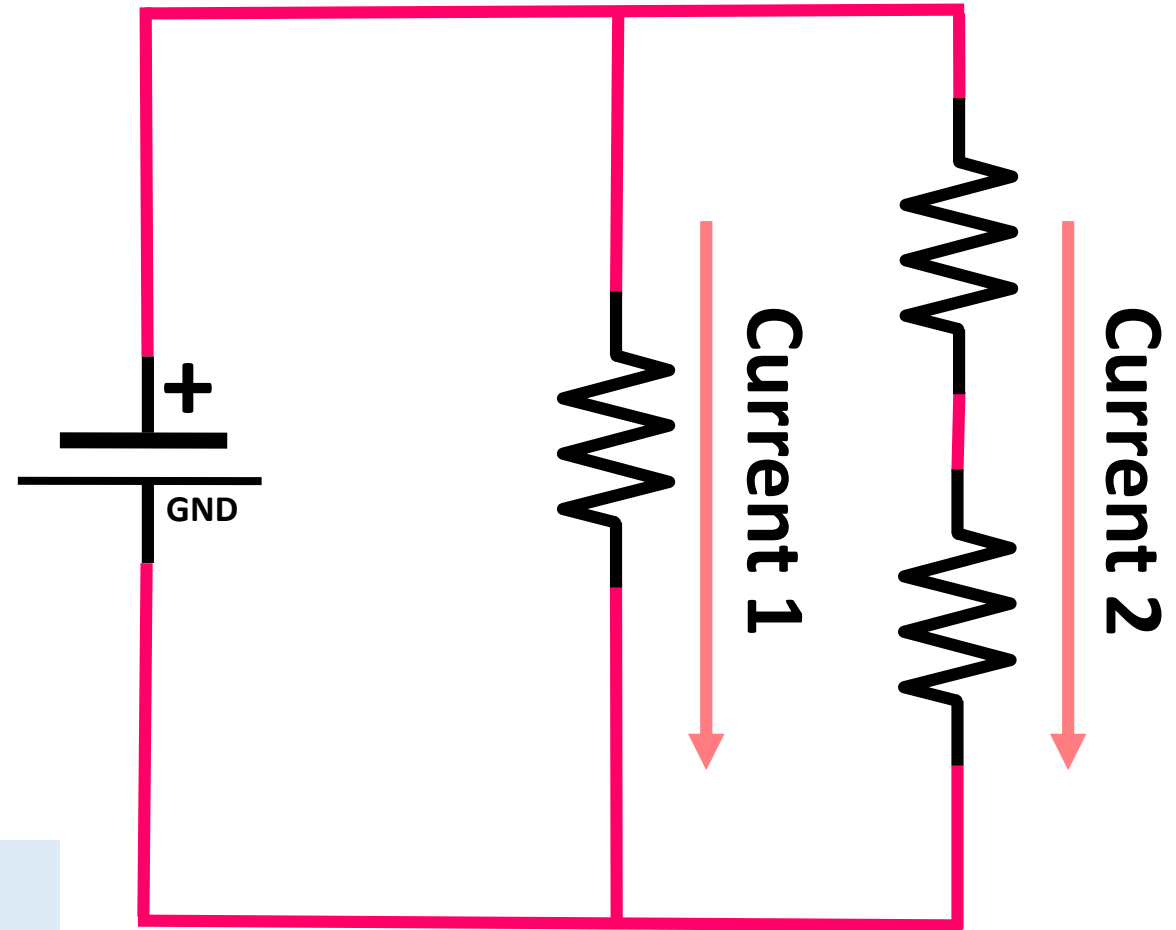No, there are multiple paths, so there is multiple currents. Each path can have different Current.




PARALLEL CIRCUIT

PARALLEL CIRCUITS

- Is the Voltage across A & B the same as across C & D? in all paths?

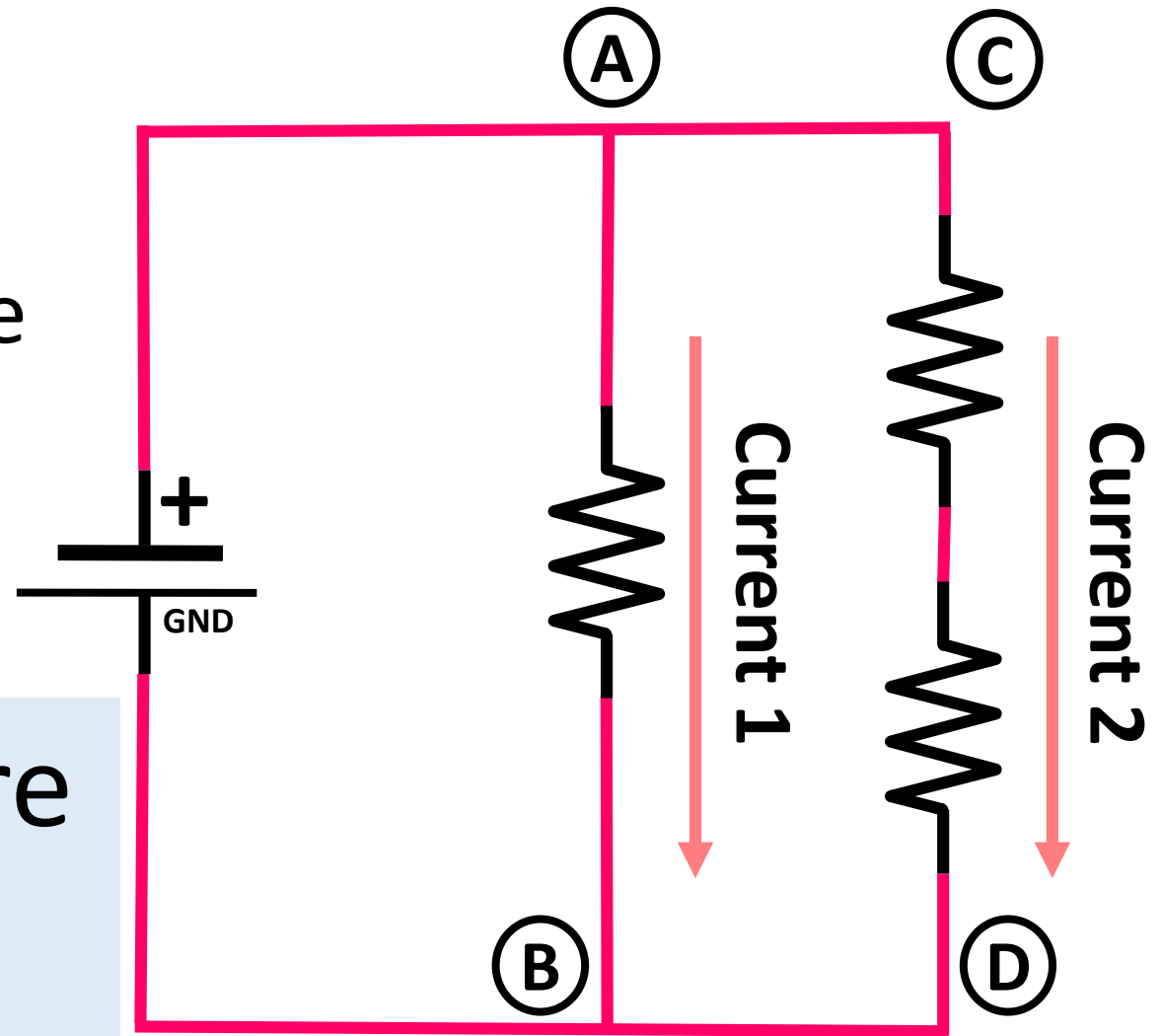
Yes, electrically, A & C are the same point. B & D are too... Right?



PARALLEL CIRCUIT

PARALLEL CIRCUITS

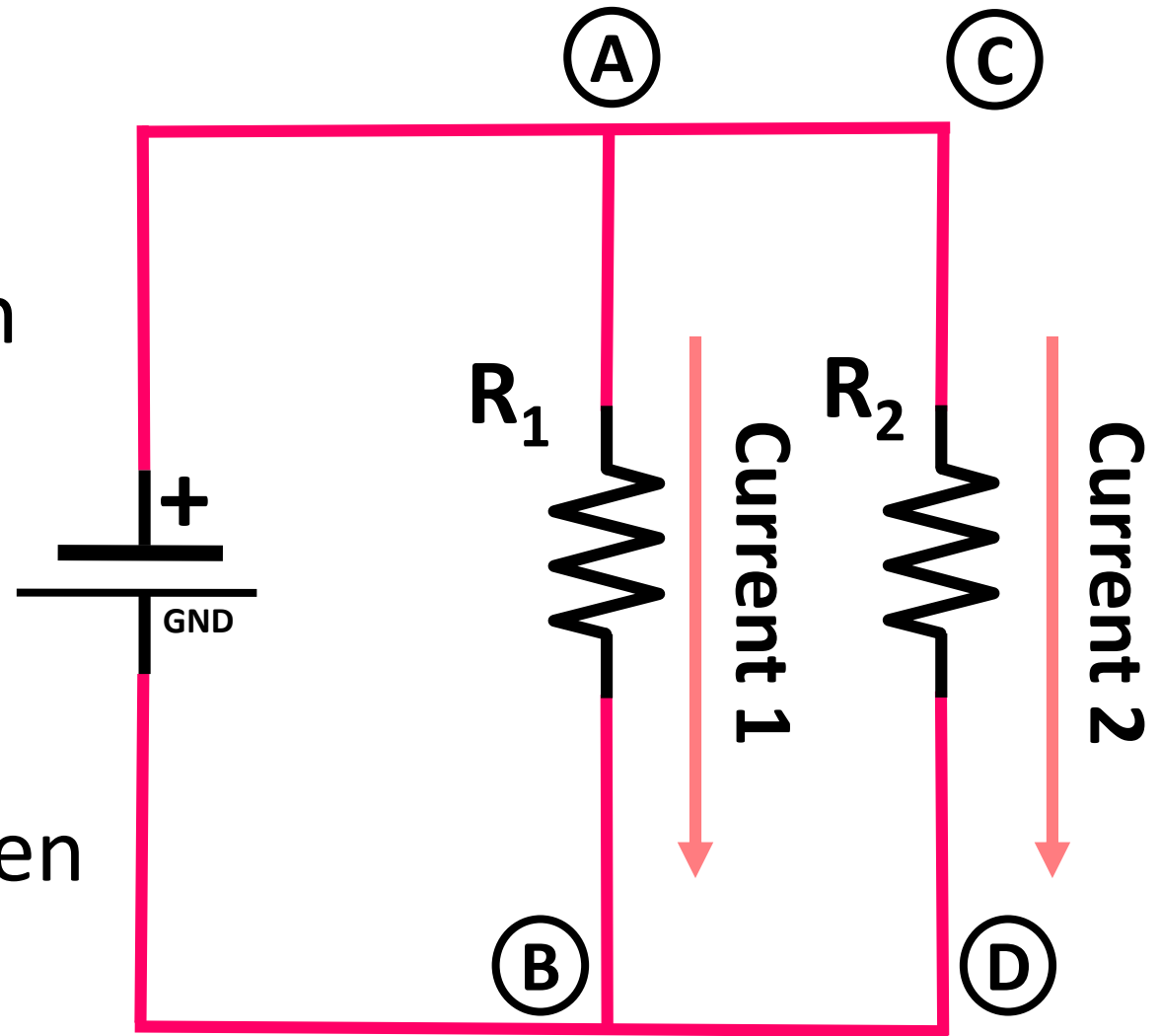- If R_1 & R_2 were both $1\text{K}\Omega$ then you really have two $1\text{K}\Omega$ resistors as “loads” drawing current from the same power supply
- If 2x the current is flowing, then what does that mean for the equivalent resistance?



PARALLEL CIRCUIT

GO GET THE FOLLOWING

- Power Supply ← the smaller ones are better
- Power to Breadboard Adaptor
- Breadboard
- About 6 wire
- 1 plastic cup
- Resistors:
 - One **100Ω** resistor
 - Two **330Ω** resistors
 - One **680Ω** resistor
 - Two **1KΩ** resistors
 - One **2KΩ** resistor

LAB TIME...



LOG SOME DATA

- Open your log books
- On the next available Page
 - Note the Date
 - Draw a table (“for a fixed 5 volt power supply”)

Parallel Circuit Measurements	Measured Resistance	Measured Voltage	Measured Current
R1 + R2 (measure in parallel)			
R1 = 1K Ω			
R2 = 1K Ω			



BUILD THIS PARALLELS CIRCUIT

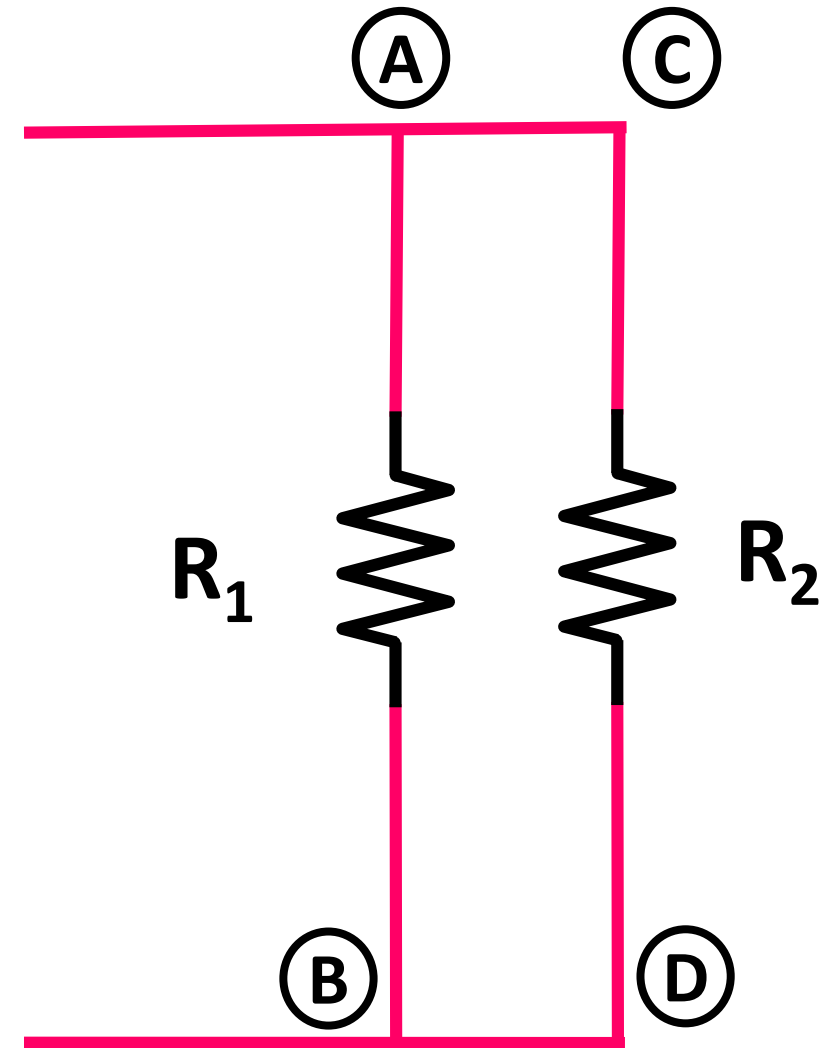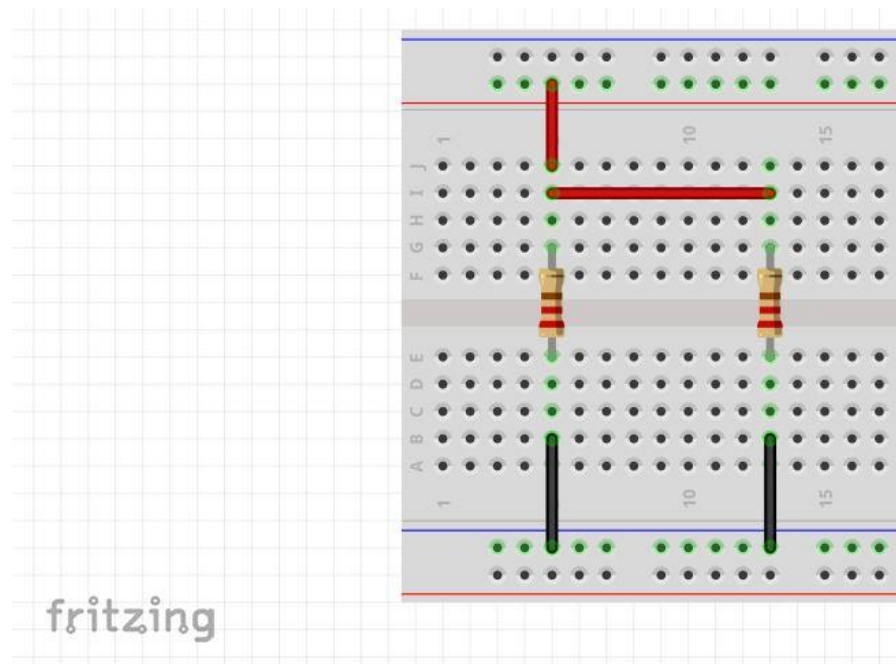- How do you measure each resistor in a Parallel circuit?
- How do you measure the total resistance, as seen by the power supply?
- $R_1 = 1K\Omega$
- $R_2 = 1K\Omega$





MEASURING INDIVIDUAL RESISTORS IN A PARALLEL CIRCUIT

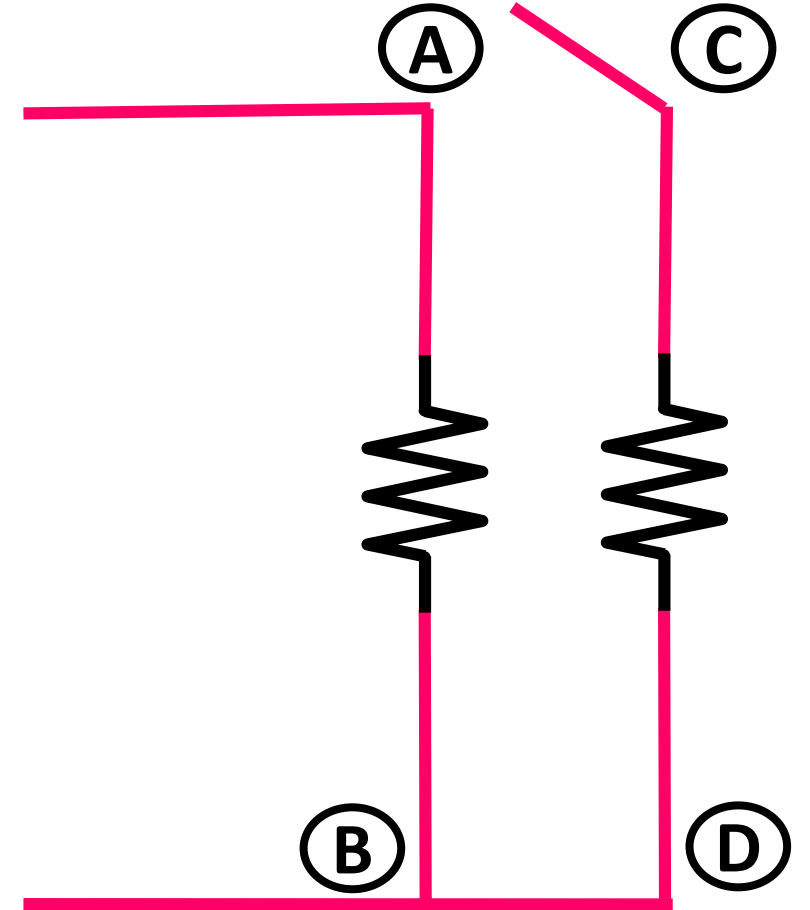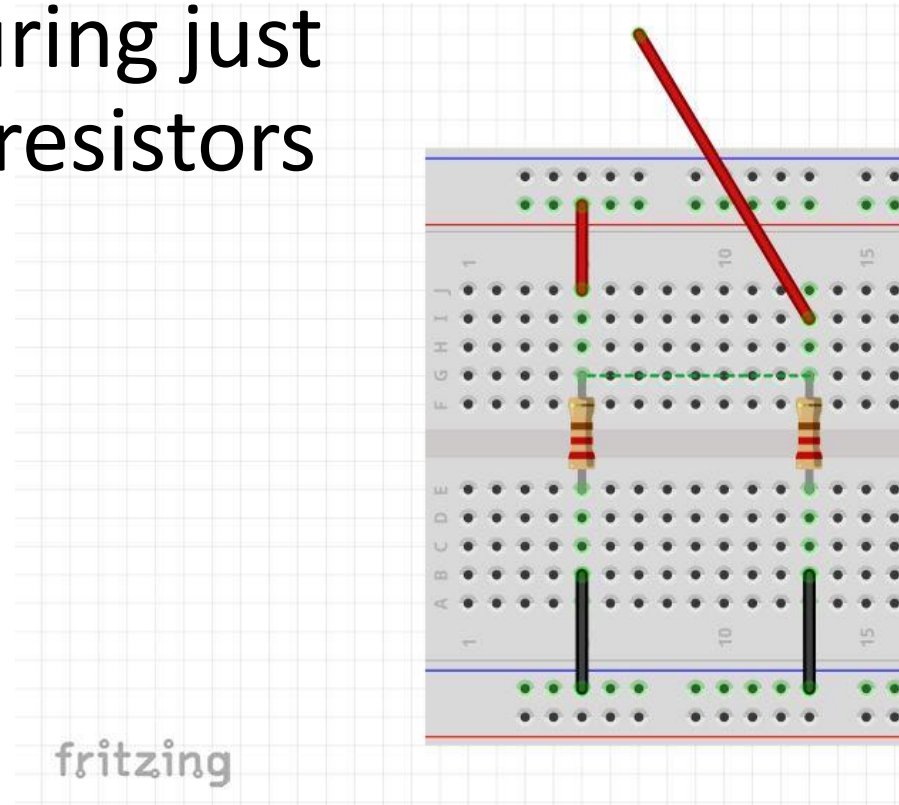
- To measure each resistor, you need to make sure you are measuring just the individual resistors




BUILD THIS PARALLELS CIRCUIT

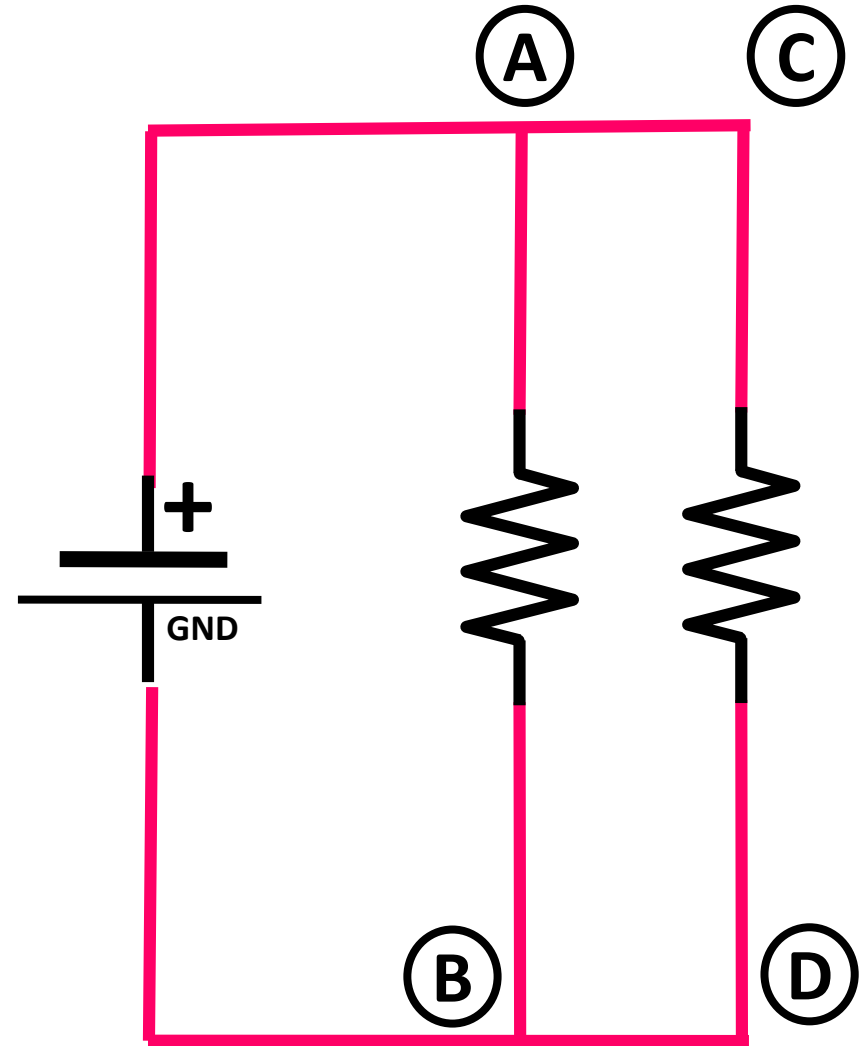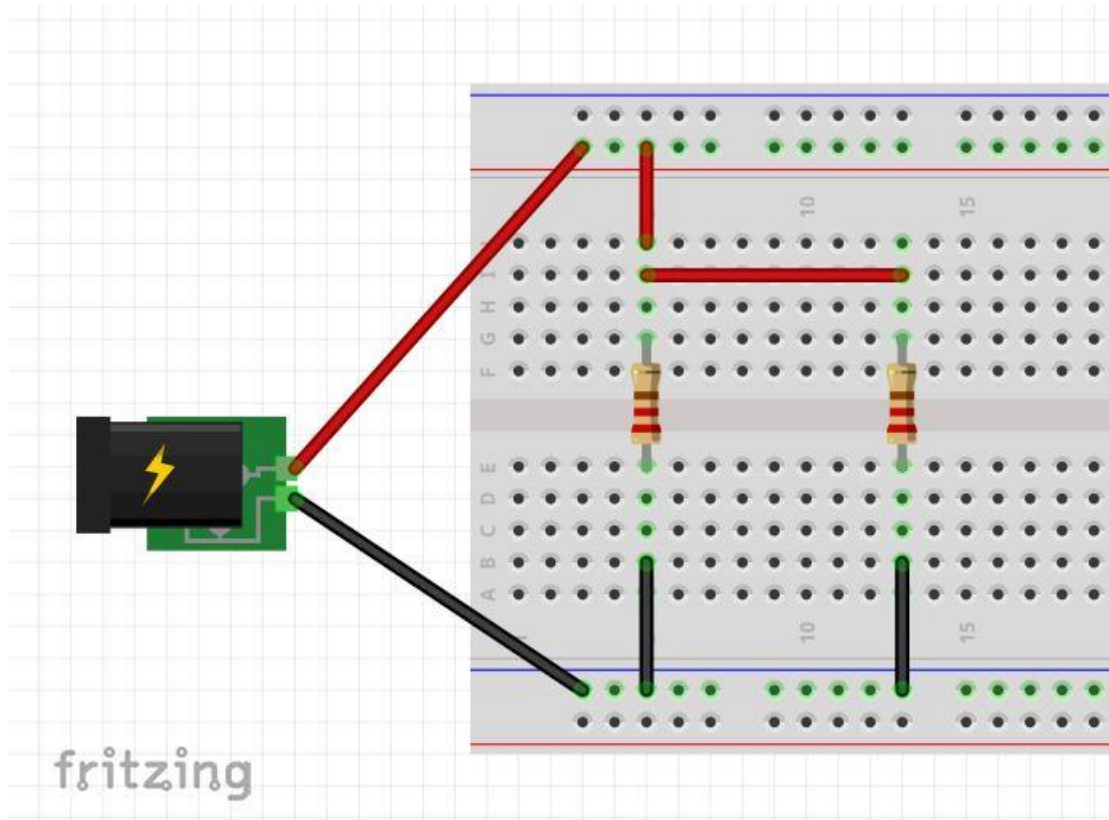


MEASURING INDIVIDUAL RESISTANCE

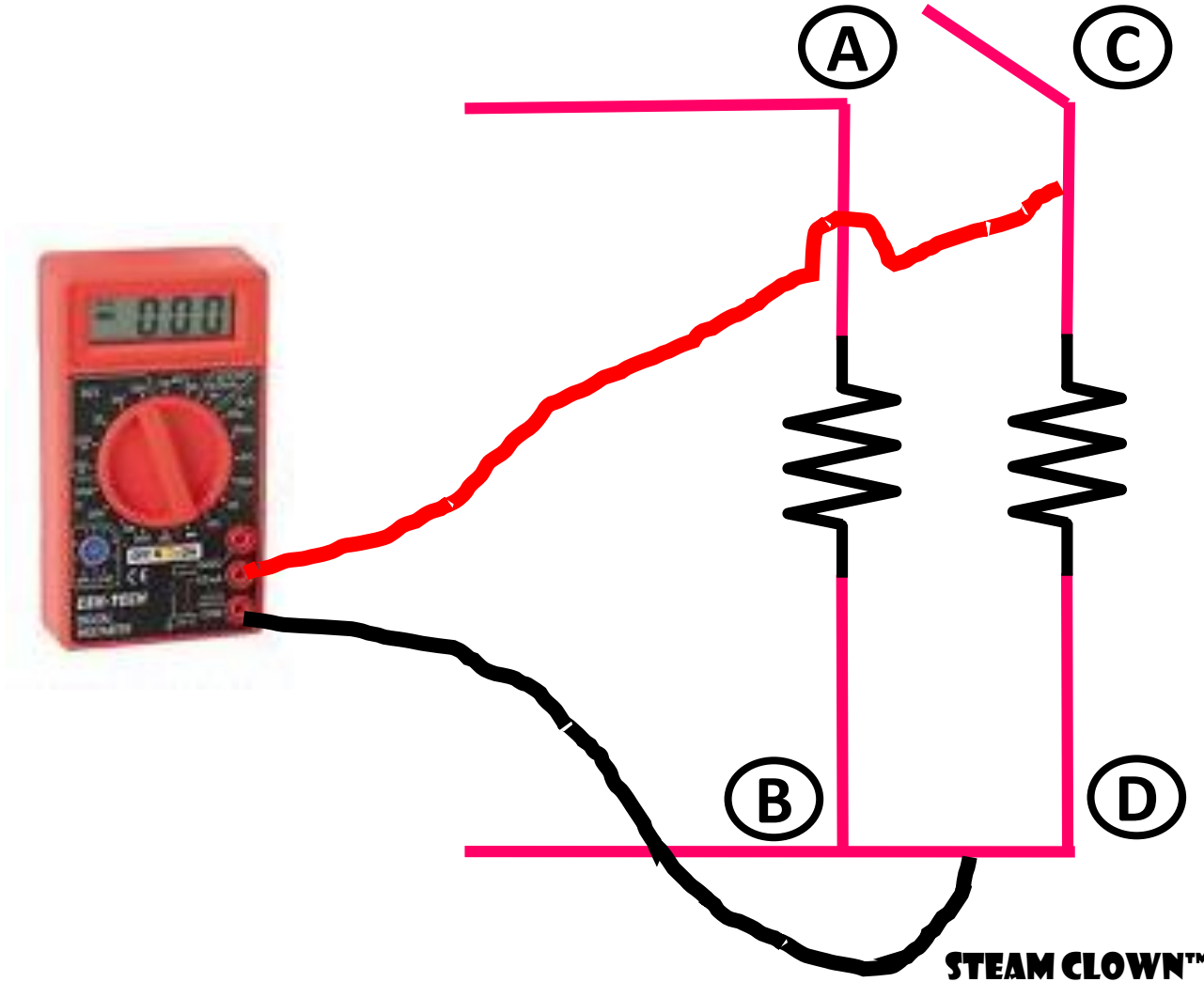


MEASURING TOTAL RESISTANCE

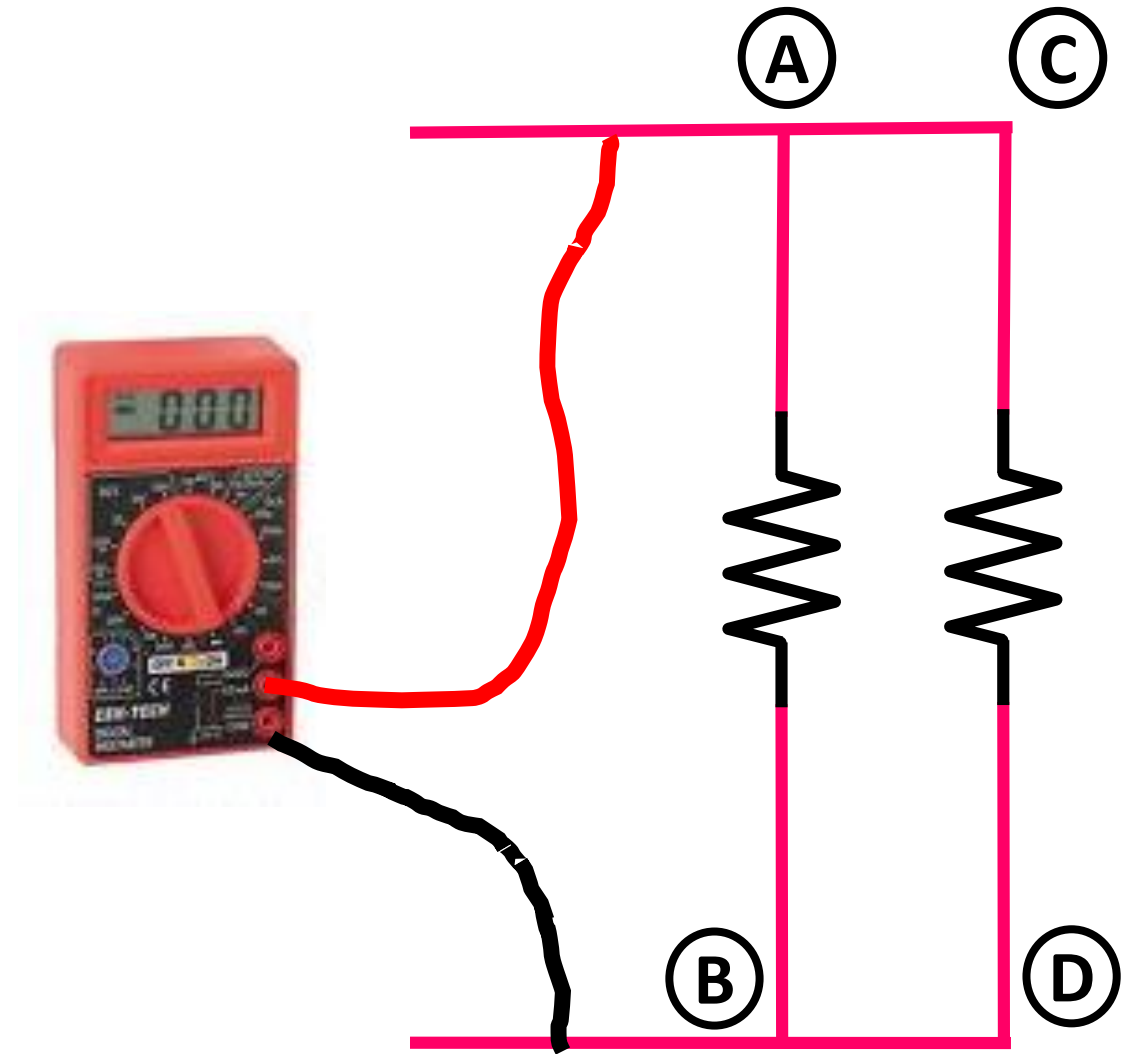

MEASURING TOTAL VOLTAGE

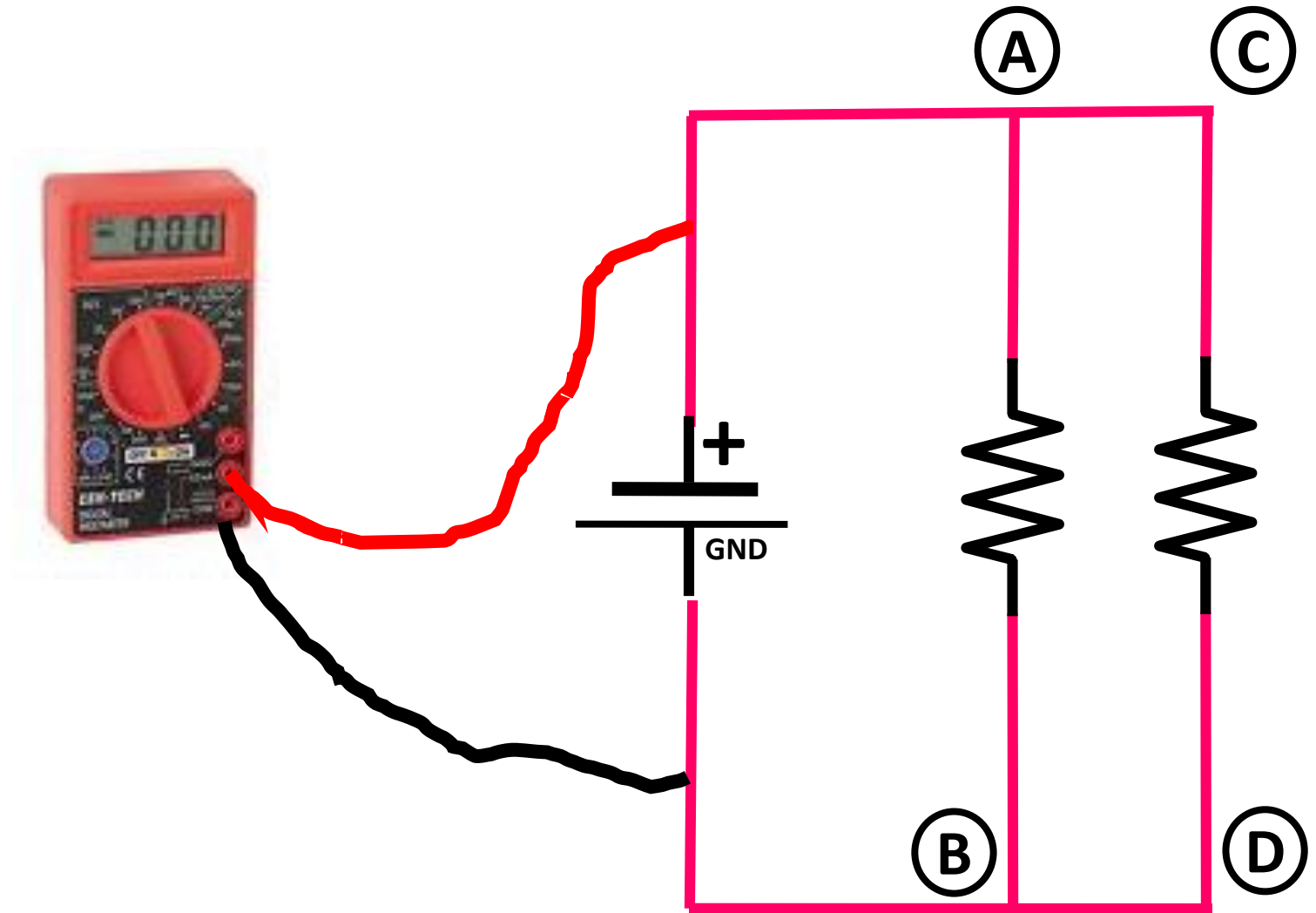


MEASURING INDIVIDUAL CURRENT

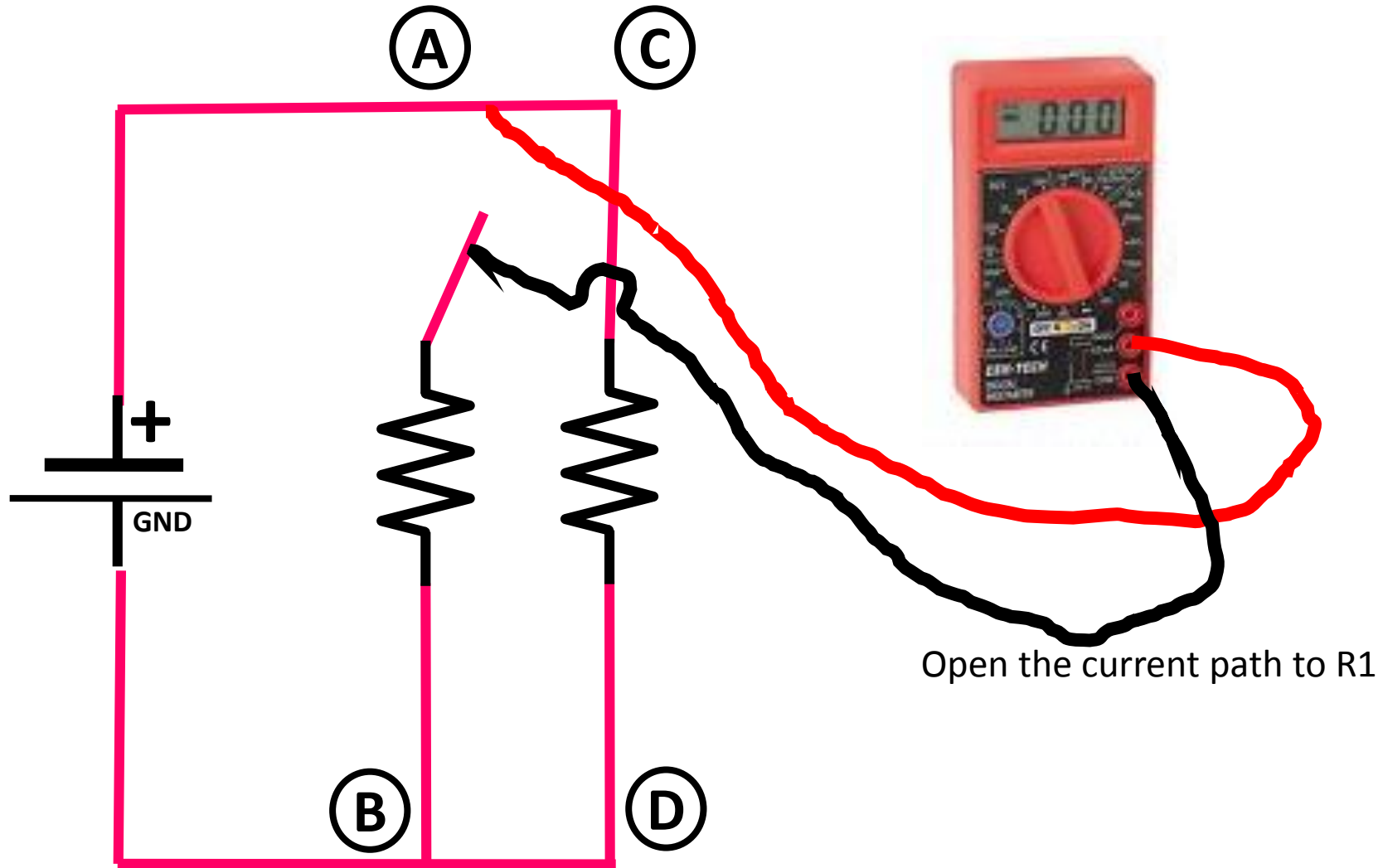


Open the current path to R1

MEASURING INDIVIDUAL CURRENT

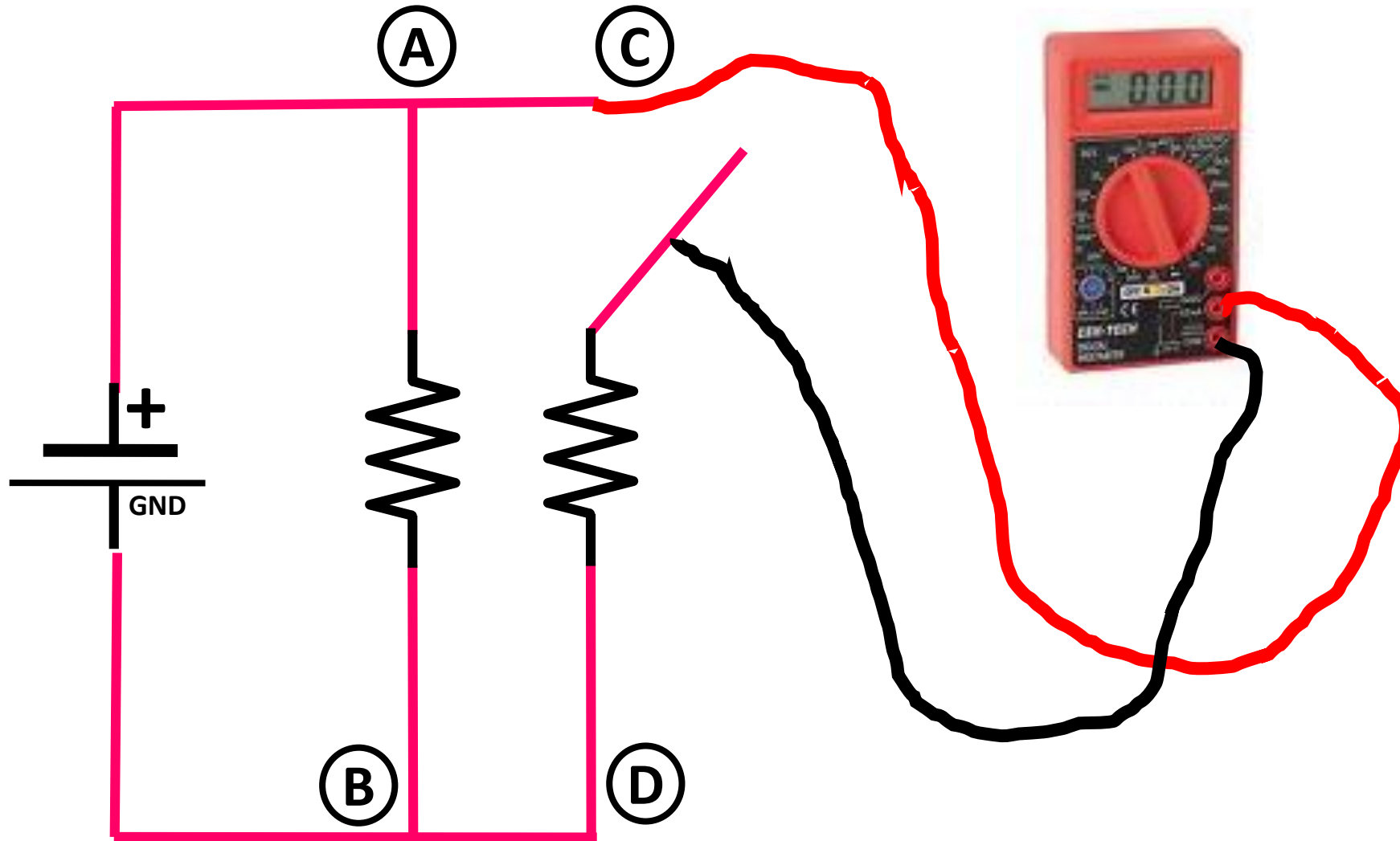

MEASURING TOTAL CURRENT?

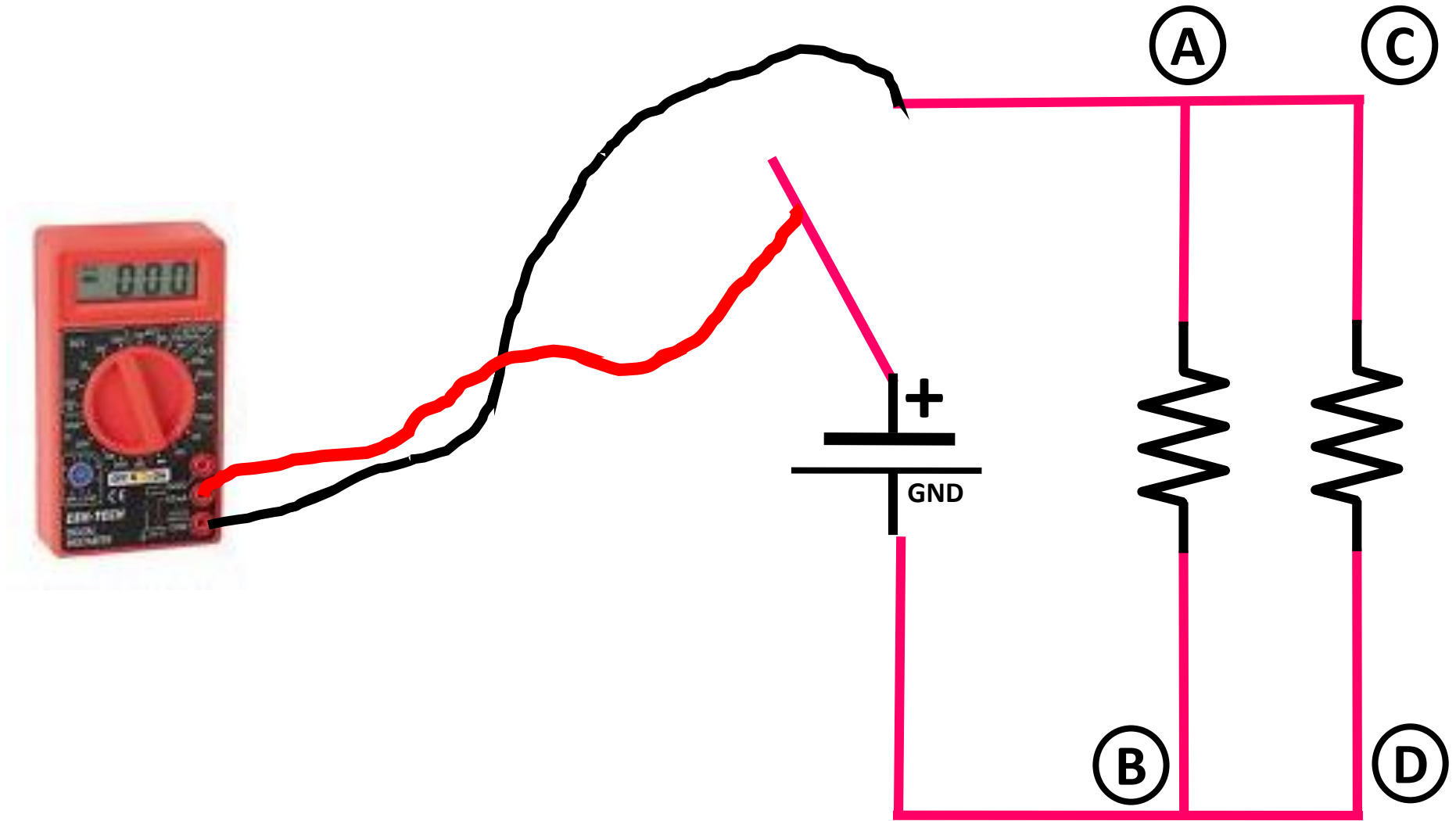

LAB - REPEAT WITH MORE RESISTOR VALUES

- Re-do lab measurements with different R_1 & R_2
 - $R_1 = 100\Omega$ & $R_2 = 330\Omega$
 - $R_1 = 100\Omega$ & $R_2 = 1K\Omega$
 - $R_1 = 680\Omega$ & $R_2 = 2K\Omega$


Parallel Circuit Measurements	Measured Resistance	Measured Voltage	Measured Current
$R_1 + R_2$ (measure in parallel)			
$R_1 = 100\Omega$			
$R_2 = 330\Omega$			

MATH BEHIND THE MEASUREMENTS

PARALLEL CIRCUITS

- Is the Voltage across A & B the same as across C & D? in all paths?

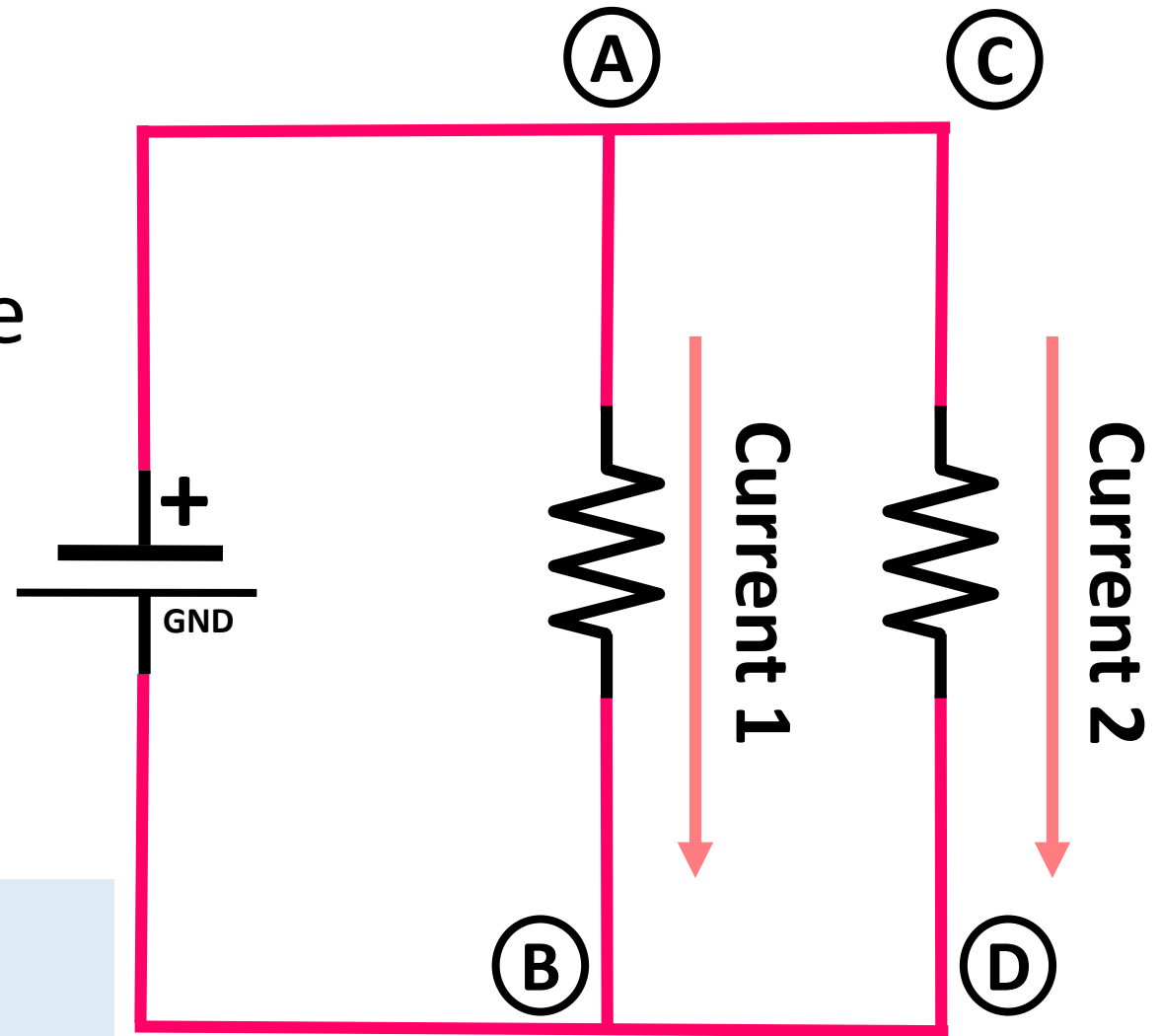The total resistance of parallel resistors is always less than the smallest individual resistor



PARALLEL CIRCUIT

CALCULATING PARALLEL RESISTORS

- Add the Reciprocals of the individual Resistors to get the reciprocal or the total Resistance
- If you only have 2 resistors

$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_n}$$

PARALLEL CIRCUIT RESISTANCE

$$R_1 = 330\Omega, R_2 = 330\Omega \quad R_t = \underline{\hspace{2cm}}$$


$$R_1 = 330\Omega, R_2 = 680\Omega \quad R_t = \underline{\hspace{2cm}}$$

$$R_1 = 1K\Omega, \quad R_2 = 2K\Omega \quad R_t = \underline{\hspace{2cm}}$$

$$R_1 = 6800\Omega, R_2 = 1K\Omega \quad R_t = \underline{\hspace{2cm}}$$

Put in your
Lab Book
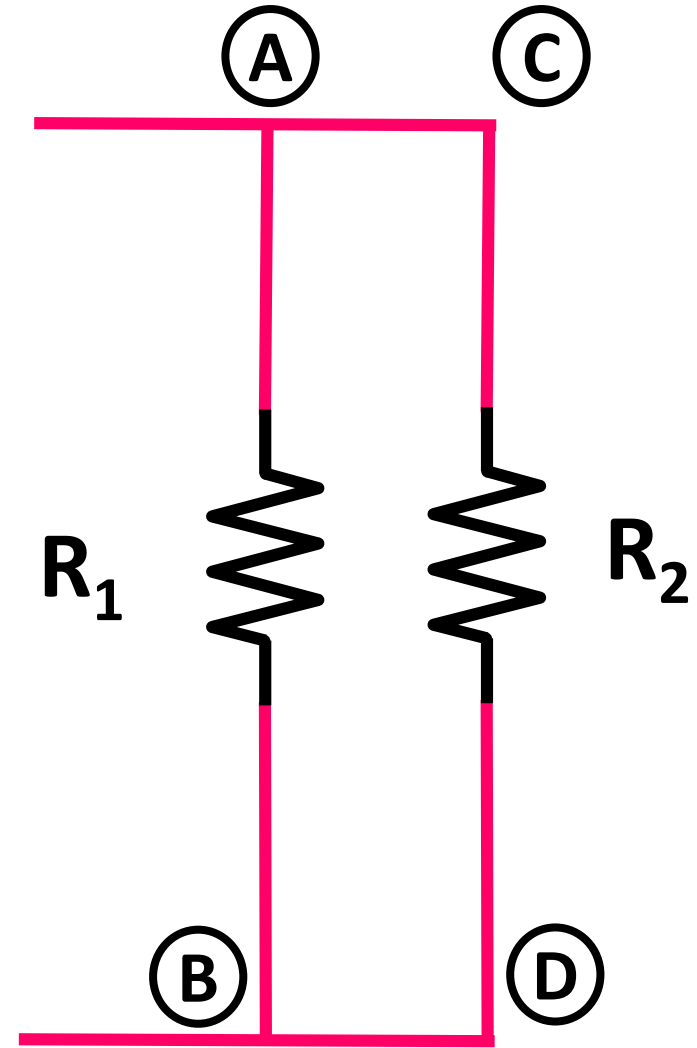
$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_n}$$



Calculate R_t


STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™


PARALLEL CIRCUITS

- $V_{cc} = 12v$
- $R_1 = 4K\Omega$
- $R_2 = 6K\Omega$
- $R_3 = 12K\Omega$
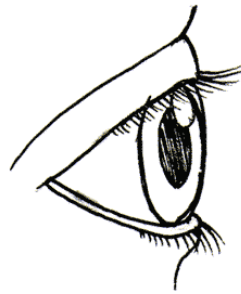
$$\frac{1}{R_t} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \frac{1}{R_n}$$



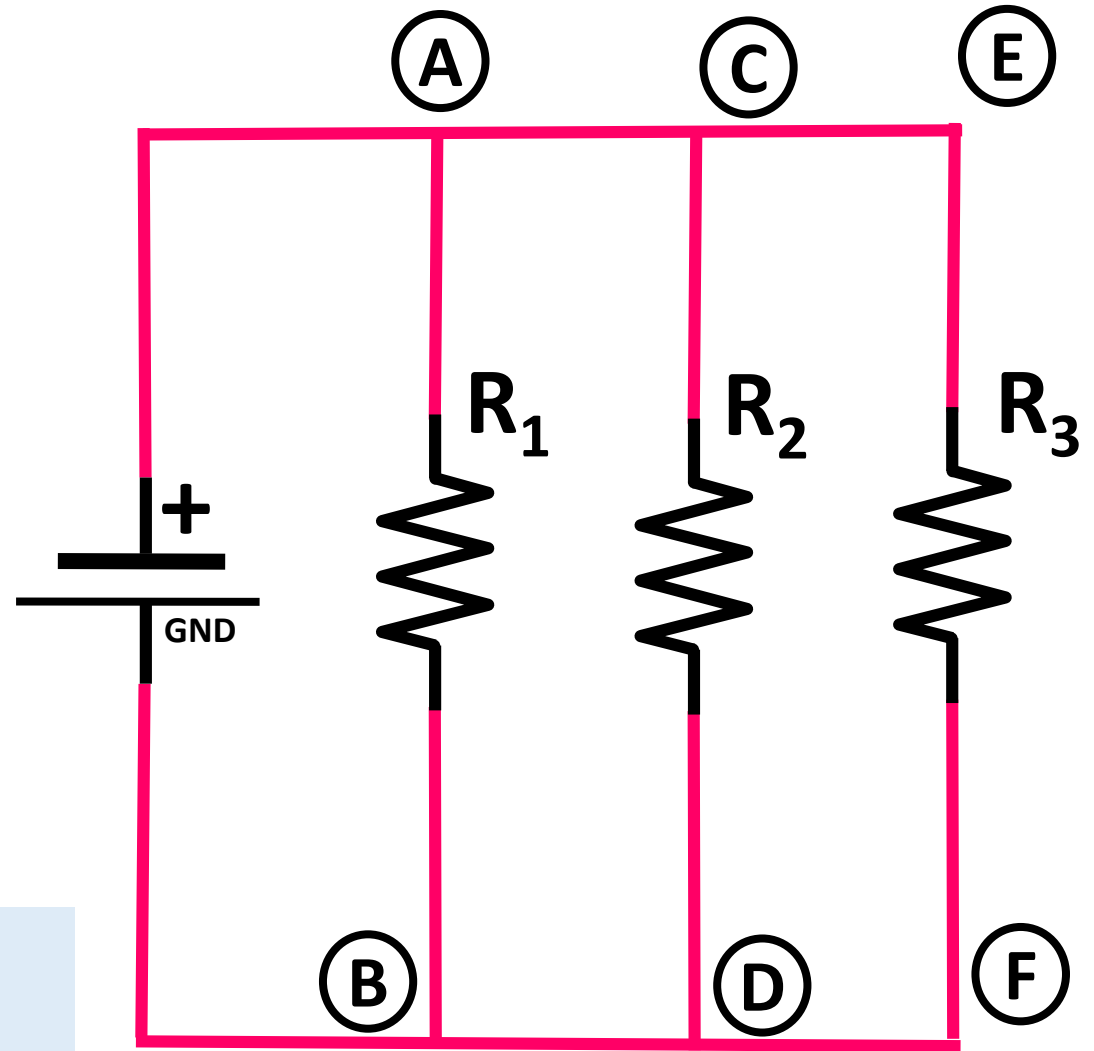What is the total resistance?
What is the current in each path?



PARALLEL CIRCUIT

REFERENCE

SOURCES

- 30 years of electronics in my head...
- Electronic Projects for Photographers
- <https://www.youtube.com/watch?v=Hck8k6ALBV8>
- <https://www.youtube.com/watch?v=2d8CUQokims>
- <https://adamcap.com/schoolwork/series-and-parallel-circuits-lab/> ←
add some of the hypothesis and Questions to the labs
- <http://www.thephysicsaviary.com/Physics/Programs/Labs/SeriesCircuitLab/index.html> <-- maybe add a lab to prove current is the same...
- <http://www.freeclassnotesonline.com/Series-Circuits-Lab.php> <--
good lab work sheet... add to presentation