



STEAM CLOWN™ PRODUCTIONS

LOGIC GATES - INTRODUCTION

OVERVIEW & INTRODUCTION

- Digital Design underpins the creation of the myriad of imaginative digital devices that surround us...
 - Computers
 - Calculators
 - Phones
 - Digital watches
 - Microwave ovens
 - Robots...

Really...
Everything



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

DIGITAL DESIGN

- Organizing an arrays of simple switches into a discrete system that performs transformations on two-level (Binary) information in a meaningful and predictable way



STEAM CLOWN™ PRODUCTIONS



**Attribution-NonCommercial-ShareAlike
3.0 Unported (CC BY-NC-SA 3.0)**

SEE APPENDIX A, FOR LICENSING & ATTRIBUTION INFORMATION

by-nc-sa-3.0

<https://creativecommons.org/licenses/by-nc-sa/3.0/>

<https://creativecommons.org/faq/#what-does-some-rights-reserved-mean>



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

WHAT YOU WILL KNOW...

- Prior Knowledge
 - Binary Numbers
 - How to count in binary
 - How to Add in Binary
 - How to Multiply in Binary
 - How...
- What You Will Know & Be Able To Do
 - Explain the difference between AND, OR, NOT logic gates
 - Read and fill out a Truth Table
 - Convert a Logical Expression in to Gate Diagram
 - Convert a Logical Expression in to a Truth Table



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

NEW WORDS...

- Binary

REVIEW BINARY NUMBERS

- Take 10 minutes and review binary numbers
 - [Binary Number Systems](#)
 - [Binary Digits](#)



HOW TO CONVERT FROM BINARY OR DECIMAL

Computer Humor

- Binary is as easy as 01, 10, 11


Convert the Following Binary Numbers:

$$0011 = ? \quad 1 \times 2 + 1 \times 1 = 3$$

$$1011 = ? \quad 1 \times 8 + 0 \times 4 + 1 \times 2 + 1 \times 1 = 11$$

$$10101 = ? \quad 1 \times 16 + 0 \times 8 + 1 \times 4 + 0 \times 2 + 1 \times 1 = 21$$
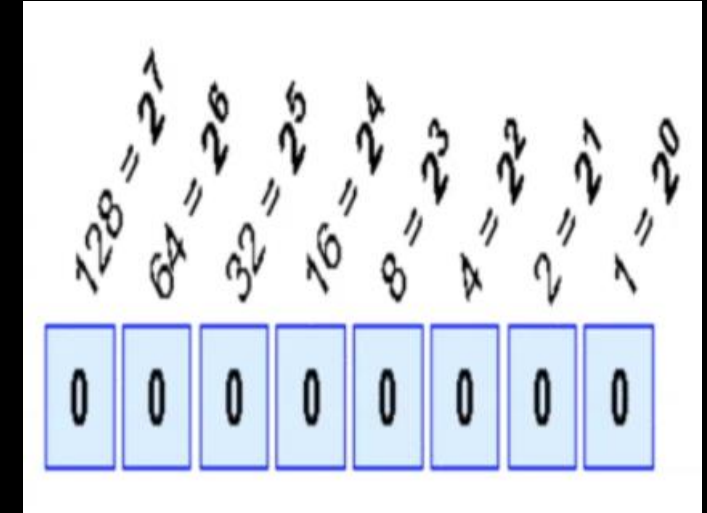
$$110011 = ? \quad 1 \times 32 + 1 \times 16 + 0 \times 8 + 0 \times 4 + 1 \times 2 + 1 \times 1 = 51$$



Place Values

BINARY QUIZ

- [https://docs.google.com/forms/d/e/1FAIpQLSc82cMmtQFs0CJ7IW1a_sVz7N6eGZl64MbAlJmrdc6ZndfYPw/viewform?usp=sf link](https://docs.google.com/forms/d/e/1FAIpQLSc82cMmtQFs0CJ7IW1a_sVz7N6eGZl64MbAlJmrdc6ZndfYPw/viewform?usp=sf_link)



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

ADDING BINARY NUMBERS

$$\begin{array}{r} 110 \\ + 101 \\ \hline 1011 \end{array}$$

Since $1 + 1 = 10$

Since $1 + 0 = 1$

Since $0 + 1 = 1$

Rule 1 $\rightarrow 0 + 0 = 0$

Rule 2 $\rightarrow 0 + 1 = 1$

Rule 3 $\rightarrow 1 + 0 = 1$

Rule 4 $\rightarrow 1 + 1 = 10 \leftarrow$ Surprise!

} Just like
decimal
addition



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

MULTIPLYING BINARY NUMBERS

$$\begin{array}{r} 110 \\ * 101 \\ \hline 110 \\ 0000 \\ 11000 \\ \hline 11110 \end{array}$$

Rule 1 $\rightarrow 0 * 0 = 0$

Rule 2 $\rightarrow 0 * 1 = 0$

Rule 3 $\rightarrow 1 * 0 = 0$

Rule 4 $\rightarrow 1 * 1 = 1$



Just like
decimal
multiplication



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

ADDING AND MULTIPLYING IN BINARY

- Adding Binary Numbers
 - [Adding in binary | Applying mathematical reasoning](#)
- Multiplying Binary Numbers
 - [Multiplying in binary | Applying mathematical reasoning](#)



BINARY LOGIC


- Deals with binary variables that take 2 discrete values (0 and 1), and with logic operations
- Three basic logic operations:
 - AND, OR, NOT
- Binary/logic variables are typically represented as letters: A, B, C, ..., X, Y, Z

BASIC LOGIC OPERATORS

- AND

- OR

- NOT

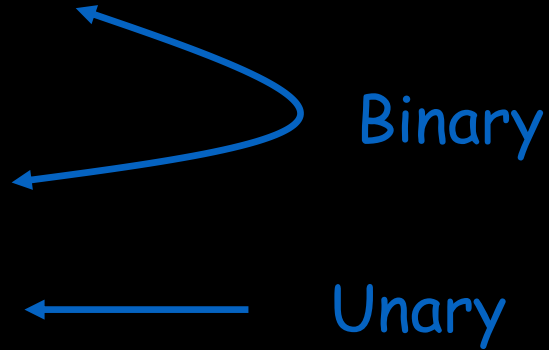

- $F(a,b) = a \cdot b$, F is 1 if and only if $a=b=1$

- $G(a,b) = a+b$, G is 1 if either $a=1$ or $b=1$

- $H(a) = a'$, H is 1 if $a=0$




STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

BINARY LOGIC FUNCTION

$F(\text{var}) = \text{expression}$

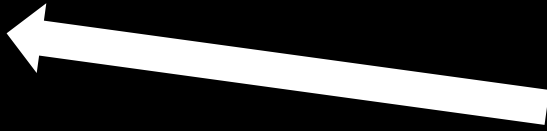

Operators (+, •, ')

Variables

Constants (0, 1)


Groupings (parenthesis)



This is a set of Binary variables
Defines the set of "Inputs"

Ex: $F(a,b) = (a' \cdot b) + b'$

$F(a,b,c) = a \cdot ((b+c') + (b'+c))$

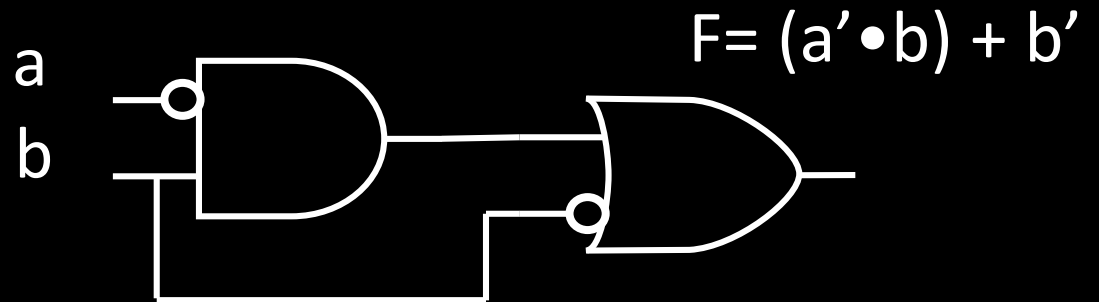

STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

BASIC AND & OR LOGIC OPERATORS


1-bit logic AND resembles binary multiplication:

$$0 \cdot 0 = 0$$

$$0 \cdot 1 = 0$$

$$1 \cdot 0 = 0$$

$$1 \cdot 1 = 1$$

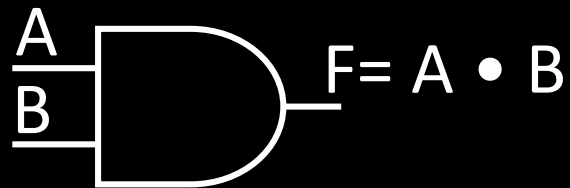


1-bit logic OR resembles binary addition, except for one operation:

$$0 + 0 = 0$$

$$0 + 1 = 1$$

$$1 + 0 = 1$$

$$1 + 1 = 1 (\neq 10_2)$$

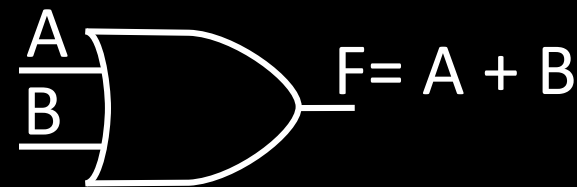

STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS




© Copyright 2017 STEAM Clown™

COMBINATIONAL LOGIC GATES

- Outputs depend directly on their inputs
- Outputs are generated asynchronously and instantaneous*
- Do not require a clock or other synchronous signals
- Let's call them "Logic Gates"

LOGIC GATES

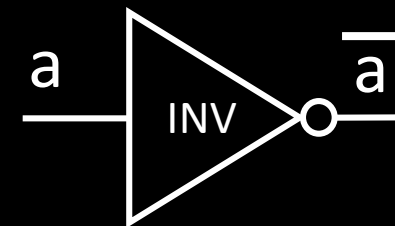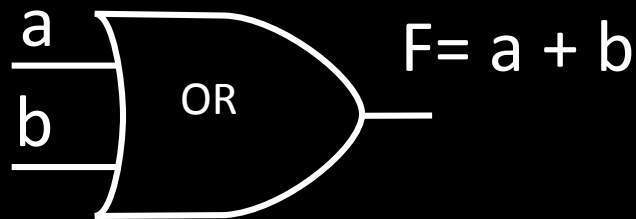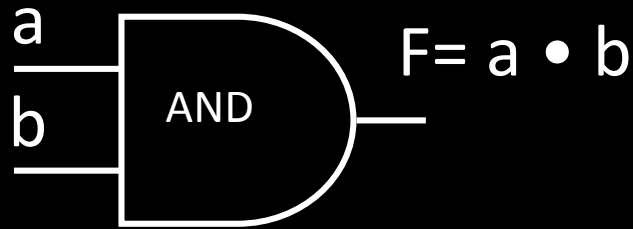- Logic gates are abstractions of electronic circuit components that operate on one or more input signals to produce an output signal




AND GATE

- This AND gate has two inputs and an output
- Output is zero unless both Inputs are 1's

The AND operation is mathematically defined as the product of two Boolean values

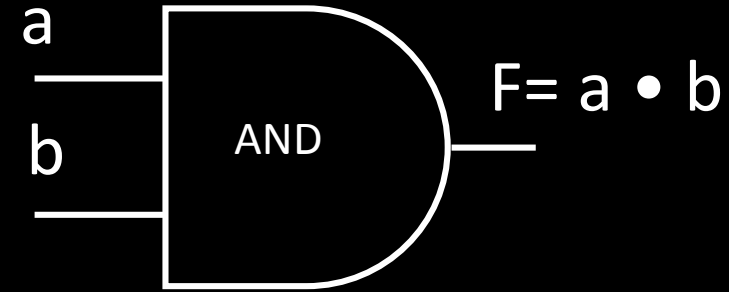Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output



2-Input AND

A	B	F=A•B
0	0	0
0	1	0
1	0	0
1	1	1




STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

OR GATE

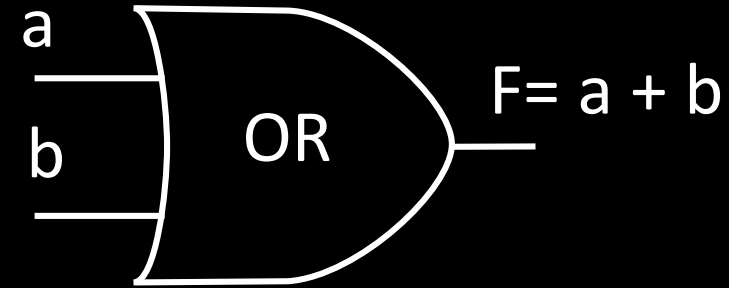- This OR gate has two inputs and an output
- Output is 1 if any of the Inputs are 1's



The OR operation is mathematically defined as the summation of two Boolean values

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input OR

A	B	F=A+B
0	0	0
0	1	1
1	0	1
1	1	1




STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

NOT (INVERTER) GATE

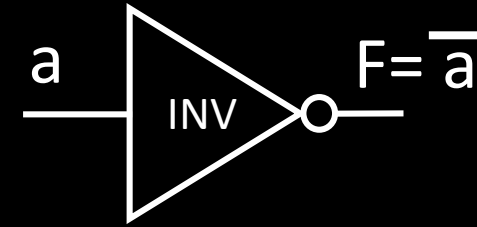- This NOT gate has one input and one output
- This is an “inverter” function
- Output is 1 if the Input is 0, and 0 if the Input is 1



(Inverter)
NOT

a	F = \bar{a}
0	1
1	0

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output

TRUTH TABLES FOR LOGIC OPERATORS

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input AND

A	B	$F=A \cdot B$
0	0	0
0	1	0
1	0	0
1	1	1

2-Input OR

A	B	$F=A+B$
0	0	0
0	1	1
1	0	1
1	1	1

NOT

A	$F=A'$
0	1
1	0



TRUTH TABLES - CHECK FOR UNDERSTANDING

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input AND

A	B	$F=A \cdot B$
0	0	
0	1	
1	0	
1	1	

2-Input OR

A	B	$F=A+B$
0	0	
0	1	
1	0	
1	1	

NOT

A	$F=A'$
0	
1	



TRUTH TABLES - CHECK FOR UNDERSTANDING

Q: Let a function $F()$ depend on n variables.

How many rows are there in the truth table of $F(a,b) = (a+b)$?

What about $F(a,b,c) = (a+b+c)$?

What about $F(a,b,c,d) = (a+b+c+d)$?

A	B	F=A+B
0	0	0
0	1	1
1	0	1
1	1	1

A: 2^n rows, since there are 2^n possible binary patterns / combinations for the n variables



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS




© Copyright 2017 STEAM Clown™

CHECK OUT THIS LOGIC LINK

- Learning about Logic Gates and Circuits
 - <https://logic.ly/lessons/>




LOGIC GATES - CHECK FOR UNDERSTANDING

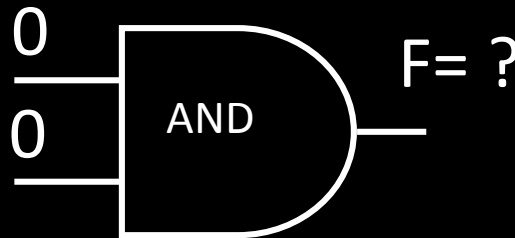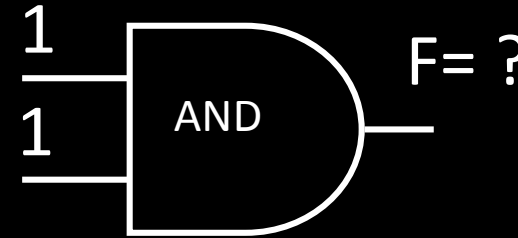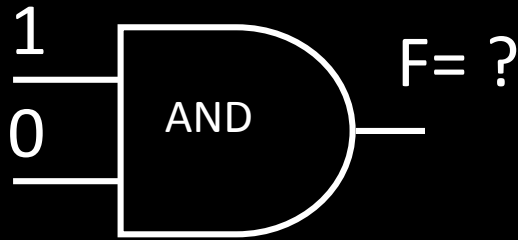- What are the outputs for each of these gates with the specified inputs values?



LOGIC GATES - CHECK FOR UNDERSTANDING

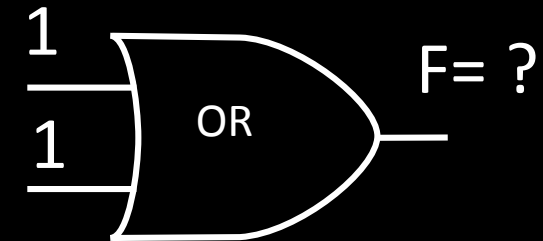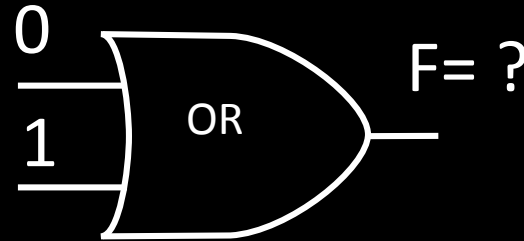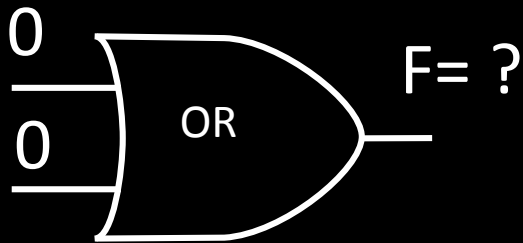- What are the outputs for each of these gates with the specified inputs values?





AND GATE + INVERTER

- This NAND gate has two inputs and an output
- Output is 1 unless both Inputs are 1's, then it's 0

2-Input NAND

A	B	F=A•B
0	0	1
0	1	1
1	0	1
1	1	0

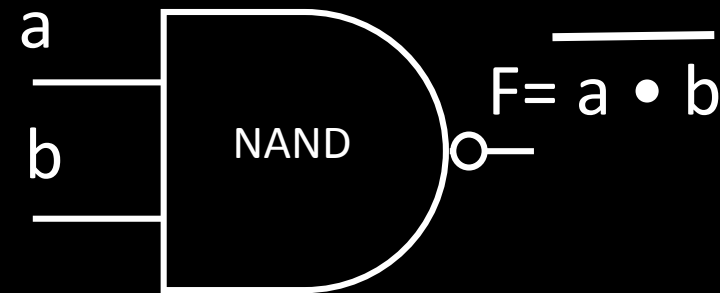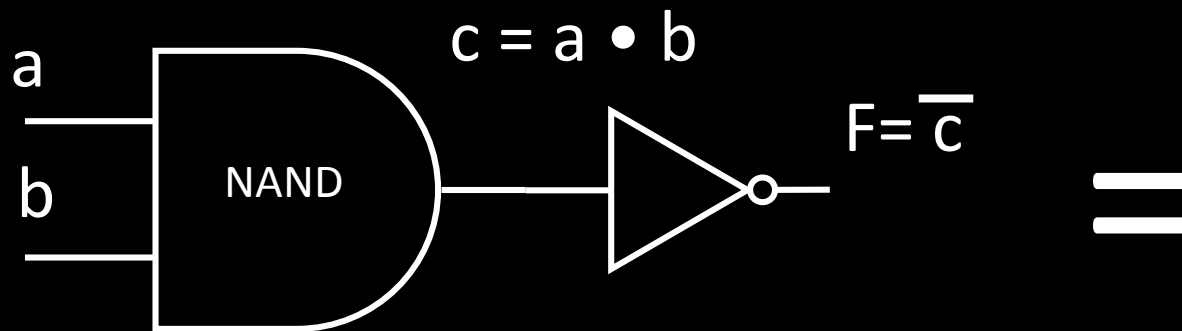


NAND GATE

- This NAND gate has two inputs and an output
- Output is 1 unless both Inputs are 1's, then it's 0

The NAND operation is mathematically defined as the product of two Boolean values

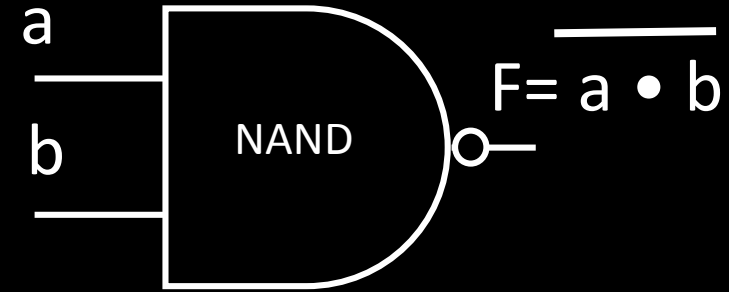Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output



2-Input NAND



A	B	F=A•B
0	0	1
0	1	1
1	0	1
1	1	0



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

NOR GATE

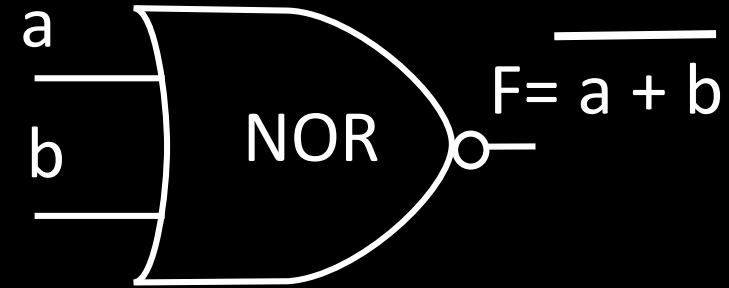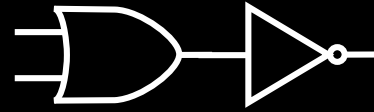

- This NOR gate has two inputs and an output
- Output is 0 if any of the Inputs are 1's

The NOR operation is mathematically defined as the summation of two Boolean values

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output

2-Input NOR

A	B	F=A+B
0	0	1
0	1	0
1	0	0
1	1	0




STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

XOR GATE

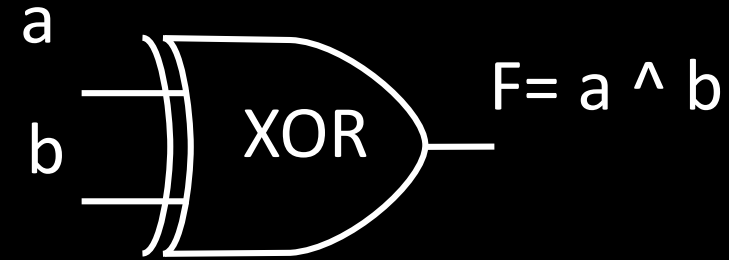- This XOR gate has two inputs and an output
- Output is 1 if the Inputs are different



2-Input XOR

A	B	F=A^B
0	0	0
0	1	1
1	0	1
1	1	0

The XOR operation is mathematically defined as the summation of two Boolean values if they are different

Truth table: tabular form that uniquely represents the relationship between the input variables of a function and its output



STEAM CLOWN™ PRODUCTIONS

REFERENCE SLIDES



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

LEARNING DOMAIN, CTE STANDARDS AND STUFF LIKE THAT...

- Learning Domain
 - [] cognitive [] affective [] psychomotor
 - What are some cognitive skills required for success in your pathway?
 - What are some affective skills required for success in your pathway?
 - What are some psychomotor skills required for success in your pathway?
- Time:
 - Lecture
 - Lab
- Standards
 - CTE
 - CCSS
 - NCSS








RESOURCES & MATERIALS NEEDED






STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

LOGIC GATES

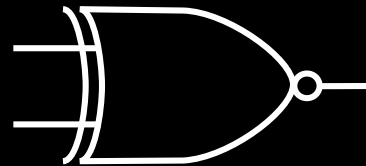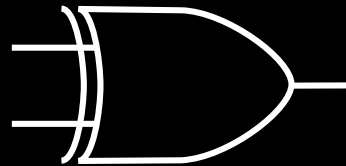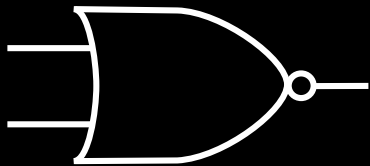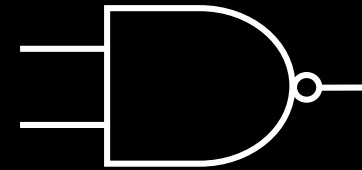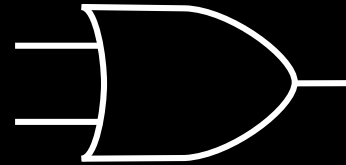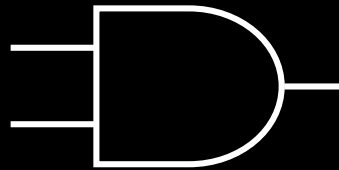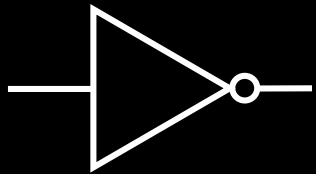

LOGIC GATES

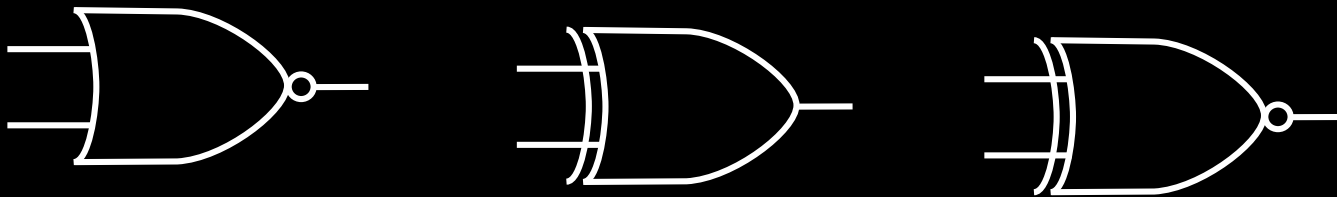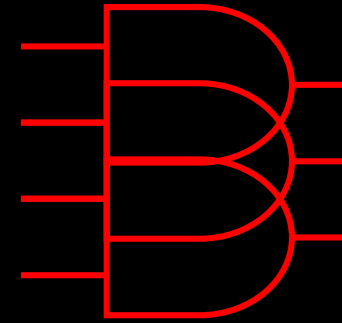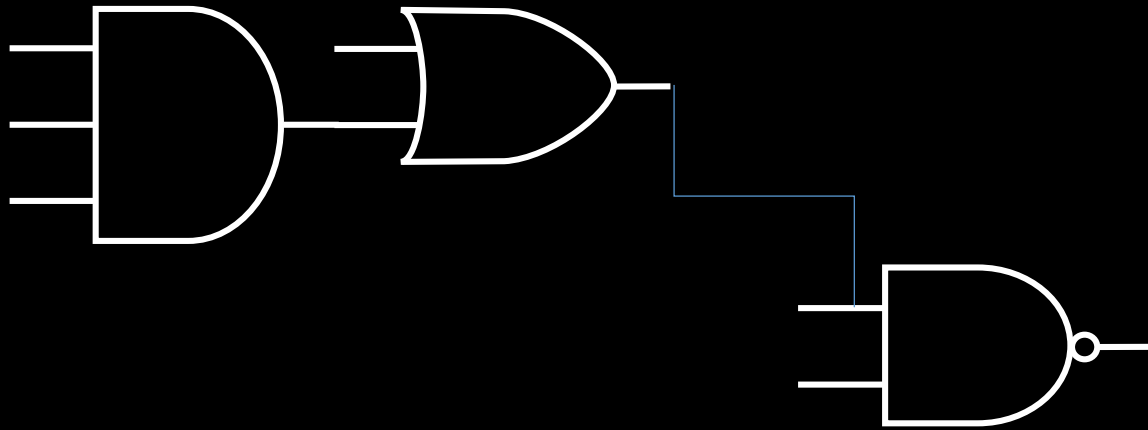

LINKS THAT I MAY USE

- https://www.youtube.com/watch?v=eJHmVlzH_9Q



STEAM CLOWN™ PRODUCTIONS

APPENDIX



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

APPENDIX A: LICENSE & ATTRIBUTION

- This interpretation is primarily the Intellectual Property of Jim Burnham, Top STEAM Clown, at STEAMClown.org
- This presentation and content is distributed under the Creative Commons License CC-by-nc-sa-3.0
- My best attempt to properly attribute, or reference any other sources or work I have used are listed in Appendix B



Under the following terms:



Attribution — You must give [appropriate credit](#), provide a link to the license, and [indicate if changes were made](#). You may do so in any reasonable manner, but not in any way that suggests the licensor endorses you or your use.



NonCommercial — You may not use the material for [commercial purposes](#).



ShareAlike — If you remix, transform, or build upon the material, you must distribute your contributions under the [same license](#) as the original.

No additional restrictions — You may not apply legal terms or [technological measures](#) that legally restrict others from doing anything the license permits.



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™

APPENDIX B: ATTRIBUTION FOR SOURCES USED

- Power Point [Logic Gates Symbols](#) – Oliver Mannay
- Slide Share [Logic Gates](#)
- PPT from Michigan Tech [EE 4271](#)



STEAM CLOWN™
& **Squeaky Hinge**
PRODUCTIONS

© Copyright 2017 STEAM Clown™